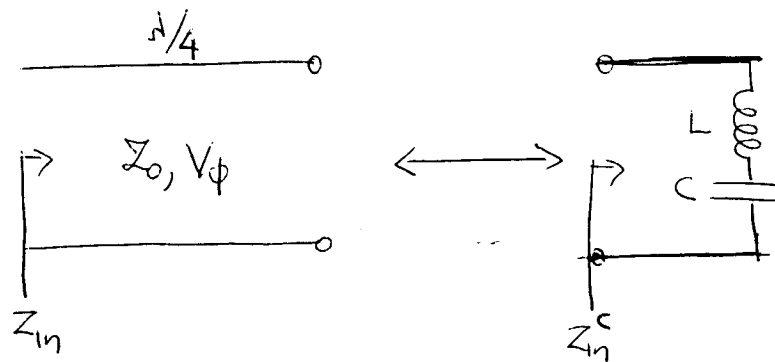


Problem 1 :

For the lumped-element case:

$$Z_{in}^c = j\omega L + \frac{1}{j\omega C}$$


At resonance $\omega = \omega_r = \frac{1}{\sqrt{LC}}$ and $Z_{in}^c = 0$.

Let us expand Z_{in}^c in a Taylor's series about $\omega = \omega_r$:

$$Z_{in}^c \cong Z_{in}^c(\omega_r) + \left. \frac{\partial Z_{in}^c}{\partial \omega} \right|_{\omega_r} (\omega - \omega_r) + \dots$$

$$= 0 + \left(jL + \frac{j}{\omega_r^2 C} \right) (\omega - \omega_r)$$

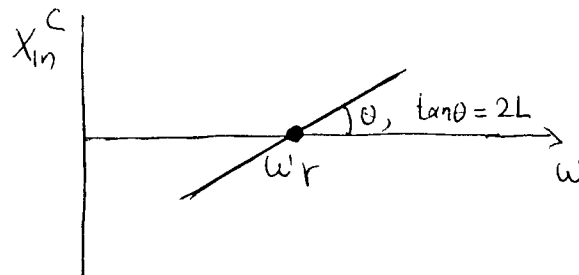Hence, $Z_{in}^c \cong \left(jL + j \frac{1}{\omega_r^2 C} L \right) (\omega - \omega_r) = 2jL (\omega - \omega_r) \dots (1)$



Now consider the distributed network case:

$$Z_{in} = -j Z_0 \cot \beta l = -j Z_0 \frac{\cos(\beta l)}{\sin(\beta l)}$$

When $\beta l = \frac{\pi}{2}$, $Z_{in}(\beta l) = 0$ since the open becomes a short at ω_r

Let us define then the resonant frequency from $\frac{\omega_r l}{V_\phi} = \frac{\pi}{2}$

i.e. $\boxed{\omega_r = \frac{\pi V_\phi}{2l}}$, $l = \lambda/4$ (2)

Expand $Z_{in}(\beta l)$ about $\beta l = \frac{\pi}{2}$, i.e.: Let $\beta l = \frac{\pi}{2} + \Delta\beta l$

$$\Rightarrow \cos(\beta l) = \cos\left(\frac{\pi}{2} + \Delta\beta l\right) = -\sin(\Delta\beta l) \approx -\Delta\beta l$$

$$\sin(\beta l) = \sin\left(\frac{\pi}{2} + \Delta\beta l\right) = \cos(\Delta\beta l) \approx 1$$

and $\Delta\beta l = \frac{(\omega - \omega_r)l}{V_\phi}$, hence

$$Z_{in}(\omega) \approx j Z_0 \Delta\beta l = j \frac{Z_0 l}{V_\phi} (\omega - \omega_r) \dots (3)$$


Comparing (1) and (3) we see that they behave in a

similar way. Also, $2L \equiv \frac{Z_0 l}{V_\phi} \Rightarrow \boxed{L = \frac{Z_0 l}{2V_\phi}, l = \lambda/4}$

and $\omega_r = \frac{\pi V_\phi}{2l} = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{C = \frac{1}{L\omega_r^2} = \frac{8l}{Z_0 \pi^2 V_\phi}}$

where L, C are the equivalent series inductance and capacitance.

Problem 2

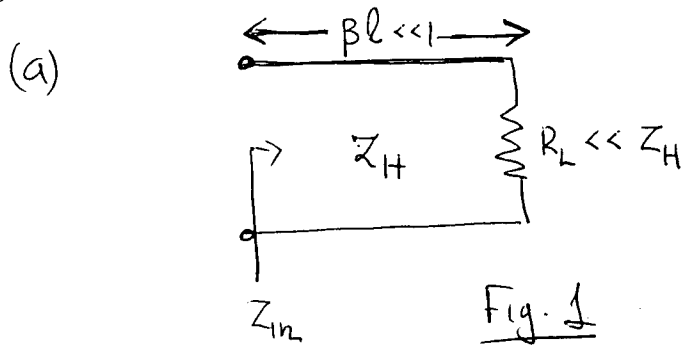


From the impedance transformation:

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \approx \frac{Z_0 Z_L + j Z_0^2 \beta l}{Z_0 + \underbrace{j Z_L \beta l}_{\text{small}}} \approx R_L + j Z_0 \beta l$$


i.e. for $\beta l \ll 1$ and $R_L \ll Z_0$

$$Z_{in} \approx R_L + j \omega \left(\frac{Z_0 l}{v_\phi} \right) \equiv R_L + j \omega L_{eq}$$

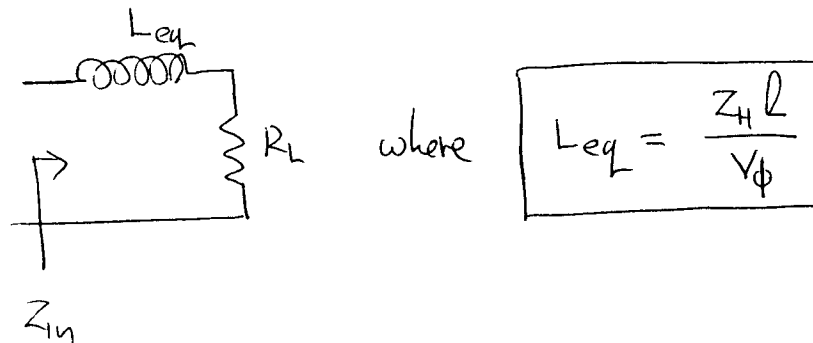This shows that the lumped equivalent circuit to Fig. 1 is



(b)

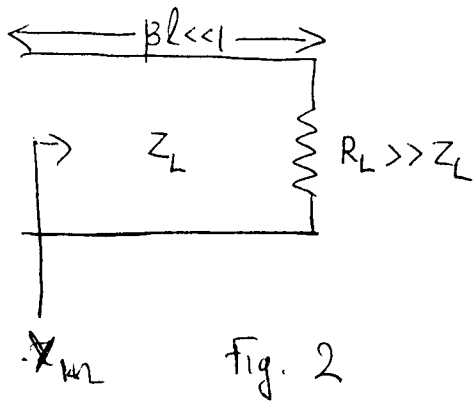


Since we are trying to show equivalence to a shunt element, it is more convenient to use admittances:

$$Y_{in} = \frac{1}{Z_L} \frac{Z_L + jR_L \tan \beta l}{R_L + \underbrace{jZ_L \tan \beta l}_{\text{very small}}} \approx \frac{1}{Z_L} \frac{Z_L + jR_L \beta l}{R_L}$$

$$\Rightarrow Y_{in} \approx \frac{1}{R_L} + j \frac{\beta l}{Z_L} = \frac{1}{R_L} + j\omega \left(\frac{l}{v_\phi Z_L} \right) \equiv \frac{1}{R_L} + j\omega C_{eq}$$

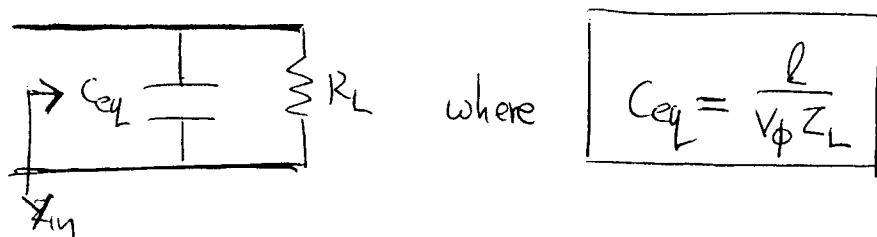This shows that the equivalent lumped circuit to fig. 2 is



These results can be generalized for complex loads as well.

The corresponding conditions are $|Z_{load}| \gg |Z_{line}|$ depending

on whether we would like to simulate a series-inductor or a shunt capacitor.

Problem 3 :

The normalized to $Z_1 = 50\Omega$ impedance at the load is

$$\bar{Z}_L = Z_L/50 = 2 + j1.5$$

Move 0.12λ towards the generator to reach $\bar{Z}_A = 1 - j1.3$

Since the inductance is in series

$$Z_B = Z_A + j30 \Rightarrow \bar{Z}_B = \bar{Z}_A + 0.6 = 1 - j0.7$$

On the other hand the capacitance is shunt connected. Therefore it is easier to use admittances.

$\bar{Y}_B = 1/\bar{Z}_B = 0.67 + 0.47j$ which is found by moving to the exact opposite point of Z_B on its SWR circle.

$$\text{Now, } Y_C = Y_B + Y_{cap}, \quad Y_{cap} = \frac{1}{j200} = 0.005j \Rightarrow \bar{Y}_{cap} = Y_{cap}/Y_0 = Z_0 Y_{cap} \\ = 50 Y_{cap} = 0.25j$$

$$\Rightarrow \bar{Y}_C = \bar{Y}_B + \bar{Y}_{cap} = 0.67 + 0.72j$$

But the input-line is normalized to $Z_2 = 150\Omega$. Hence I should

first denormalize \bar{Y}_C to get $Y_C = \frac{1}{50}(0.67 + 0.72j) = 0.0134 + 0.0144j$

Normalize to $Z_2 = 150\Omega \Rightarrow \bar{Y}_C = 150 Y_C = 2.01 + 2.16j$.


Move on the corresponding SWR circle 0.06λ toward the generator to reach \bar{Y}_{in} .

Finally moving to the opposite point of the \bar{Y}_{in} SWR-circle, we obtain

$$\bar{Z}_{in} \approx 0.22 + 0.125j, \text{ Hence } Z_{in} = \bar{Z}_{in}(150) = 33 + j18.75 \quad (33.7 + j17.5j)$$


Exact solution.

IMPEDANCE OR ADMITTANCE COORDINATES

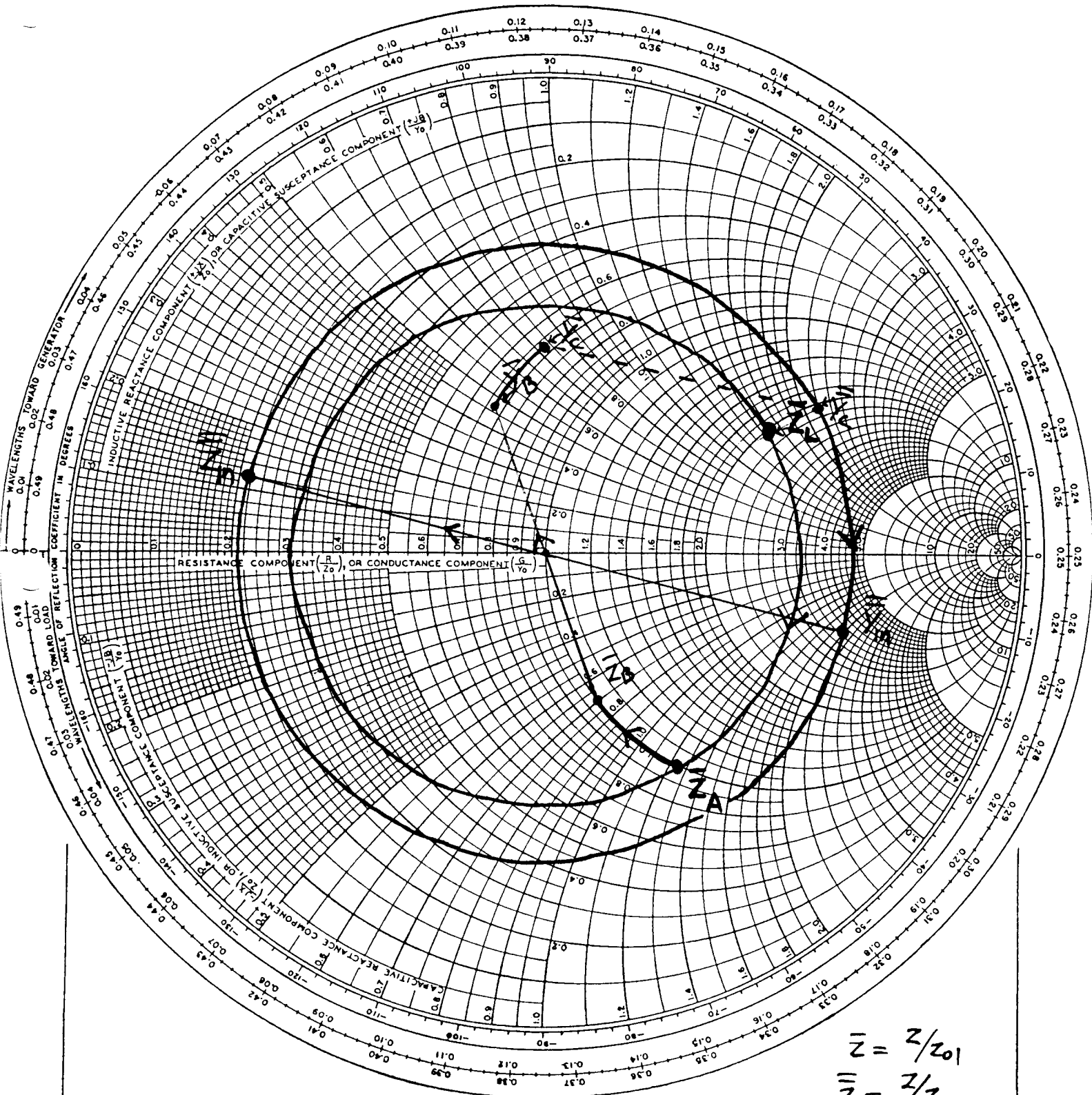

$$\bar{Z} = Z/Z_0$$

$$\bar{Z} = Z/Z_0$$

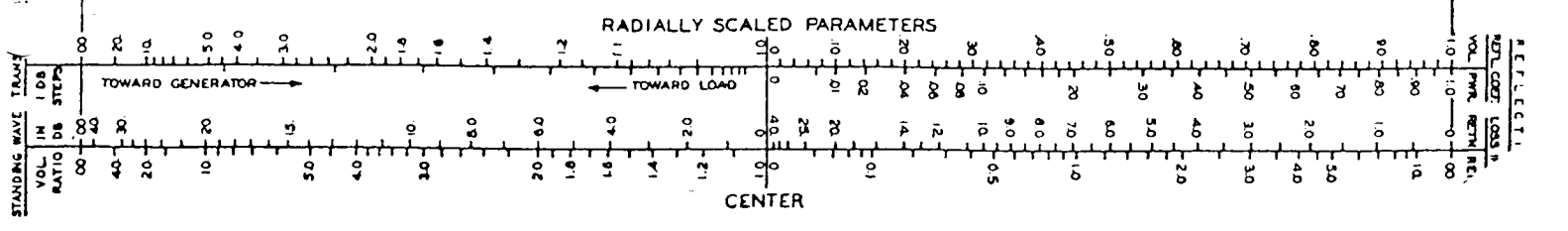

Problem 4 :

5.9 Smith chart solution

1. Plot $y_L = 1.4 + j2.0$ (ADMITTANCE CHART)
2. plot rotated $1 + jb$ circle
3. add a stub susceptance of $-j0.1$ to y_L to move to rotated $1 + jb$ circle
4. move $\lambda/8$ towards generator, to $1 + jb$ circle
5. add a stub susceptance of $+j1.6$ to move to center of chart.
6. The open-circuited stub lengths are,

$$l_1 = 0.484 \lambda \checkmark$$

$$l_2 = 0.161 \lambda \checkmark$$


(Analytically, we obtain $l_1 = 0.487 \lambda$, $l_2 = 0.163 \lambda$)


The alternative matching solution has,

$$l'_1 = 0.326 \lambda \checkmark$$

$$l'_2 = 0.053 \lambda \checkmark$$

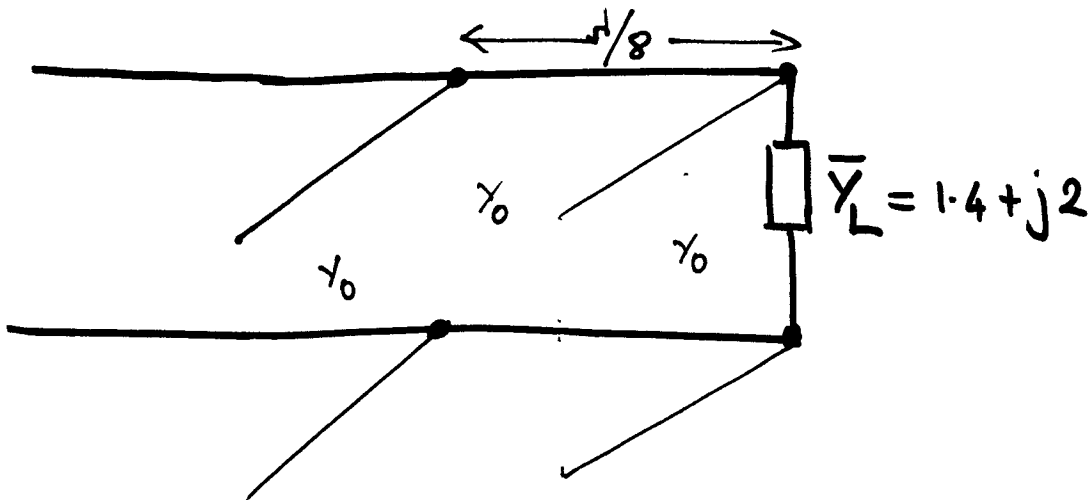The Smith chart for the first solution is shown on the following page.



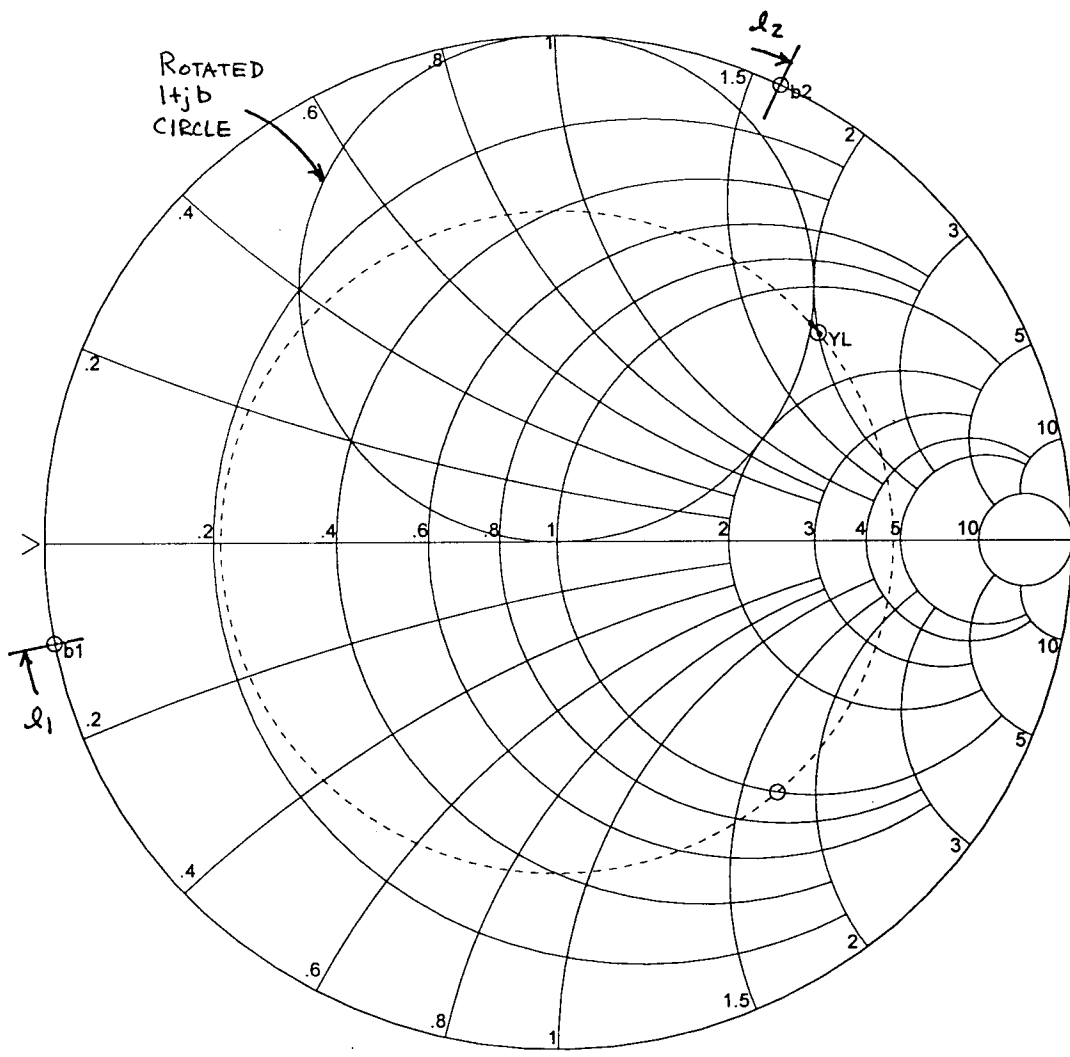

Smith chart for Problem 5.9