
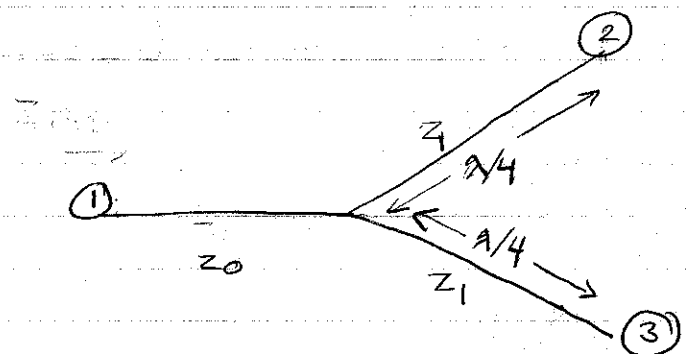


Question # 1 Problem Set # 7

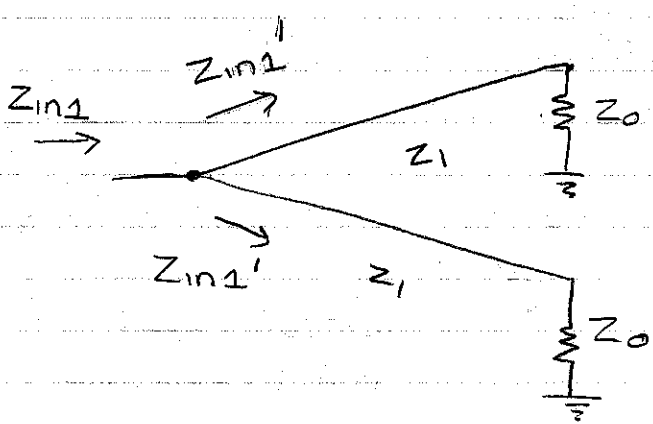

Finding S<sub>11</sub>




$$\begin{aligned}
 Z_{in} &= Z_{in1}' \parallel Z_{in1}' \\
 &= \frac{Z_{in1}'}{2} \\
 &= \frac{z_1^2}{z_0} \left( \frac{1}{2} \right)
 \end{aligned}$$


$$S_{11} = \frac{Z_{in} - z_0}{Z_{in} + z_0} = \frac{\frac{z_1^2}{2z_0} - z_0}{\frac{z_1^2}{2z_0} + z_0} = \frac{z_1^2 - 2z_0^2}{z_1^2 + 2z_0^2}$$

Finding  $S_{22}$  ( $S_{22} = S_{33}$  due to symmetry)

Use even/odd analysis

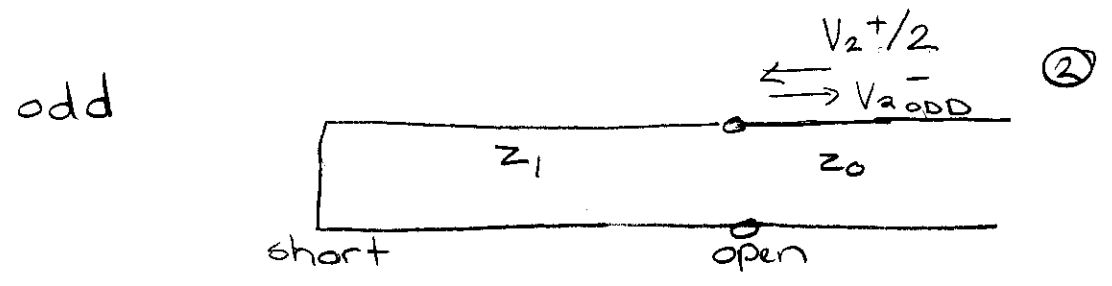

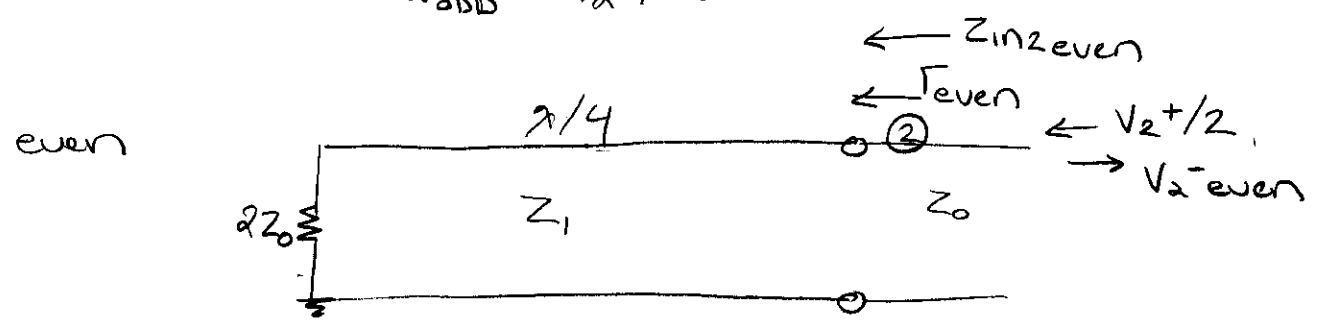since you see an open circuit looking into port 2  
 $V_{2\_ODD}^- = V_{2\_ODD}^+$



$$\Gamma_{\text{Even}} = \frac{Z_{\text{in even}} - Z_0}{Z_{\text{in even}} + Z_0} \qquad Z_{\text{in even}} = \frac{Z_1^2}{2Z_0}$$

$$= \frac{\frac{Z_1^2}{2Z_0} - Z_0}{\frac{Z_1^2}{2Z_0} + Z_0}$$

$$= \frac{Z_1^2 - 2Z_0^2}{Z_1^2 + 2Z_0^2}$$

∴  $V_{2\_even}^- = \left( \frac{Z_1^2 - 2Z_0^2}{Z_1^2 + 2Z_0^2} \right) V_{2\_even}^+$


superpose both solutions

$$S_{22} = \frac{V_{2\_ODD}^- + V_{2\_even}^-}{V_{2\_ODD}^+ + V_{2\_even}^+}$$


$$= \frac{V_2^+ + \left( \frac{Z_1^2 - 2Z_0^2}{Z_1^2 + 2Z_0^2} \right) V_2^+}{2V_2^+} = \frac{Z_1^2}{Z_1^2 + 2Z_0^2}$$

Finding  $S_{12}$  ( $S_{12} = S_{21}$  due to reciprocity)

Use even/odd analysis

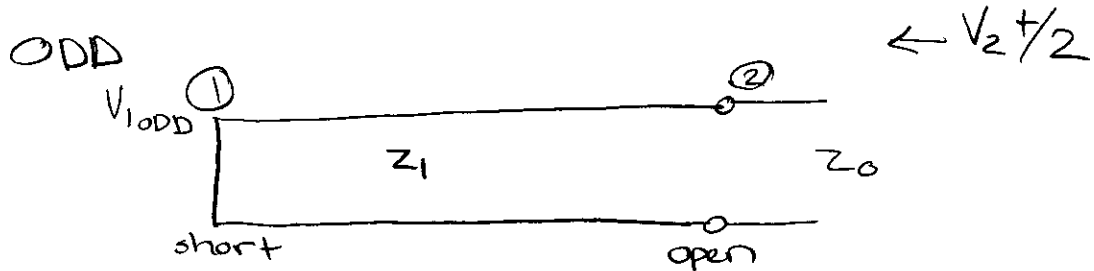

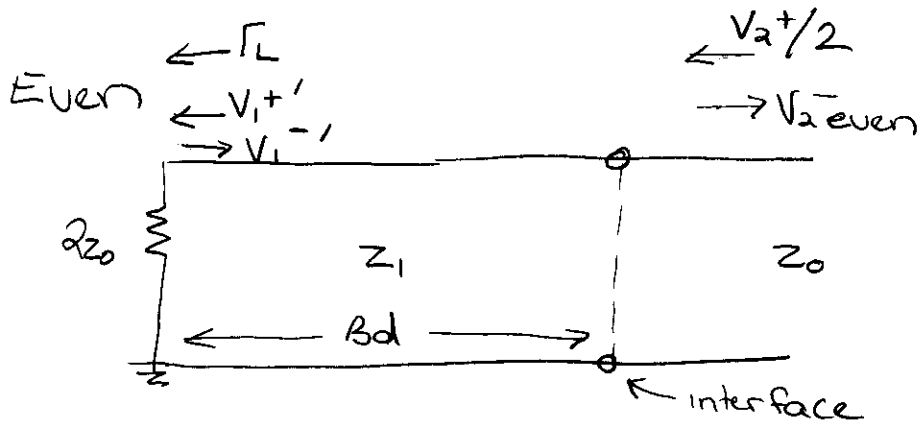Since you see a short at port 1  
 $V_{1,ODD} = 0V$  (voltage at port 1)



note  $V_{2^-_{even}} = \Gamma_{even} V_2^+/2$

Boundary condition at interface

$$V_1^+ e^{j\beta d} + V_1^- e^{-j\beta d} = \frac{V_2^+}{2} + V_{2^-_{even}}$$

$$\because \beta d = \frac{2\pi \lambda}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \quad \therefore j V_1^+ - j V_1^- = \frac{V_2^+}{2} + V_{2^-_{even}}$$

$$j V_1^+ (1 - \Gamma_L) = \frac{V_2^+}{2} (1 + \Gamma_{even})$$

$$V_1^+ = \frac{\frac{V_2^+}{2} (1 + \Gamma_{even})}{j (1 - \Gamma_L)}$$

$$S_{12} = \frac{V_1^{+'} + V_1^{-'} + 0}{\frac{V_2^+}{2} + \frac{V_2^+}{2}}$$

$$= \frac{V_1^{+'} + V_1^{-'}}{V_2^+}$$

$$= \frac{V_1^{+'}(1 + \Gamma_L)}{V_2^+}$$

$$S_{12} = \frac{(1 + \Gamma_L)(1 + \Gamma_{even})}{2j(1 - \Gamma_L)}$$

recall  $\Gamma_{even} = \frac{z_1^2 - 2z_0^2}{z_1^2 + 2z_0^2}$

$$\Gamma_L = \frac{2z_0 - z_1}{2z_0 + z_1}$$


$$\therefore S_{12} = \frac{\left(\frac{4z_0}{2z_0 + z_1}\right) \left(\frac{2z_1^2}{z_1^2 + 2z_0^2}\right)}{2j \left(\frac{2z_1}{2z_0 + z_1}\right)}$$

$$= \frac{2z_1^2 z_0 / z_1}{(z_1^2 + 2z_0^2)j}$$


$$S_{12} = \frac{-2z_1 z_0 j}{z_1^2 + 2z_0^2}$$

Finding  $S_{23}$  ( $S_{23} = S_{32}$  due to reciprocity, symmetry)

Use: even/odd analysis

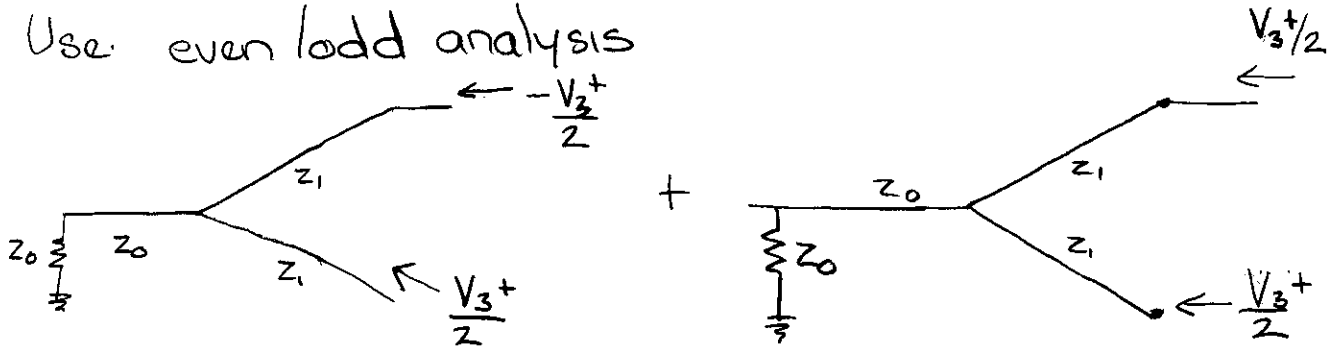


ODD

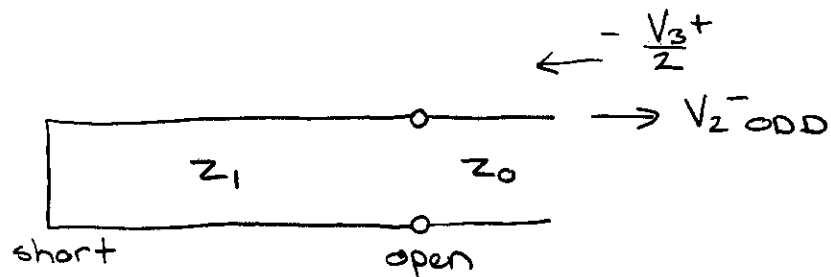

$V_{2-odd} = -\frac{V_{3+}}{2}$  since you see an open at port 2 (reflection coefficient = 1)

EVEN

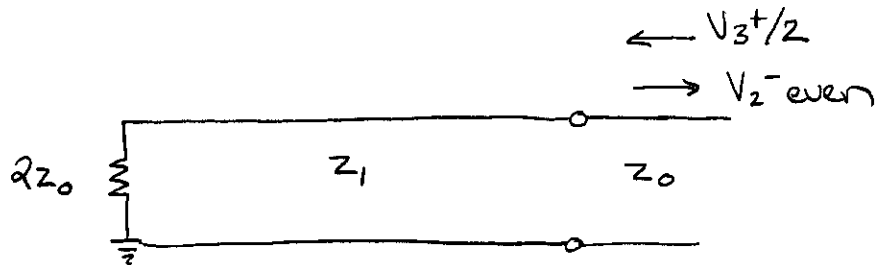


$V_{2-even} = \left( \frac{z_1^2 - 2z_0^2}{z_1^2 + 2z_0^2} \right) \left( \frac{V_{3+}}{2} \right)$  same as  $V_{2-even}$  in  $S_{22}$  calculation

$$S_{23} = \frac{V_{2-odd} + V_{2-even}}{\frac{V_{3+}}{2} + \frac{V_{3+}}{2}} = \frac{1}{2} \left( \frac{-4z_0^2}{z_1^2 + 2z_0^2} \right)$$

$$S_{23} = \frac{-2z_0^2}{z_1^2 + 2z_0^2}$$

7.3 :

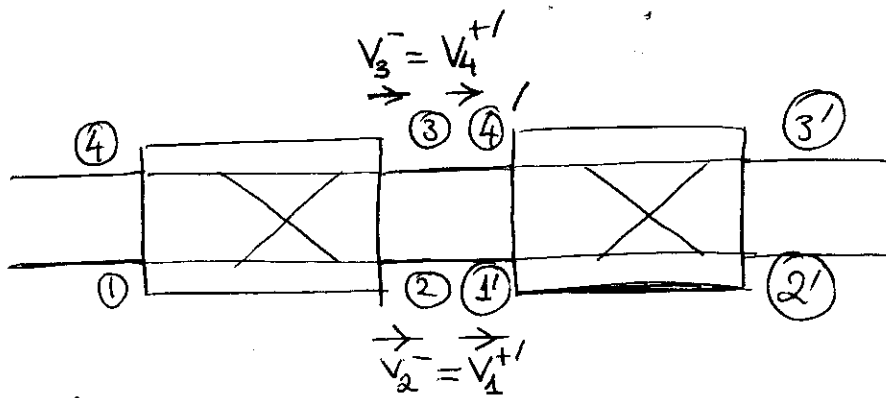

The coupling  $C = -20 \log \beta = 8.34 \text{ dB} \Rightarrow \beta = |S_{13}| = 0.383$   
 $\alpha = \sqrt{1 - \beta^2} = 0.924$

In the first coupler,  $V_1^+ = 1 \angle 0^\circ$  :

Coupled-voltage :  $V_3^- = j\beta V_1^+ = 0.383 \angle 90^\circ$

Through-voltage :  $V_2^- = \alpha V_1^+ = 0.924 \angle 0^\circ$

$V_2^-$ ,  $V_3^-$  become the input to the second coupler :


$$V_3^{-'} = j\beta V_1^{+'} + \alpha V_4^{+'} = j\beta V_2^- + \alpha V_3^- = 0.707 \angle 90^\circ$$

Also  $V_2^{-'} = \alpha V_1^{+'} + j\beta V_4^{+'} = \alpha V_2^- + j\beta V_3^- = 0.707 \angle 0^\circ$

In other words, the output suggests that the cascaded  $C = 8.34 \text{ dB}$  couplers function like a single 3dB hybrid.


# Problem 7.7 :

resistive divider :

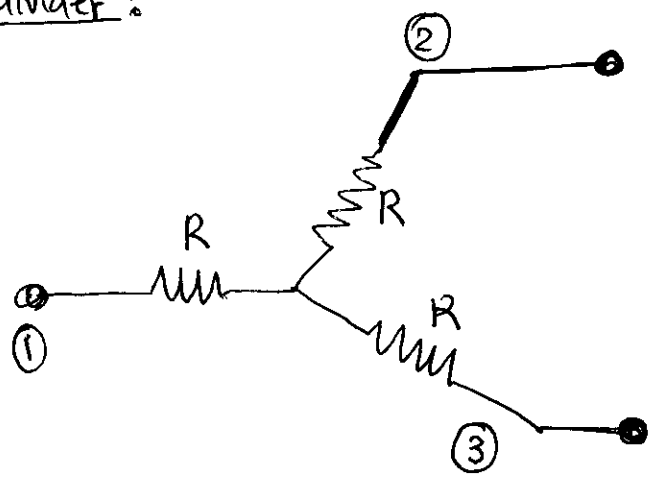

Derivation of the S-matrix :

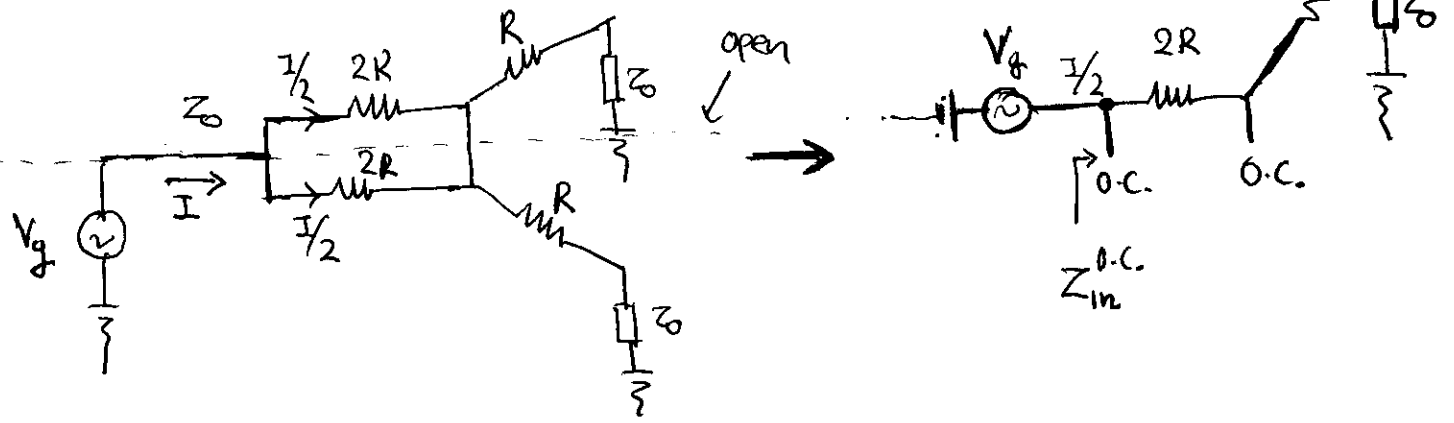Excite port ① and match ports 2 and 3 to  $Z_0 = 100 \Omega$




$$Z_{in} = \frac{V_g}{I} = \frac{1}{2} \frac{V_g}{I/2} = \frac{1}{2} Z_{in}^{o.c.} = \frac{1}{2} (2R + R + Z_0) = \frac{1}{2} (3R + Z_0)$$

For a matched port ①,  $Z_{in} = Z_0$ , i.e.  $3R + Z_0 = 2Z_0 \Rightarrow$

$$R = \frac{Z_0}{3} = 33 \Omega$$

Hence with  $R = 33.3 \Omega$ ,  $S_{11} = 0$

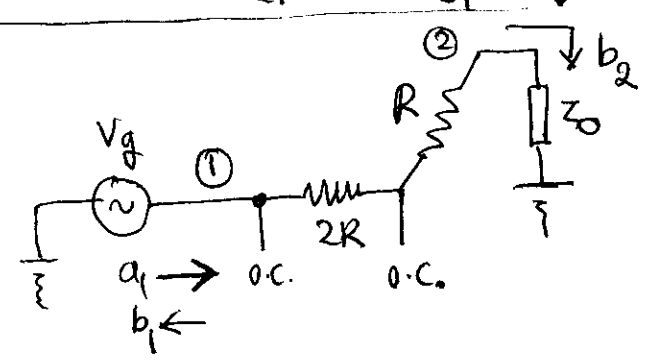Derivation of  $S_{21}$  and  $S_{31}$  :



$$V_1 = \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_0} a_1 = V_1^+$$

$$V_2 = \sqrt{Z_0} (a_2 + b_2) = \sqrt{Z_0} b_2 = V_2^-$$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{\sqrt{Z_0} b_2}{\sqrt{Z_0} a_1} = \frac{V_2}{V_1}$$


From the voltage divider :  $V_2 = V_1 \frac{Z_0}{3R + Z_0} = V_1 \frac{Z_0}{2Z_0} = \frac{1}{2} V_1$

i.e.  $S_{21} = \frac{1}{2}$  and from symmetry  $S_{31} = \frac{1}{2}$  as well.

From reciprocity,  $S_{12} = S_{21} = \frac{1}{2}$   
 $S_{13} = S_{31} = \frac{1}{2}$

Derivation of  $S_{22}/S_{33}$  :

Even-Excitation :

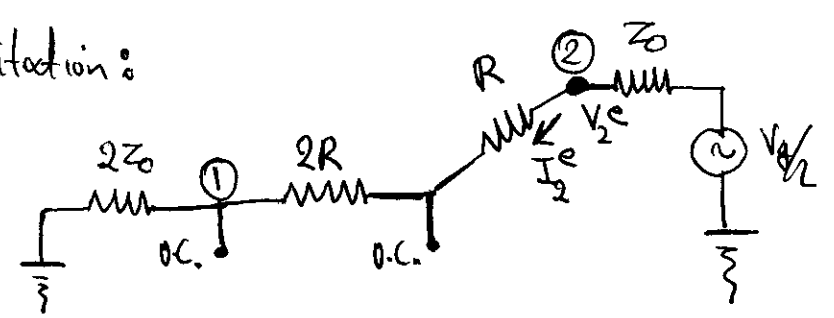


$$V_2^e = \frac{V_g/2}{3R + 3Z_0} (3R + 2Z_0)$$

$$I_2^e = \frac{3}{4} \frac{V_g}{2}$$

$$I_2^e = \frac{V_g/2}{3R + 3Z_0} = \frac{1}{4Z_0} \frac{V_g}{2}$$

Odd-Excitation :

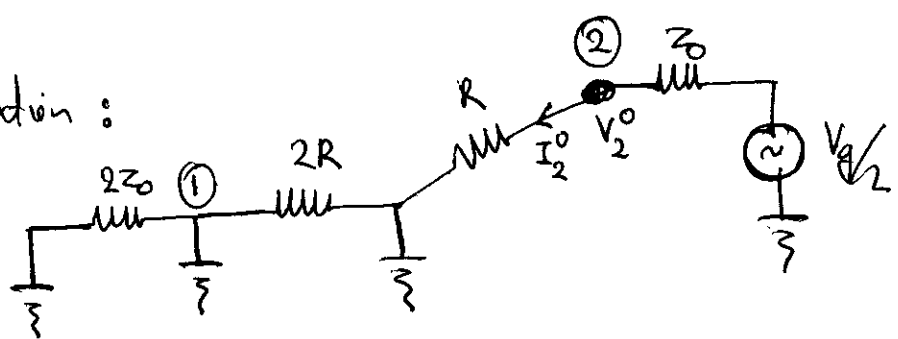

$$V_2^o = \frac{V_g/2}{R + Z_0} R = \frac{1}{4} \frac{V_g}{2}$$

$$I_2^o = \frac{V_g/2}{R + Z_0} = \frac{3}{4Z_0} \frac{V_g}{2}$$

i.e.  $Z_{in}^{(2)} = \frac{V_2^e + V_2^o}{I_2^e + I_2^o} = \frac{\frac{3}{4} + \frac{1}{4}}{\frac{1}{4} + \frac{3}{4}} Z_0 = Z_0 //$

Hence  $S_{22} = 0$ .  
 By symmetry  $S_{33} = 0$ .



Derivation of  $S_{32}$  (Isolation) :  $S_{32} = \frac{V_3^-}{V_2^+} = \frac{V_3}{V_2}$

Even Excitation : Same as port 3 i.e.  $V_3^e = V_2^e = \frac{3}{4} \frac{V_0}{2} =$


Odd Excitation :  $V_3^o = -V_2^o = -\frac{1}{4} \frac{V_0}{2}$

Therefore  $S_{32} = \frac{V_3^e + V_3^o}{V_2^e + V_2^o} = \frac{V_2^e - V_2^o}{V_2^e + V_2^o} = \frac{\frac{3}{4} - \frac{1}{4}}{\frac{3}{4} + \frac{1}{4}} = \frac{1}{2}$

i.e. there is no perfect isolation.

From reciprocity  $S_{23} = 0$ .

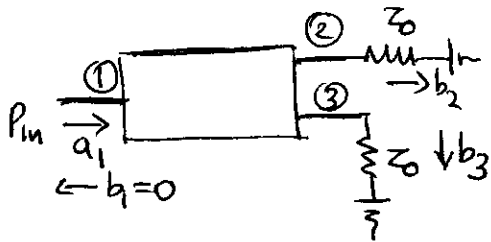Finally  $[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$




$$P_3 = \frac{1}{2} |b_3|^2$$

But  $b_3 = S_{31}a_1 + S_{32}a_2 + S_{33}a_3$   
 i.e.  $b_3 = S_{31}a_1$

Hence  $P_3 = \frac{1}{2} |S_{31}|^2 |a_1|^2 = |S_{31}|^2 P_{in}$

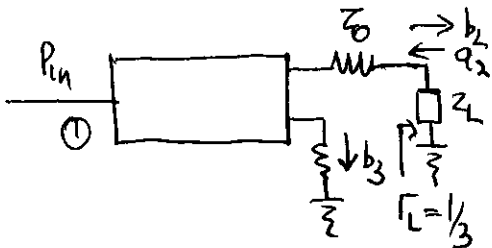For port 2 matched  $P_3 = \frac{1}{4} P_{in}$



This time  $b_3 = S_{31}a_1 + S_{32}a_2$

But  $\frac{a_2}{b_2} = \Gamma = \frac{1}{3}$ , i.e.  $b_3 = S_{31}a_1 + S_{32}\Gamma b_2$

Also  $b_2 = S_{21}a_1 + S_{22}a_2 + S_{23}a_3$

Hence  $b_3 = S_{31}a_1 + S_{32}\Gamma b_2 = S_{31}a_1 + S_{32}S_{21}\Gamma a_1$

and  $b_3 = \left(\frac{1}{2} + \frac{1}{4} \frac{1}{3}\right) a_1 = 0.583 a_1$

i.e.  $P_3' = \frac{1}{2} |a_1|^2 (0.583)^2 = (0.583)^2 P_{in}$ . Hence  $10 \log \frac{P_3}{P_3'} = 10 \log \frac{0.25}{0.34} = -1.3 \text{ dB}$

# Problem 7-32 :

The idea here is to exploit the symmetry that exists along the line  $Z_0$ . The input port (#1) is then treated as follows:

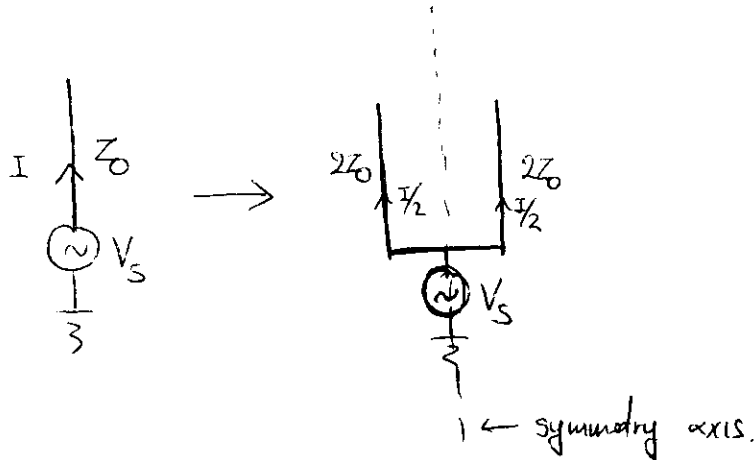


Fig-1

Along the symmetry axis, I can place open-circuits (magnetic wall):

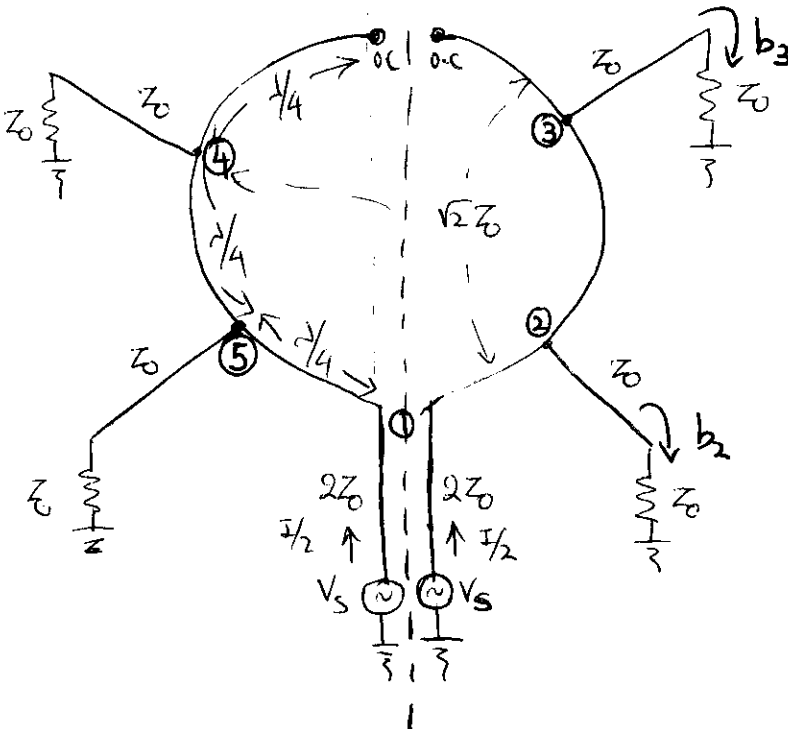


Fig. 2

Considering the right half:

1) The o.c. becomes a short at port-3. Therefore,  
 $b_3=0$  and  $S_{31}=0$ . By symmetry  $S_{41}=0$  as well.

2) The short at port ③ becomes an open at port ②.  
 Therefore, for each half we have:


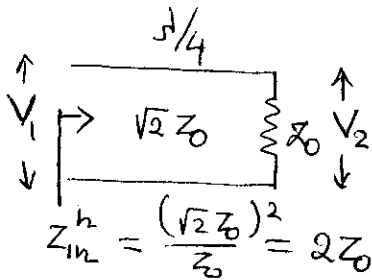


Fig. 3

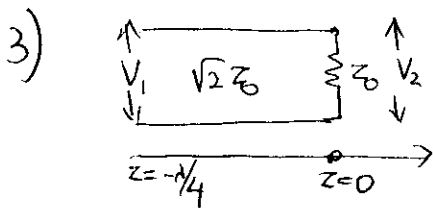Hence the input-impedance at port ① is  $2Z_0 // 2Z_0 = Z_0$ , i.e. port ① is matched and  $b_1=0$  ( $S_{11}=0$ ).



$$\begin{aligned}
 V &= V_+ (e^{-j\beta z} + \Gamma e^{j\beta z}) \\
 \Rightarrow \left. \begin{aligned} V_2 &= V(z=0) = V_+ (1 + \Gamma) \\ V_1 &= V(z=l/4) = jV_+ (1 - \Gamma) \end{aligned} \right\} \Rightarrow \frac{V_2}{V_1} = \frac{1}{j} \frac{1 + \Gamma}{1 - \Gamma} \\
 &= \frac{1}{j} \frac{Z_0}{Z_0 \sqrt{2}} = \frac{-j}{\sqrt{2}}
 \end{aligned}$$

Therefore,  $S_{21} = \frac{V_2}{V_1} = -\frac{j}{\sqrt{2}}$

Finally :

$$\begin{aligned}
 V_1^- &= 0 \\
 V_2^- &= V_5^- = S_{21} V_1^+ = -\frac{j}{\sqrt{2}} \\
 V_3^- &= V_4^- = 0
 \end{aligned}$$

Note that  $|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 + |S_{51}|^2 = 0 + \frac{1}{2} + 0 + 0 + \frac{1}{2} = 1$   
 (lossless condition). Power is equally split between ports ② and ⑤