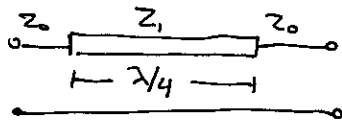



# ECE424F - 2001: Homework #8

## Question # 1

Step #1:



→ Find the S-parameters for this line.

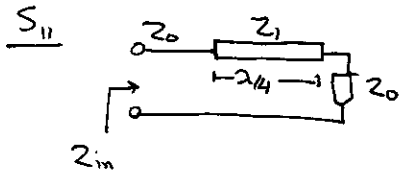

$$Z_{in} = \frac{Z_1^2}{Z_0} \Rightarrow S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_1^2/Z_0 - Z_0}{Z_1^2/Z_0 + Z_0} = \frac{Z_1^2 - Z_0^2}{Z_1^2 + Z_0^2}$$

$$\therefore \boxed{S_{11} = S_{22} = \frac{Z_1^2 - Z_0^2}{Z_1^2 + Z_0^2}}$$

S<sub>12</sub>

The line is lossless  $\Rightarrow \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

$\rightarrow S_{11} S_{12}^* + S_{12} S_{21}^* = 0$  But  $S_{11}$  is real  $\Rightarrow S_{12} + S_{12}^* = 0$


$\therefore S_{12} = S_{21}$  is imaginary

Also,  $|S_{21}|^2 = 1 - |S_{11}|^2 = \frac{4Z_1^2 Z_0^2}{(Z_0^2 + Z_1^2)^2}$  from the lossless condition

So  $S_{21} = \pm j \frac{2Z_0 Z_1}{Z_0^2 + Z_1^2}$ , choose the  $-j$  branch so that when  $Z_0 = Z_1$ ,  $S_{21} = -j = e^{-j\pi/2}$

$\xrightarrow{a_1} \xrightarrow{b_2 = S_{21} a_1} -j a_1$

OR: S<sub>12</sub>

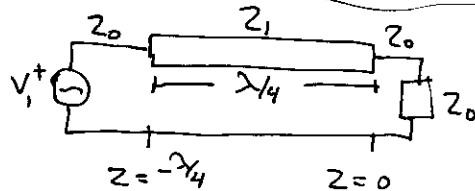

Voltage along line  $\ni V(z) = V^+(e^{-j\beta z} + \Gamma_L e^{j\beta z})$   
 where  $\Gamma_L = \frac{Z_0 - Z_1}{Z_0 + Z_1}$

①  $V(z=0) = V^+(1 + \Gamma_L) = V_2^+ + V_2^- = V_2^-$  (Since  $V_2^+ = 0$  due to matched port #2)

②  $V(z = -\lambda/4) = V^+(j - j\Gamma_L) = V_1^+ + V_1^- = V_1^+(1 + S_{11})$  (since  $S_{11} = \frac{V_1^-}{V_1^+}$ )

Using ① + ② to solve for  $S_{21} = \frac{V_2^-}{V_1^+} = (1 + S_{11}) \frac{(1 + \Gamma_L)}{j(1 - \Gamma_L)} = \left( \frac{2Z_1^2}{Z_1^2 + Z_0^2} \right) \left( \frac{2Z_0}{Z_0 + Z_1} \right) \left( \frac{Z_0 + Z_1}{2Z_1} \right) \frac{1}{j}$


$$\therefore \boxed{S_{21} = \frac{-j 2 Z_1 Z_0}{Z_1^2 + Z_0^2}}$$

Steps #2/3:

i) Convert S-matrix to Y-matrix for  $Z_1 = Z_0$ .

$$S = \begin{bmatrix} 0 & -j \\ -j & 0 \end{bmatrix} \Rightarrow Y = \begin{bmatrix} 0 & j/2Z_0 \\ j/2Z_0 & 0 \end{bmatrix} \quad \begin{matrix} L' = Z_0/\omega \\ C' = 1/\omega Z_0 \quad \omega = 2\pi f. \end{matrix}$$


Pi-Equivalent Circuit:

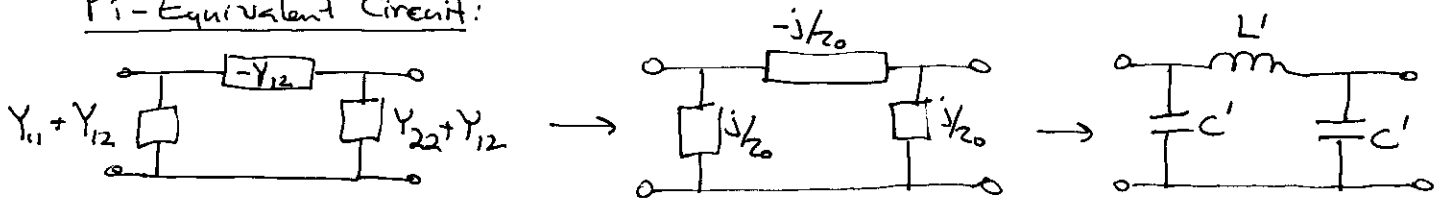


ii) Convert S-matrix to Y-matrix for  $Z_1 = Z_0/\sqrt{2}$

$$S = \begin{bmatrix} -1/3 & -j2\sqrt{2}/3 \\ -j2\sqrt{2}/3 & -1/3 \end{bmatrix} \Rightarrow Y = \begin{bmatrix} 0 & j\sqrt{2}/2Z_0 \\ j\sqrt{2}/2Z_0 & 0 \end{bmatrix} \quad \begin{matrix} L = \frac{\sqrt{2}Z_0}{\omega\sqrt{2}} \\ C = \frac{\sqrt{2}}{2\omega Z_0} \end{matrix}$$


Pi-Equivalent Circuit

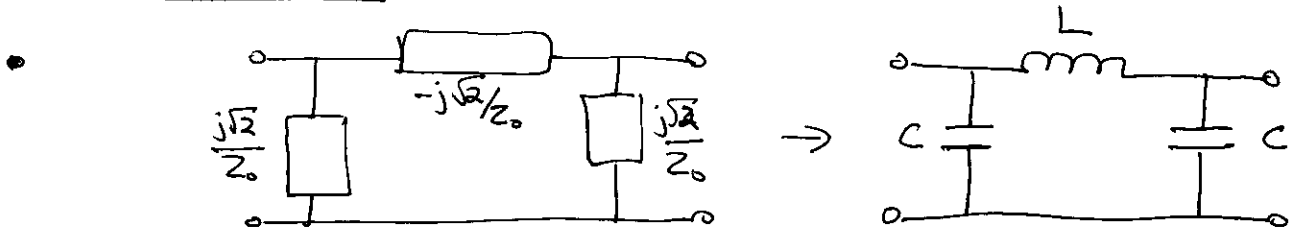

Step #4:

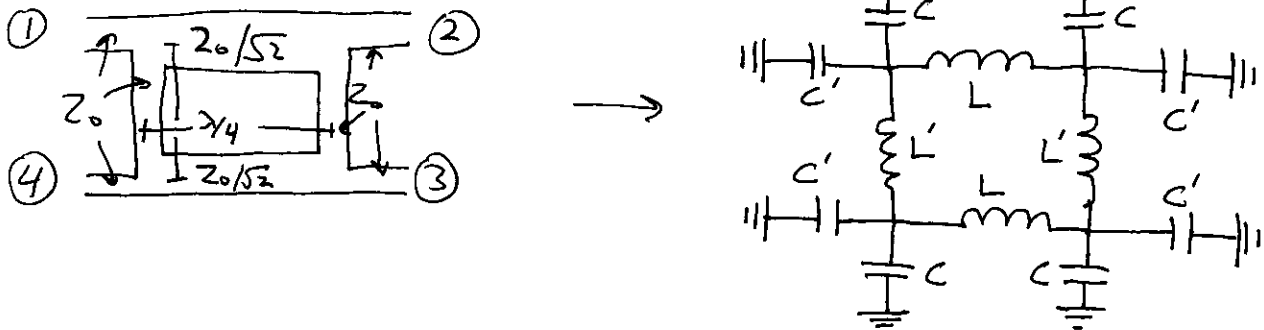

Step #5:

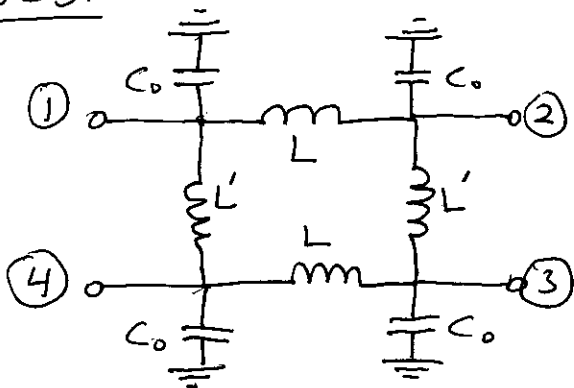

$$\begin{aligned} C_0 &= C + C' \\ \text{At } f &= 16 \text{ GHz}, Z_0 = 50 \Omega \\ L &= Z_0/\sqrt{2}\omega_0 = 5.63 \text{ nH} \\ C &= \frac{\sqrt{2}}{2\omega_0 Z_0} = 4.5 \text{ pF} \\ L' &= Z_0/\omega_0 = 7.96 \text{ nH} \\ C' &= \frac{1}{\omega_0 Z_0} = 3.18 \text{ pF} \end{aligned}$$

7.18 :

$$b = 0.32 \text{ cm}, \epsilon_r = 2.2, Z_{0e} = 70 \Omega, Z_{0o} = 40 \Omega$$

$$\text{Hence } \sqrt{\epsilon_r} Z_{0e} = 104 \Omega, \sqrt{\epsilon_r} Z_{0o} = 59 \Omega$$

From Figure 7.2g

$$s/b = 0.075 \Rightarrow S = 0.24 \text{ mm}$$

$$w/b = 0.67 \Rightarrow W = 2.1 \text{ mm}$$

Problem 7.21 :

$$C = 10^{-10.1/20} = 0.1109, f = 8 \text{ GHz}, Z_0 = 60 \Omega$$

$$Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}} = 67.1 \Omega, Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}} = 53.7 \Omega$$

for a stripline having  $\epsilon_r = 2.2$ ,  $b = 0.32 \text{ cm}$ ,

$$\sqrt{\epsilon_r} Z_{0e} = 93.5 \Omega \text{ and } \sqrt{\epsilon_r} Z_{0o} = 79.7 \Omega$$


From Figure 7.2g

$$s/b = 0.36 \Rightarrow S = 1.15 \text{ mm}$$

$$w/b = 0.60 \Rightarrow W = 1.92 \text{ mm}$$

$$\text{Line length: } l = \frac{\lambda_g}{4} = \frac{c}{4\sqrt{\epsilon_r} f} = 6.32 \text{ mm}$$

Problem 7.28 :

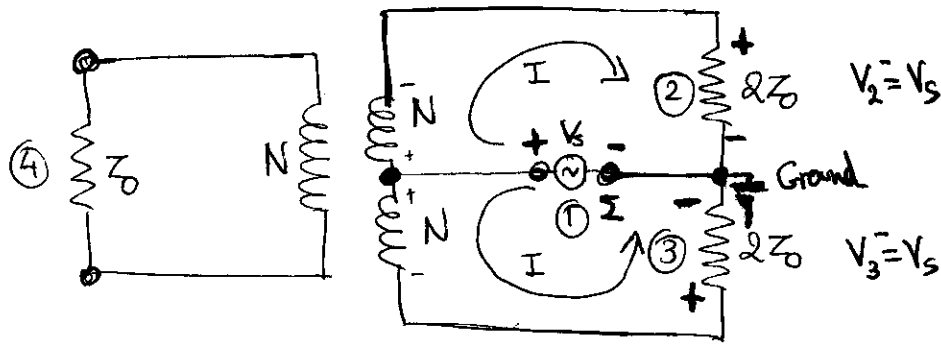

1.) Assume exciting the input port ① while matching the rest ports to their characteristic impedance.

\* Due to symmetry, the primary windings of the transformer are excited out-of-phase. Hence, the induced voltage on the secondary is zero and  $V_4^- = 0$ , i.e. port ④ is isolated and  $S_{41} = S_{14} = 0$ .

\* Since  $I = V_s / 2Z_0$ , the voltages across ports ② and ③ are  $V_2^- = V_s$  and  $V_3^- = +V_s$  respectively.

\*  $V_s$  sees the parallel combination of  $2Z_0 // 2Z_0$ , i.e.  $Z_{in}^{①} = Z_0$ . Hence  $V_1^+ = V_s$ ,  $V_1^- = 0$  and  $S_{11} = 0$  (matched).

\* In order to determine  $S_{21}, S_{31}$  we should be careful and take into account that ports ① and ②, ③ are normalized with a different characteristic impedance. Thus, we should use generalized scattering parameters:

$$S_{21} = \frac{b_2}{a_1} = \frac{V_2^- / \sqrt{2Z_0}}{V_1^+ / \sqrt{Z_0}} = \frac{V_2^-}{V_1^+ \sqrt{2}}$$

Similarly,

$$S_{31} = \frac{V_3^-}{V_1^+} \frac{1}{\sqrt{2}}$$

I.e  $S_{21} = \frac{V_2^-}{V_1^+ \sqrt{2}} = \frac{V_s}{V_s \sqrt{2}} = \frac{1}{\sqrt{2}}$


and  $S_{31} = \frac{V_3^-}{V_1^+ \sqrt{2}} = \frac{-V_s}{V_s \sqrt{2}} = -\frac{1}{\sqrt{2}}$

finally,  $S_{21} = S_{12} = \frac{1}{\sqrt{2}}$

$S_{31} = S_{13} = -\frac{1}{\sqrt{2}}$  ✓

Note that in general, passive RLC circuits are reciprocal.

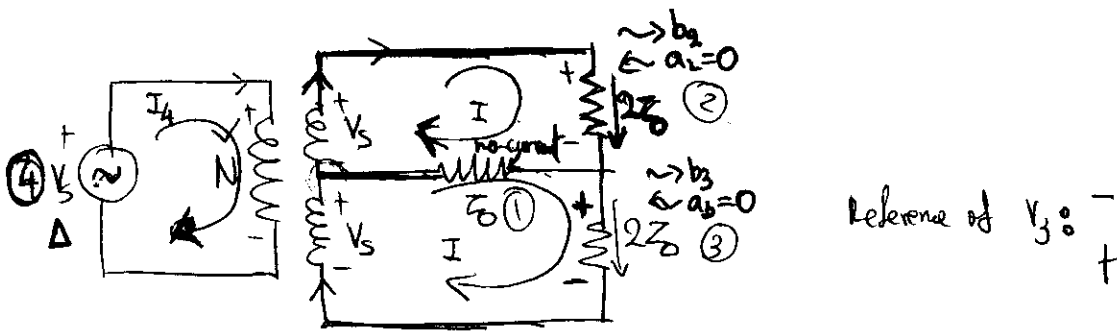2) Assume now exciting port #4 while matching the rest ports:



\* In this case, port ① is excited in an odd fashion and no current passes through  $Z_0$ ! Thus,  $S_{14} = 0$  as expected.

\* Again  $V_s$  sees the parallel combination of  $2Z_0 // 2Z_0$  and therefore  $Z_{in}^{(4)} = Z_0$ , i.e.  $V_4^+ = V_s$ ,  $V_4^- = 0$  and  $S_{44} = 0$ .

\*  $\left. \begin{matrix} V_2^- = V_s = V_4^+ \\ V_3^- = -V_s = -V_4^+ \end{matrix} \right\} \Rightarrow \begin{matrix} S_{24} = \frac{1}{\sqrt{2}} \\ S_{34} = -\frac{1}{\sqrt{2}} \end{matrix}$

Also,  $I_4 = 2I$  but  $I = \frac{V_s}{2Z_0} \Rightarrow$

$I_4 = \frac{2V_s}{2Z_0} = \frac{V_s}{Z_0} \Rightarrow Z_{in}^{(4)} = Z_0$  and  $S_{44} = 0$

$S_{44} = \frac{b_2}{a_4} = \frac{V_s / \sqrt{2}}{V_s / \sqrt{2}} = \frac{V_s}{V_s} \cdot \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}}$

Thus port ④ acts as the difference port, while port ① acts as the sum port.

For the remaining S-parameters we can use even and odd mode analysis for exciting ports ② and ③. However, we can just use the fact that our circuit is lossless:

$$|S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 + |S_{42}|^2 = 1$$

$$\text{But } |S_{12}|^2 = |S_{42}|^2 = \frac{1}{2} \Rightarrow S_{22} = S_{32} = 0$$

Similarly


$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 + |S_{43}|^2 = 1$$

$$\text{with } |S_{13}|^2 = |S_{43}|^2 = \frac{1}{2} \Rightarrow S_{23} = S_{33} = 0$$


The conclusion is that the indicated network behaves like a 3dB, 180° Hybrid coupler.

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & +1 \\ 1 & 0 & 0 & -1 \\ 0 & +1 & -1 & 0 \end{bmatrix}$$

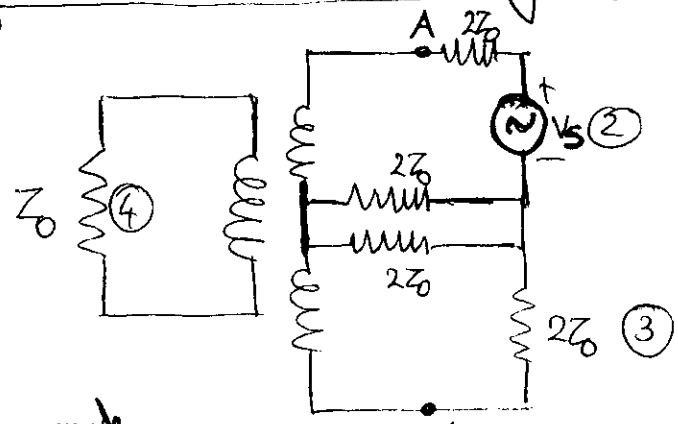
Using Even and Odd Analysis: (To determine  $S_{22}$  and  $S_{32}$ )



Even-mode

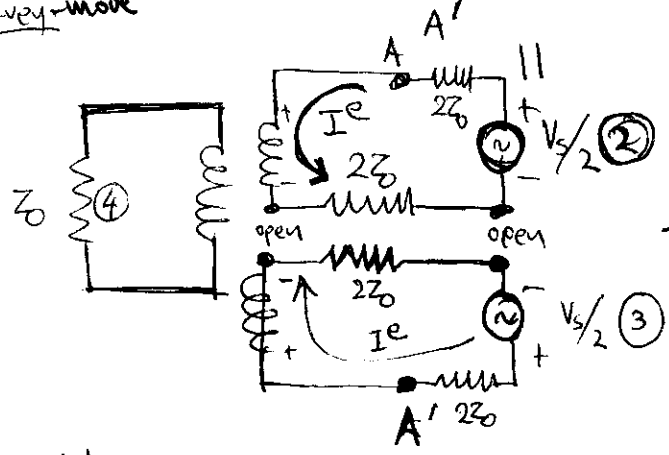

odd-mode

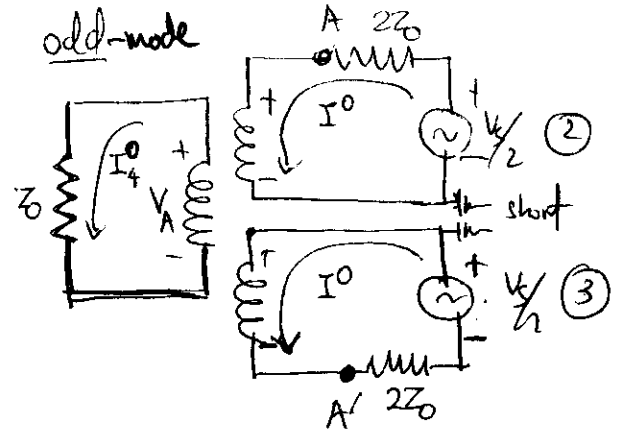

Even Excitation

- (a) Port 4 is not excited as voltages on trans. primaries are out-of-phase.
- (b)  $I^e = \frac{V_s/2}{2(2Z_0)} = \frac{V_s}{8Z_0}$ ,  $V_A^e = \frac{V_s/2}{2} = \frac{V_s}{4}$ , also  $V_A^e = \frac{V_s}{4}$
- (c) Note that  $Z_{inA}^e = 2Z_0 \Rightarrow \Gamma_e = 0$  (matched)

Odd Excitation

- (a)  $I_4^o = 2I^o$  and  $V_A = I_4^o Z_0 = 2I^o Z_0 \Rightarrow I^o = \frac{V_A^o}{2Z_0}$
- (b)  $Z_{inA}^o = \frac{V_A}{I^o} = 2Z_0 \Rightarrow \Gamma_o = 0$  (matched)
- (c) Since  $Z_{inA}^o = 2Z_0 \Rightarrow$  from the voltage divider at 2 and 3  
 $V_A^o = \frac{V_s}{4}$ ,  $V_{A'}^o = -\frac{V_s}{4} \Rightarrow I^o = \frac{V_s/4}{2Z_0} = \frac{V_s}{8Z_0}$

Finally: ①  $S_{22} = \frac{1}{2}(\Gamma_e + \Gamma_o) = 0$  or  $Z_{inA}^A = \frac{-V_A^e + V_{A'}^o}{I^e + I^o} = \frac{V_s/4 + V_s/4}{\frac{V_s}{8Z_0} + \frac{V_s}{8Z_0}} = \frac{V_s/2}{V_s/4Z_0} = 2Z_0$

$\Rightarrow S_{22} = \frac{Z_{inA}^A - 2Z_0}{Z_{inA}^A + 2Z_0} = 0 \Rightarrow \boxed{S_{22} = 0}$

②  $S_{32} = \frac{V_3^-}{V_2^+}$  But  $V_3^- = V_{A'}^e + V_{A'}^o = \frac{V_s}{4} - \frac{V_s}{4} = 0 \Rightarrow \boxed{S_{32} = 0}$