

Monolithic Inductors for Silicon Radio Frequency Integrated Circuits

Mina Danesh
M.A.Sc. Candidate

Supervisor: Prof. John R. Long

January 22, 1999





Outline

- **Introduction**
- **Microstrip lines on silicon**
- **Spiral inductor modeling**
- **Differential excitation**
- **Symmetric spiral inductors**
- **Application: oscillator design**
- **Conclusion**



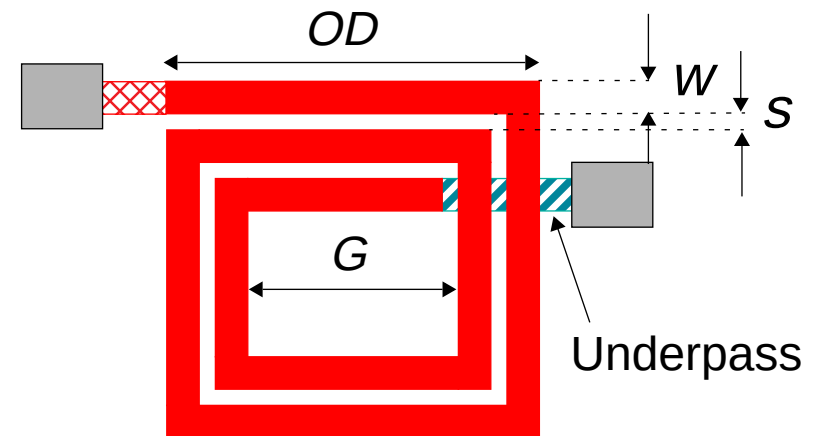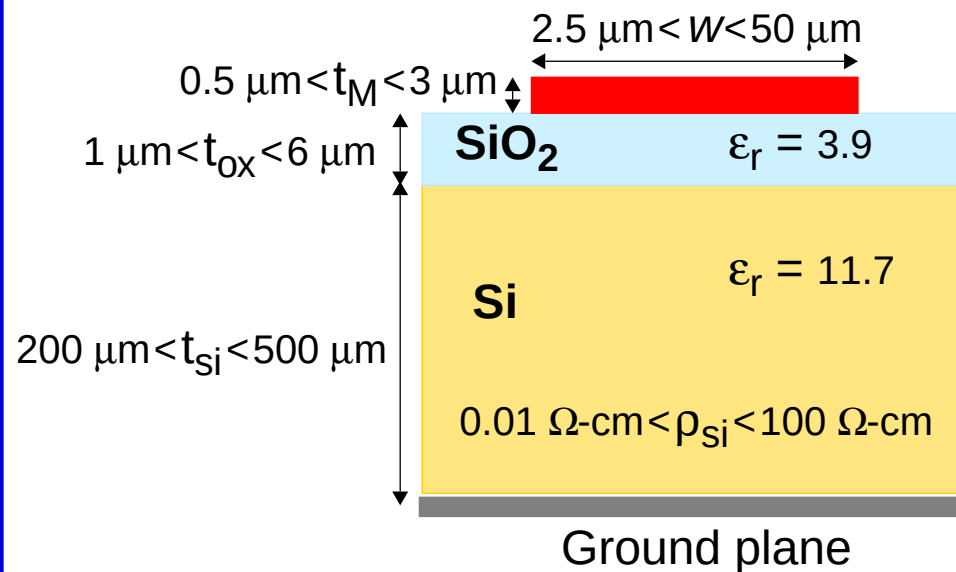Monolithic Inductors for Si RF Applications





Rectangular spiral inductor



LOW Q -factor
 $Q_{\text{typical}} < 10$



Propagation Modes

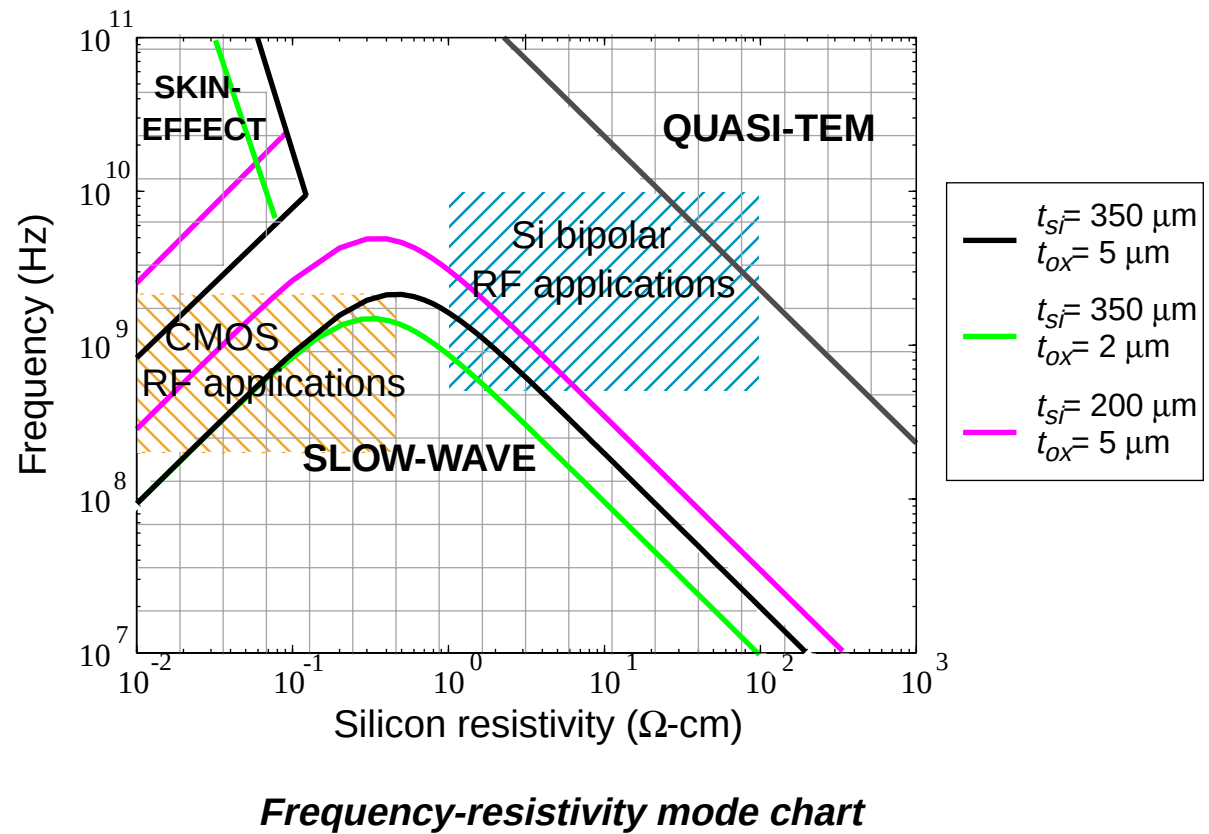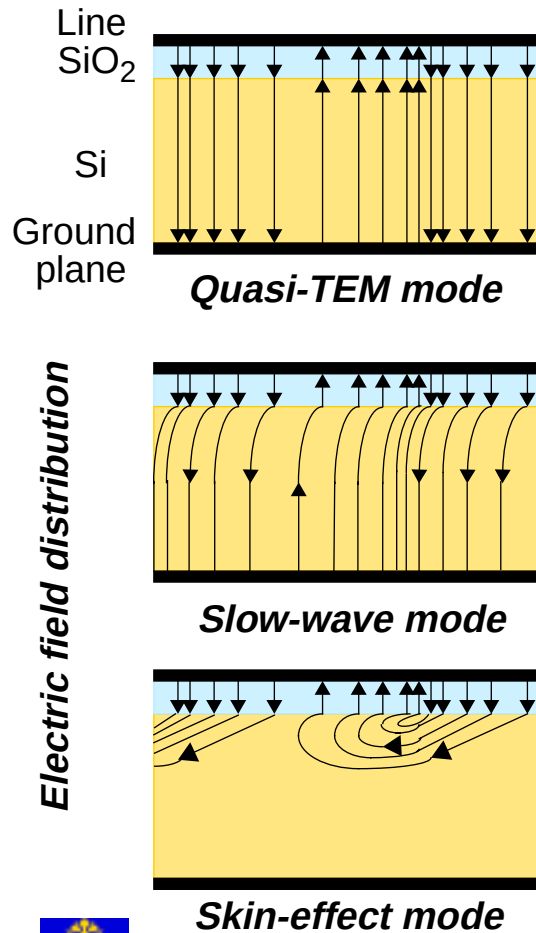

Microstrip Line Modeling



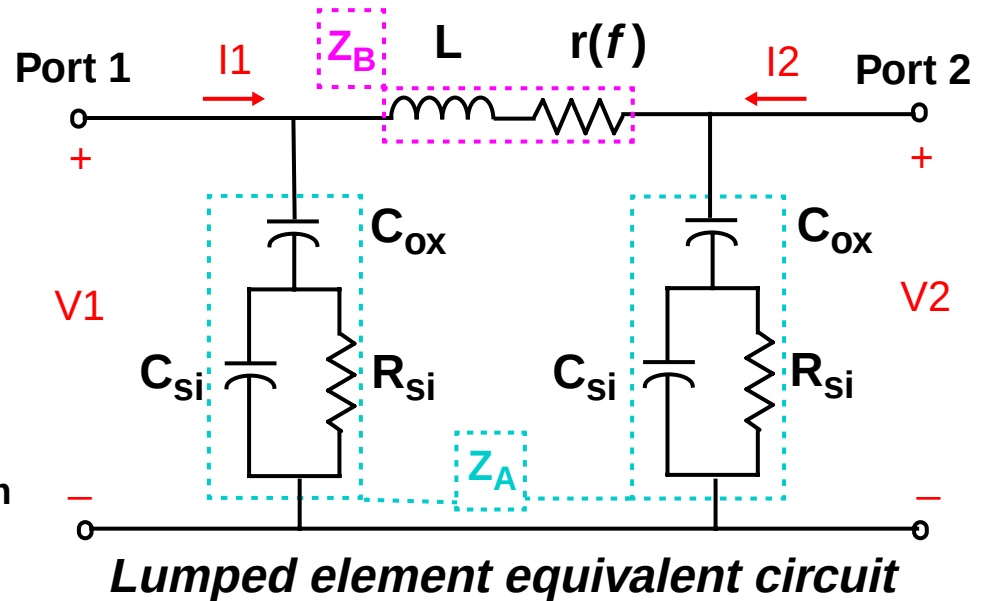
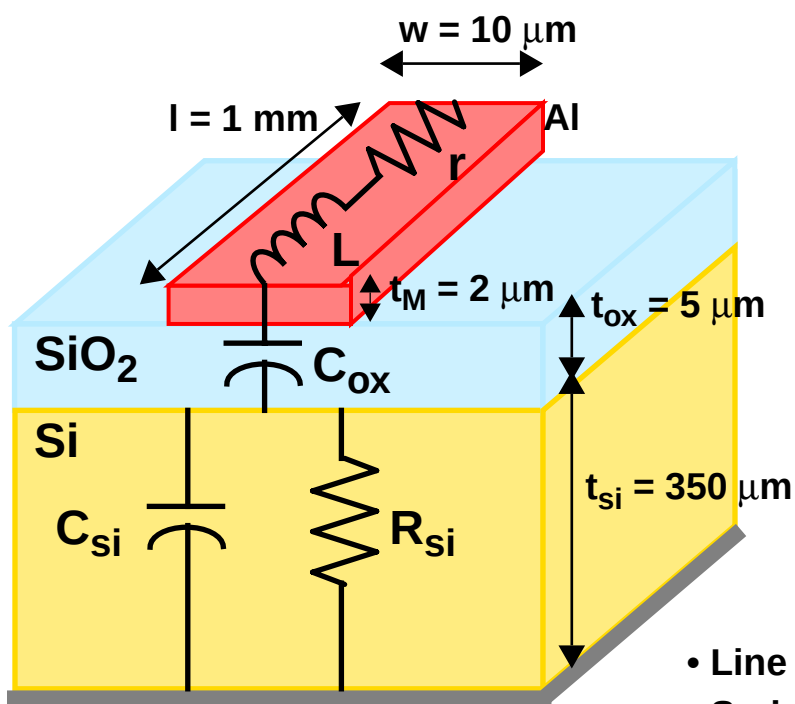


- Line inductance
- Series resistance: skin-effect, conduction current in Si
- C_{ox} } line-to-ground capacitance, extracted separately with
- C_{si} } 2D numerical method for oxide and silicon layers





• R_{si} :
$$R_{si} = \frac{\epsilon_{si} \cdot \rho_{si}}{C_{si}} (\Omega)$$



Microstrip Line Modeling

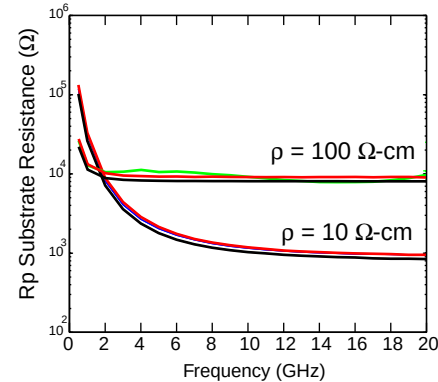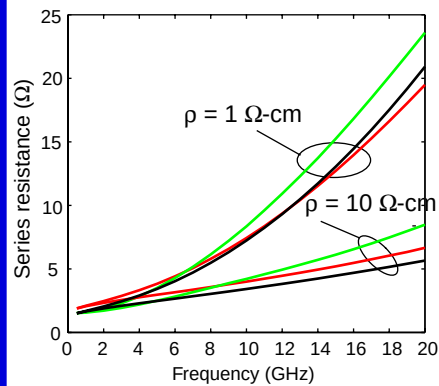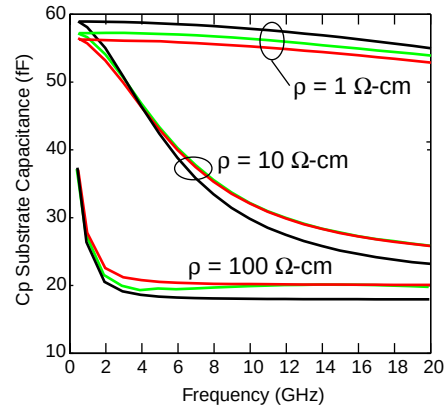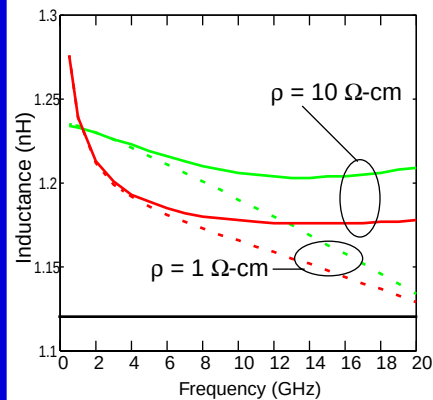

Transmission line distributed parameters

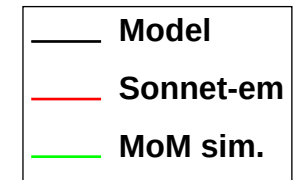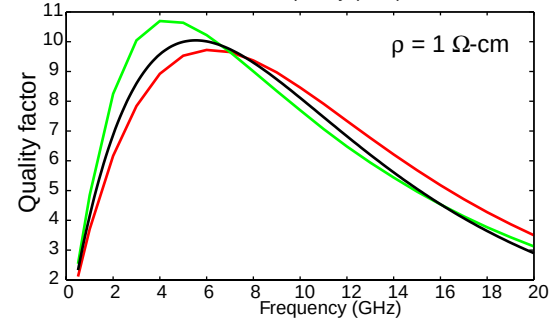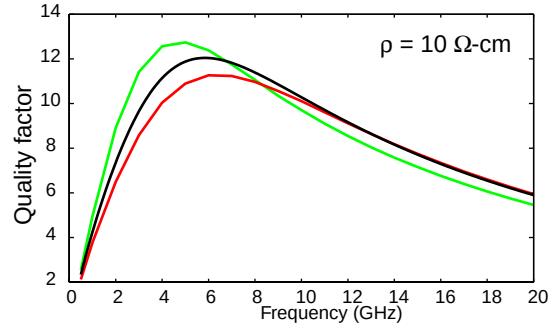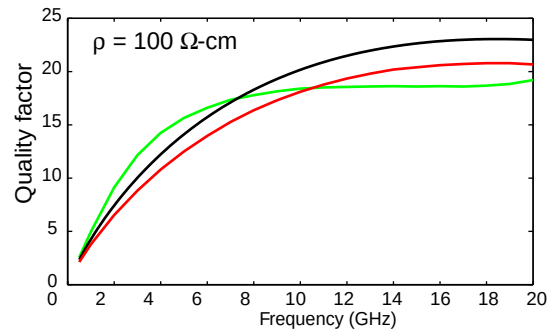


Quality-factor

$$Q = \frac{1}{\text{Re}[Y_{in}] \cdot \omega L_p}$$

**below the first
self-resonant
frequency**




Spiral Inductor Modeling

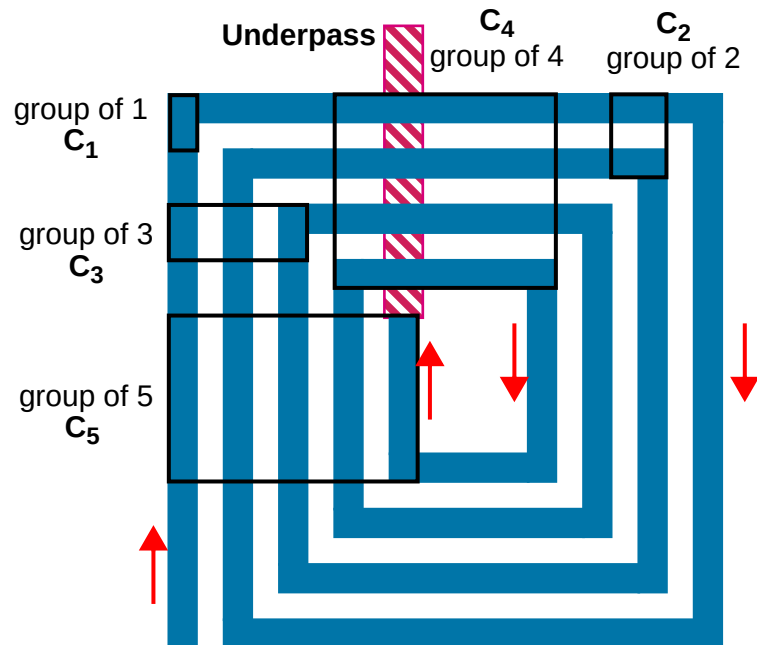

- Substrate capacitance

$$\frac{C_{ox}}{C_{si}} \propto (C_5, C_4, C_3, C_2, C_1; w+s)$$

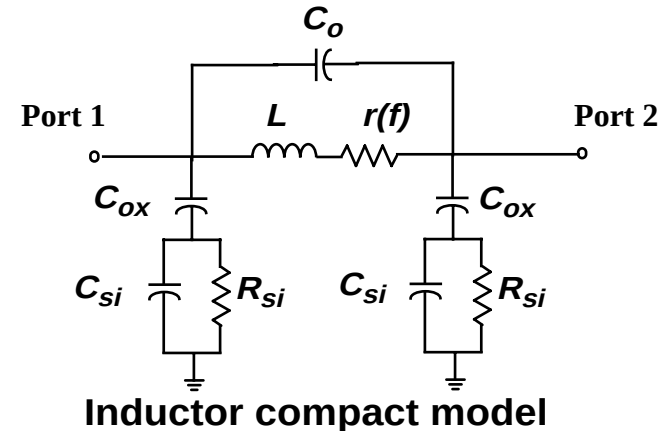- C_o Line-to-line interwinding capacitance
Underpass parallel-plate capacitance



- Inductance:
Summation of self- and mutual inductances
- Series resistance

$$r(f) \begin{cases} \text{- Metallization} \propto f^{1/2} \\ \text{- Conductive Si} \propto f^2 \end{cases}$$

- Silicon substrate resistance

$$R_{si} = \frac{2 \cdot \epsilon_{si} \cdot \rho_{si}}{C_{si}} (\Omega)$$








Spiral Inductor Modeling



4.5 turns, $OD = 241 \mu\text{m}$, $w = 10 \mu\text{m}$, $s = 5 \mu\text{m}$ square spiral inductor

Table 1: Inductor Model Lumped elements




L (nH)	R_{dc} (Ω)	C_{ox} (fF)	C_{si} (fF)	R_{si} (Ω)	C_o (fF)
5.3	8.7	178	45	229	15

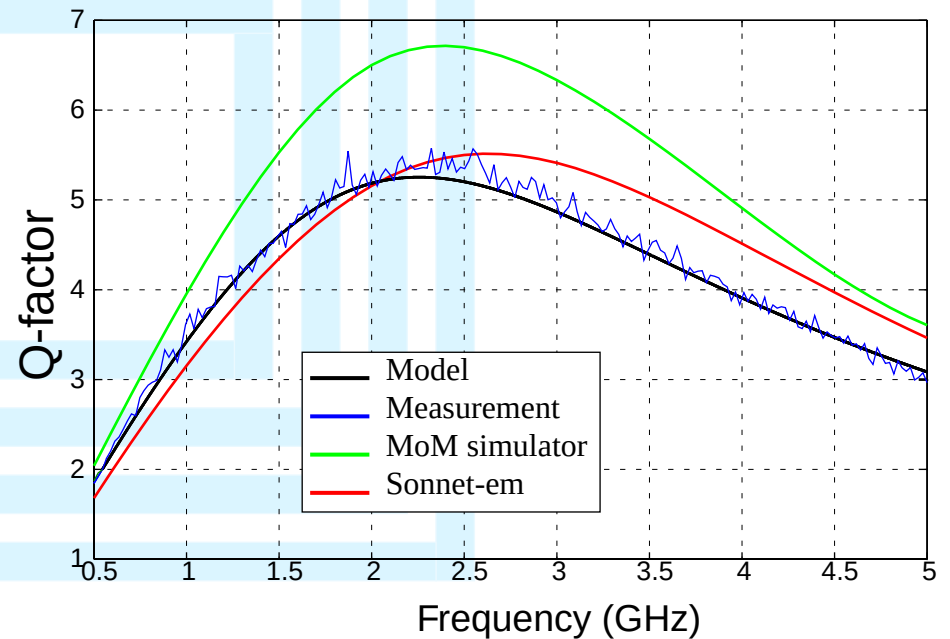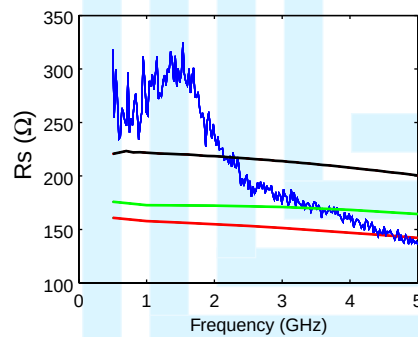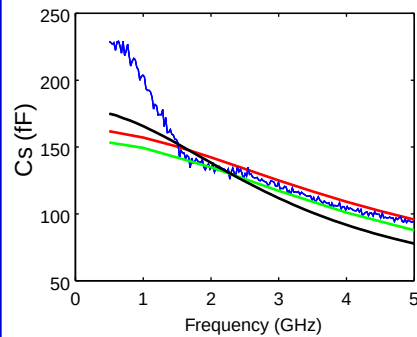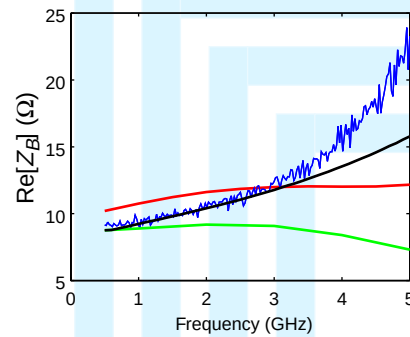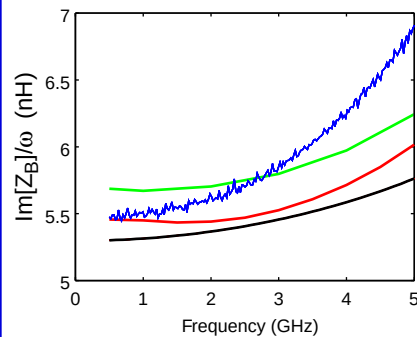


Inductor Realizations in Si

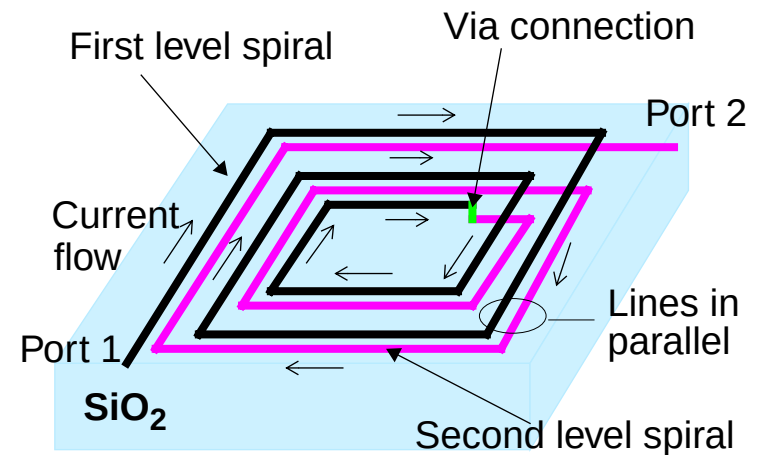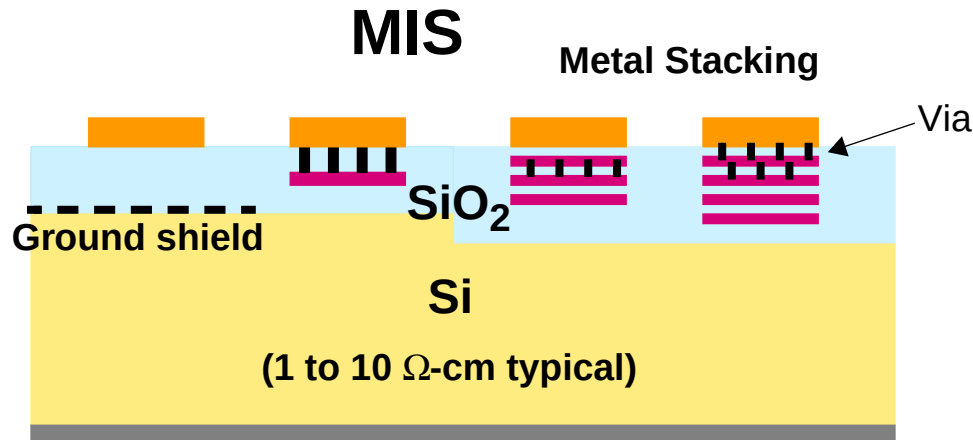

Alternate structures

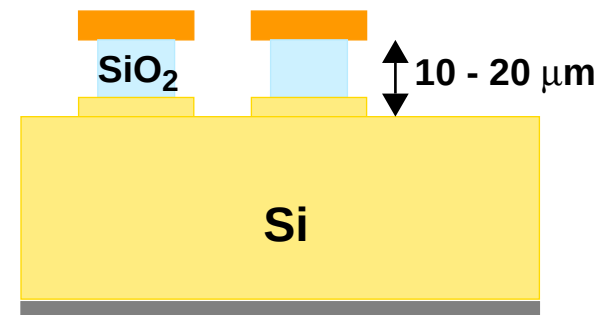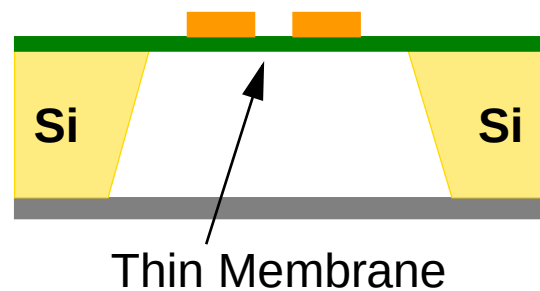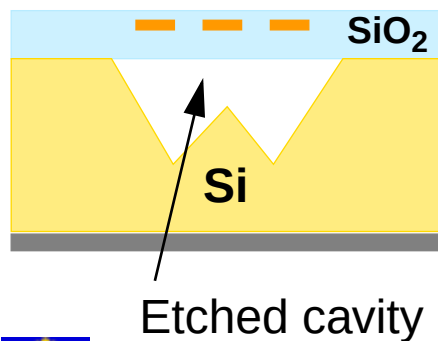

Single-ended / Differential Excitation

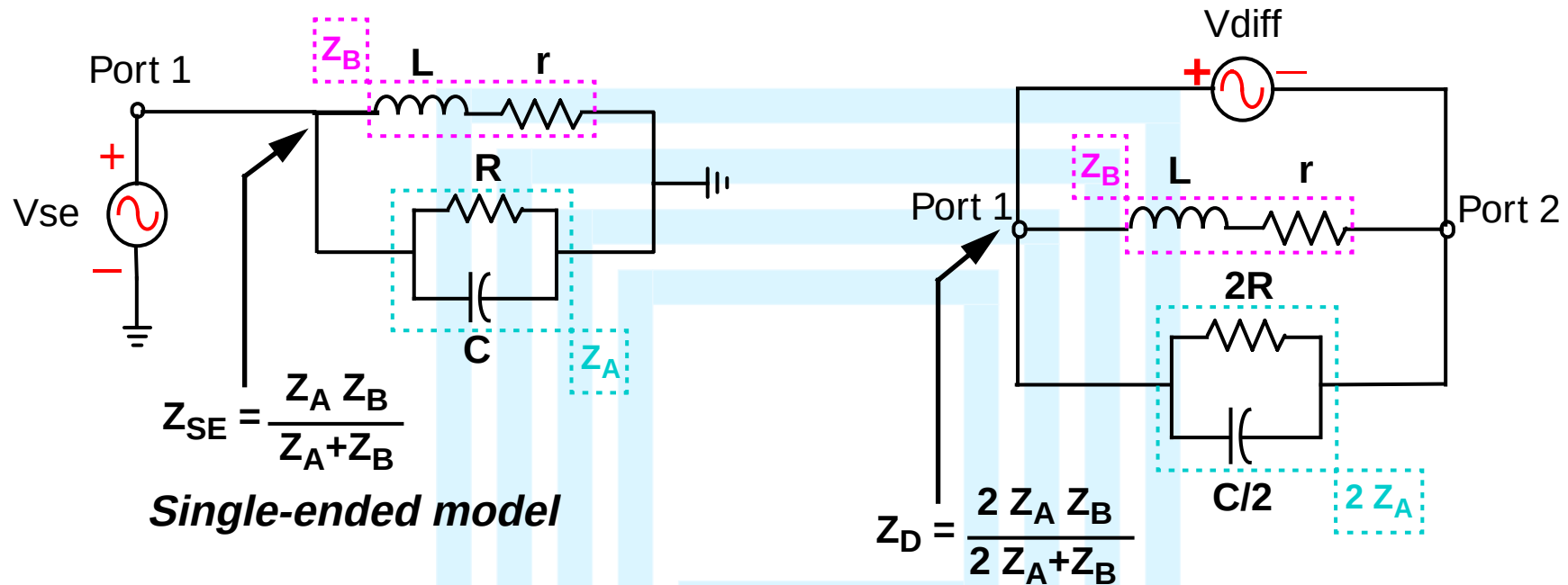

- Low frequencies (<1 GHz)

$$Z_{differential} \approx Z_{single-ended}$$


- Higher frequencies: increasing influence of substrate parasitics

$$\text{Re}[Z_{differential}] < \text{Re}[Z_{single-ended}]$$

Differential excitation: Higher Q and broader bandwidth





Asymmetrical vs. Symmetrical

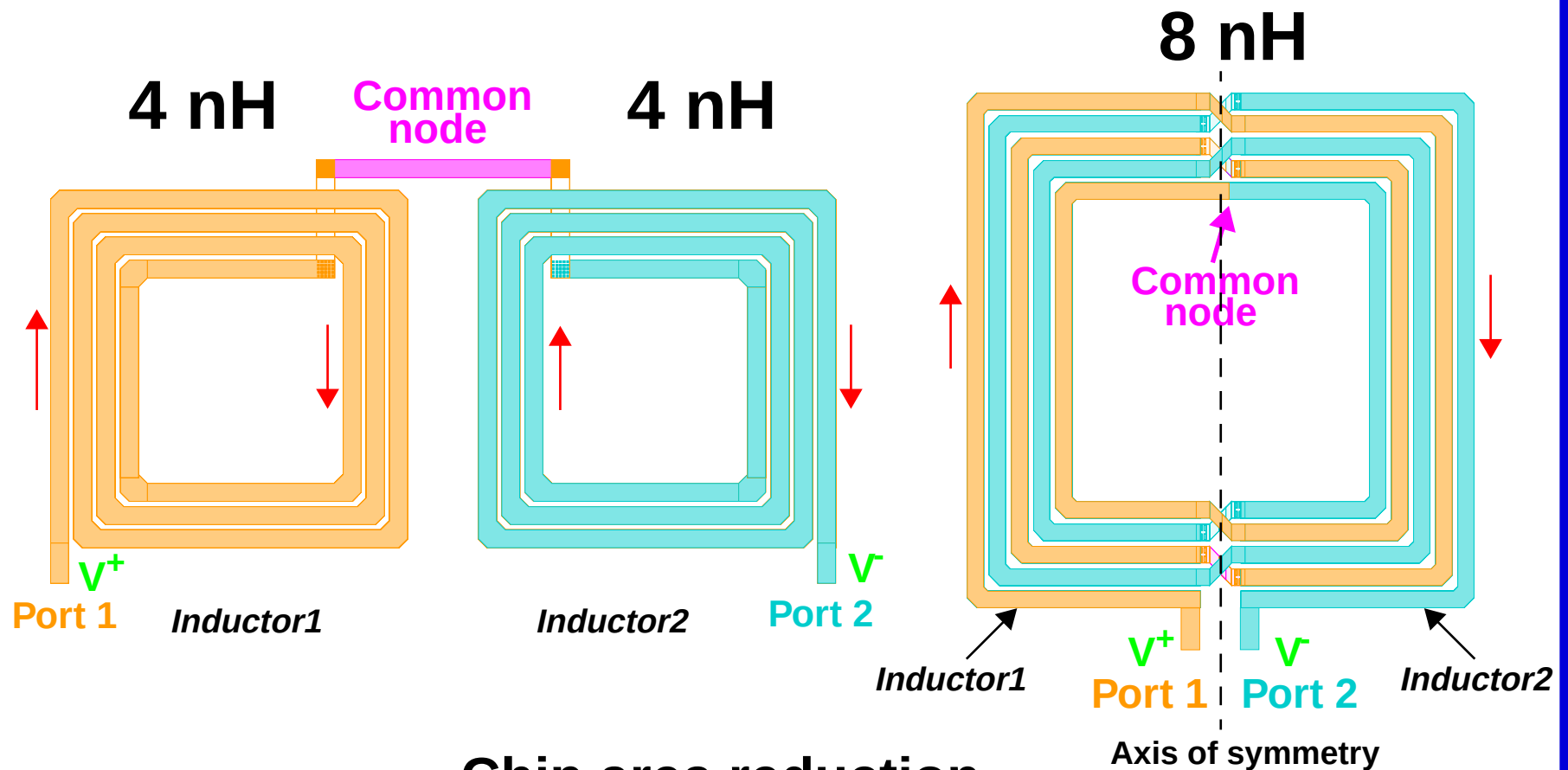

Chip area reduction



Symmetrical Spiral Inductor

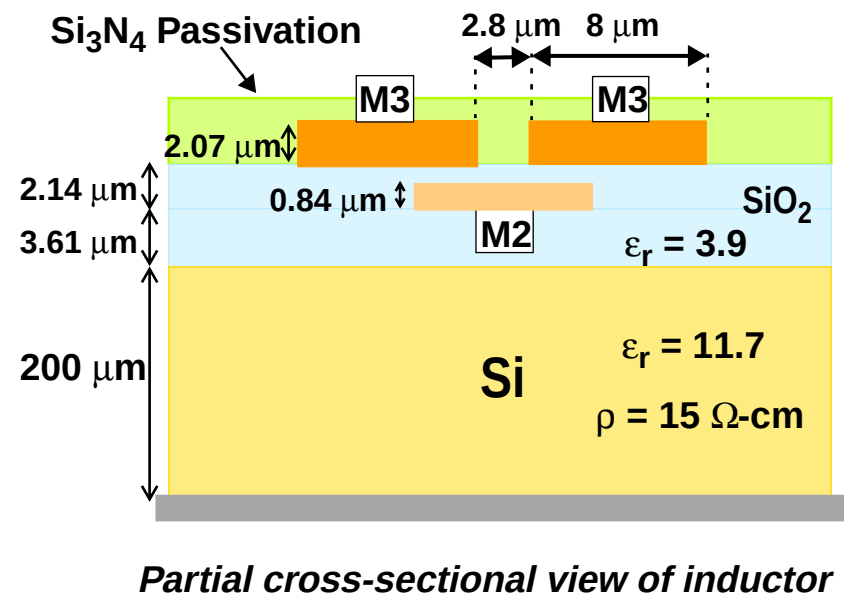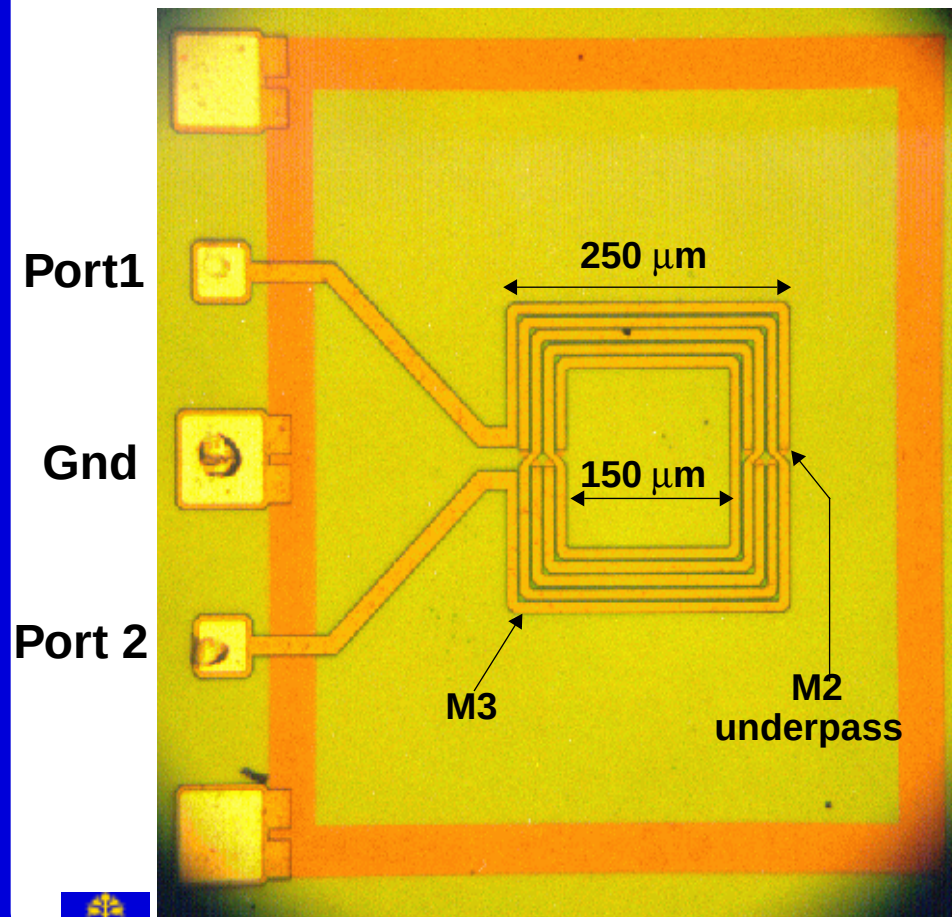

Model / Simulation / Measurement

- Symmetric inductor modeling

Table 2: Symmetric Inductor Lumped Elements

L (nH)	R_{dc} (Ω)	C_{ox} (fF)	C_{si} (fF)	R_{si} (Ω)	C_o (fF)
8	7.5	146	52.7	590	52

- Full-wave EM simulation

- Measurement

2-port calibration:

- Probes on opposing sides for thru calibration
- Probes moved to same side for measurement

De-embedding: Open / Short

- Differential:



$$S_d = \frac{S_{11} + S_{22} - S_{12} - S_{21}}{2}$$

- Input impedance:


$$Z_d = 2Z_o \left(\frac{1 + S_d}{1 - S_d} \right) \quad (Z_o = 50 \Omega)$$



Input Impedance

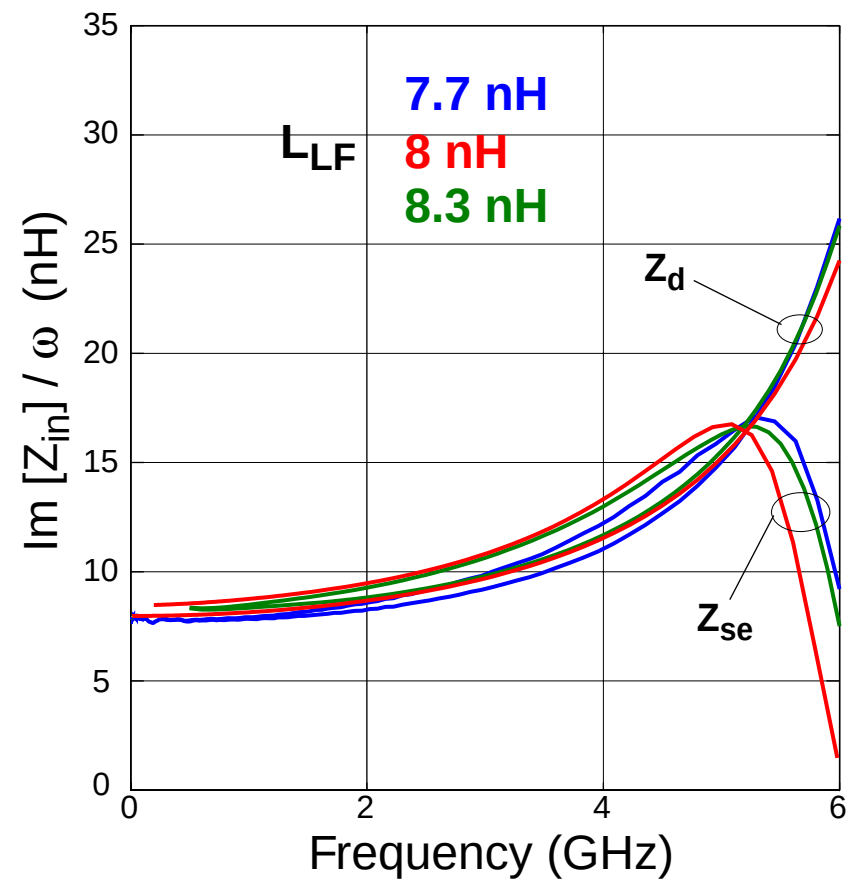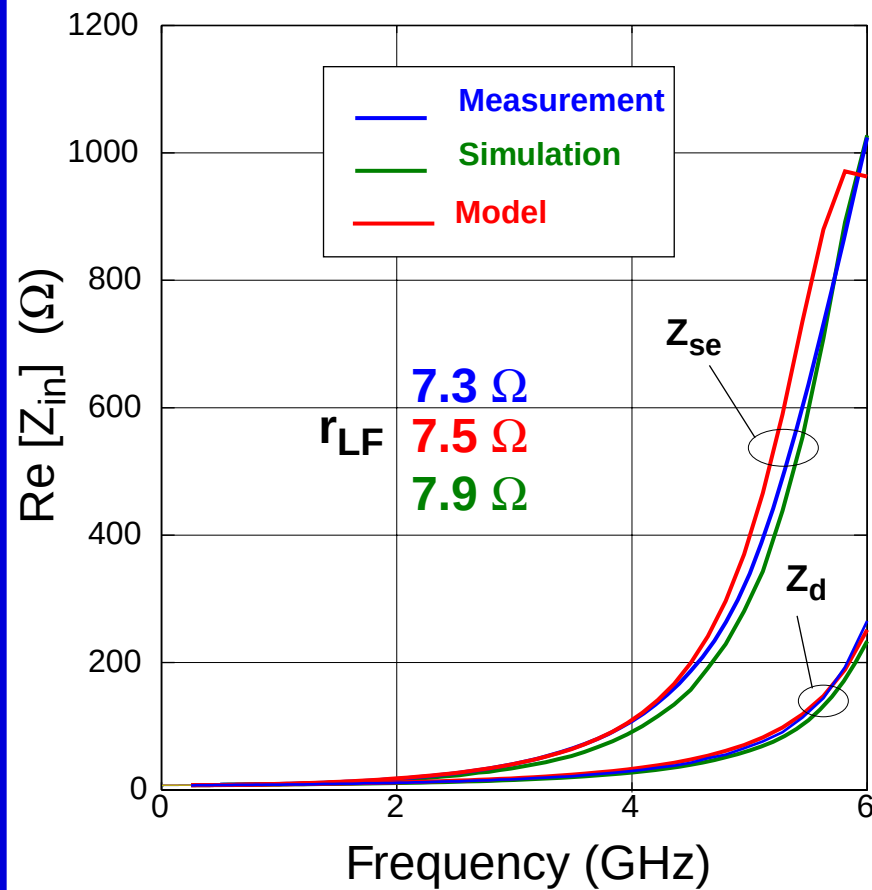

Quality Factor

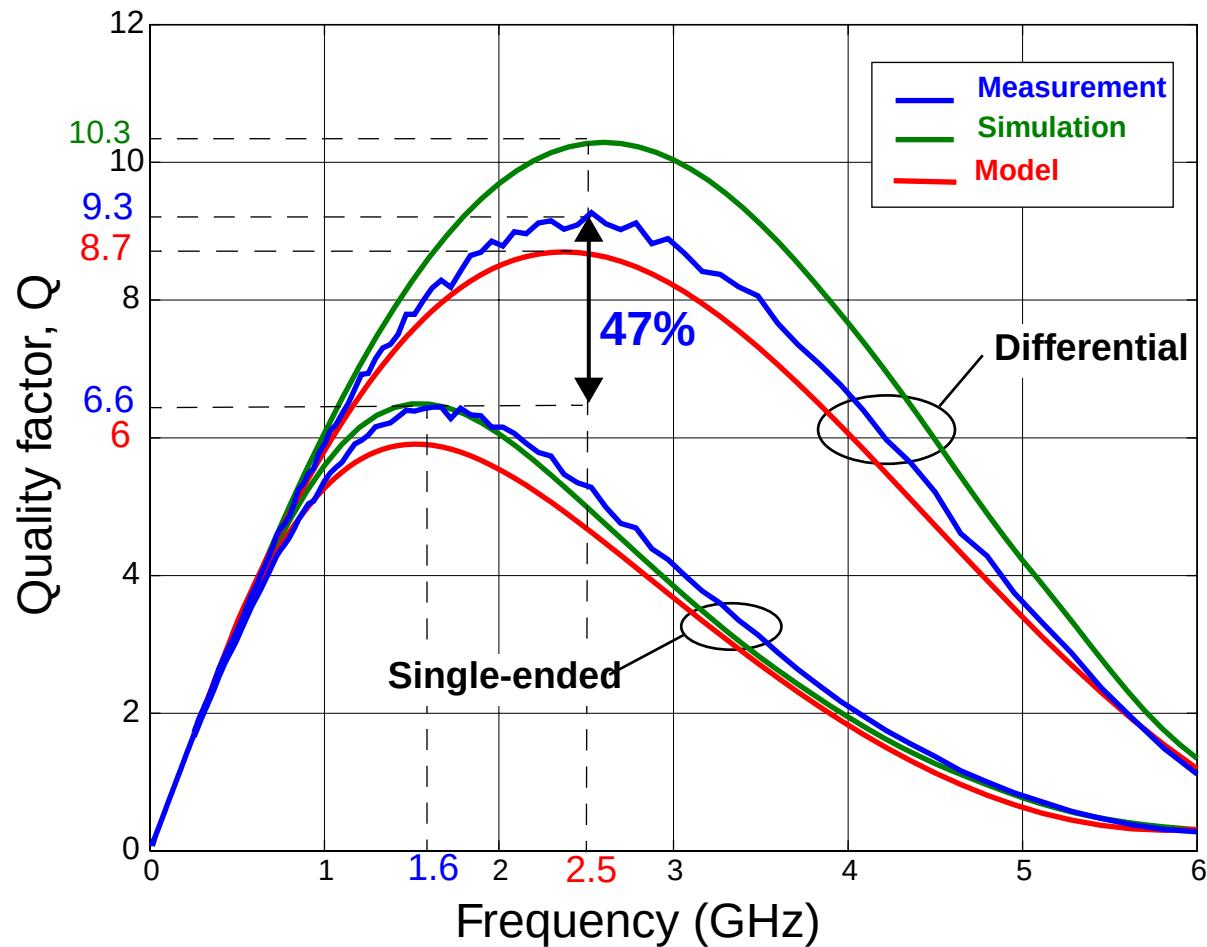

Literature Comparison

<i>Inductor type</i>	<i>Reference</i>	<i>Si ρ</i>	<i>t_M (μm)</i>	<i>L (nH)</i>	<i>Q-factor</i>
1-level metal	Long	10 Ω -cm	1-3	1.88	6-10 @ 4 GHz
2-level metal	Park	2 k Ω -cm	2	13	12 @ 3 GHz
5-level metal	Burghartz	12 Ω -cm	4.3	2.2	16 @ 2 GHz
Ground shield	Yue	10-20 Ω -cm	2	8	7.2 @ 1.5 GHz
Membrane	Chi	2 k Ω -cm	1 (Au)	0.9	20 @ 4.3 GHz
Etched oxide/Si	Rieh	10 k Ω -cm		1.2	Res. freq: 70 GHz
				2	Res. freq: 30 GHz
Differential	Danesh	15 Ω -cm	2	8	9.3 @ 2.5 GHz
Single-ended	Long				6.6 @ 1.6 GHz




Application: Differential Oscillator

Table 3: Comparison between inductors.



Characteristics	8 nH symmetric	4 nH asymmetric
OD / N	250 μm / 5	210 μm / 3.5
Inner gap	150 μm	140 μm
Total length	4 mm	2.44 mm
R_{dc}	7.5 Ω	4.56 Ω
Q @ 2.1 GHz	8.6	7.5

Table 4: Comparison of overall performance.

Parameters	8 nH symmetric	4 nH asymmetric
f_{osc} (GHz)	2.061	2.114
V_{out} swing (V)	2.8	1.6
PN (dBc/Hz) @ 1 MHz	-120.9	-118.9
P_{out} (dBm)	7.1	5.4
3 rd harmonic P_{out} (dBm)	-30.9	-29.1

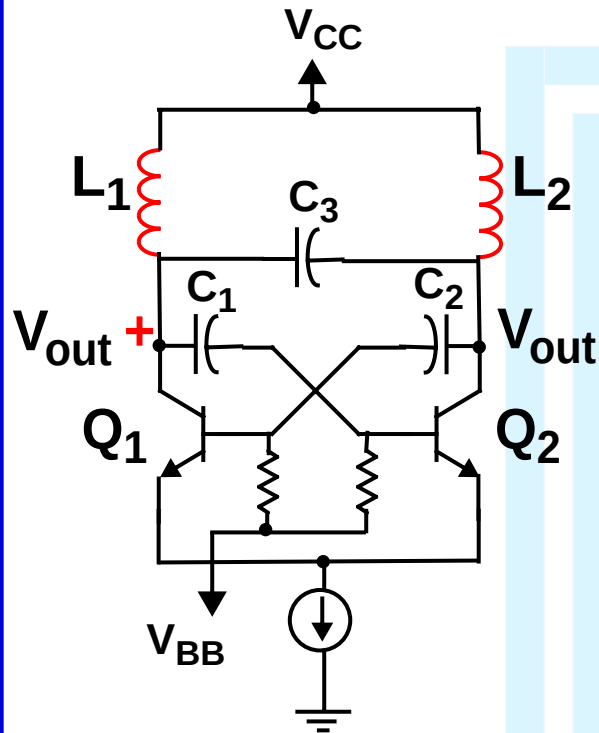

Cross-coupled Oscillator

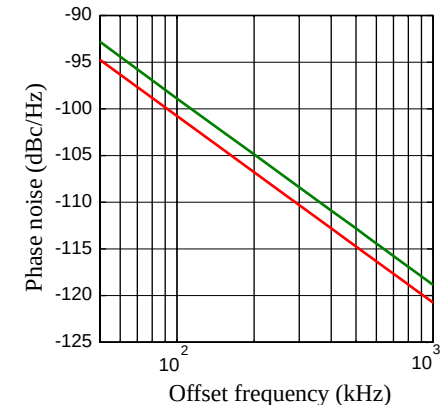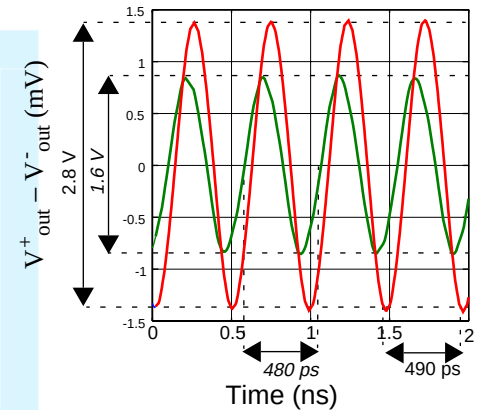

Conclusion

- Propagation modes for silicon substrates
- Microstrip line and spiral **inductor modeling**
- **Differential** vs single-ended excitation: lower parasitics
 - Higher peak Q-factor** (50% +)
 - Higher peak frequency** (50% +)
 - Broader operating bandwidth**
- RF applications
 - Symmetric inductors** (**reduced chip area**)
 - Oscillators, amplifiers, mixers ...
- Other substrates: GaAs

