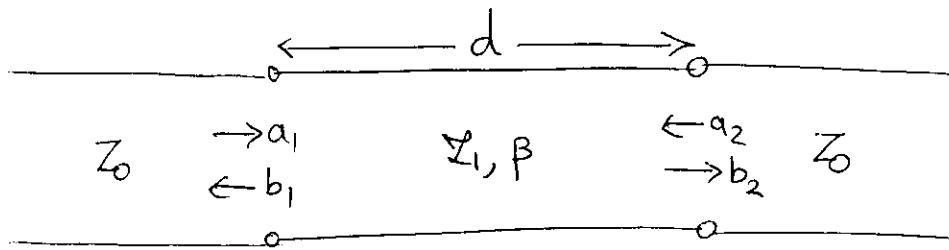


Problem ①


$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$$

- The circuit is symmetric  $\Rightarrow S_{11} = S_{22}$ , reciprocal  $\Rightarrow S_{12} = S_{21}$  and lossless  $\Rightarrow SS^* = U$ .

$$S = \begin{bmatrix} S_{11} & S_{12} \\ S_{12} & S_{11} \end{bmatrix}$$

Computing  $S_{11}$  (and  $S_{22}$ ) :

$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$ , i.e.  $S_{11}$  is equivalent to the reflection coefficient in the circuit:

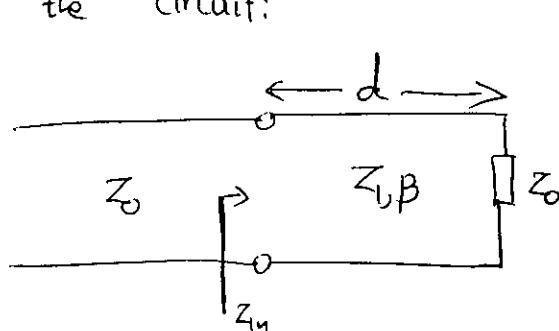


i.e.  $S_{11} = \Gamma_m = \frac{Z_m - Z_0}{Z_m + Z_0}$  where  $Z_m = Z_0 \frac{Z_0 + j Z_1 \tan \theta}{Z_1 + j Z_0 \tan \theta}$ ,  $\boxed{\theta = \beta d}$

$$S_{11} = \frac{j (Z_1^2 - Z_0^2) \tan \theta}{2Z_1 Z_0 + j (Z_1^2 + Z_0^2) \tan \theta} = \boxed{\frac{j (Z_1^2 - Z_0^2) \sin \theta}{2Z_0 Z_1 \cos \theta + j (Z_0^2 + Z_1^2) \sin \theta}} = S_{11}$$

### Computing $S_{21}$ (and $S_{12}$ ):

One way to proceed is to exploit the fact that the circuit is lossless and we  $SS^* = U$ . However, we choose the definition for illustration purposes:

$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$ . Therefore, we have to compute the transmission coefficient in the following circuit:

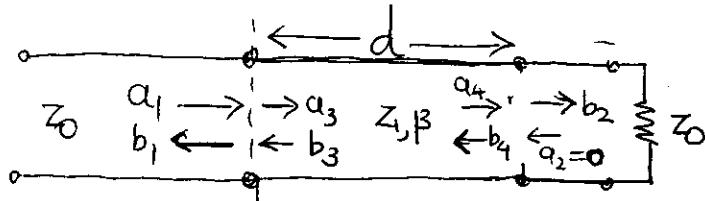

$$\text{We can write: } V_1 = \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_1} (a_3 + b_3) \quad (1)$$

$$V_4 = \sqrt{Z_0} b_2 = \sqrt{Z_1} (a_4 + b_4) \quad (2)$$

$$a_4 = a_3 e^{-j\theta} \quad (3)$$

$$b_3 = b_4 e^{-j\theta} \quad (4)$$

$$\frac{b_4}{a_4} = \Gamma_L = \frac{Z_L - Z_1}{Z_0 + Z_1} \quad (5)$$

$$b_1 = S_{11} a_1 \quad (6)$$

$$\text{From (1) and (6): } V_1 = \sqrt{Z_0} a_1 (1 + S_{11}) = \sqrt{Z_1} (a_3 + b_3) \quad (7)$$

$$\text{From (2) and (5): } \sqrt{Z_1} a_4 (1 + \Gamma_L) = \sqrt{Z_0} b_2 \quad (8)$$

$$\text{From (7) and (3), (4): } \sqrt{Z_0} a_1 (1 + S_{11}) = \sqrt{Z_1} (a_4 e^{j\theta} + b_4 e^{-j\theta})$$

$$\stackrel{(5)}{=} \sqrt{Z_1} a_4 (e^{j\theta} + \Gamma_L e^{-j\theta}) \dots \quad (9)$$

$$\text{From (9) and (8): } \sqrt{Z_0} a_1 (1 + S_{11}) = \sqrt{Z_1} (e^{j\theta} + \Gamma_L e^{-j\theta}) \frac{\sqrt{Z_0} b_2}{\sqrt{Z_1} (1 + \Gamma_L)}$$

Therefore,  $a_1 \in (1+s_{11})(1+r_L) = b_2 (e^{j\theta} + r_L e^{-j\theta})$

$$\Rightarrow S_{21} = \frac{b_2}{a_1} = \frac{(1+s_{11})(1+r_L)}{(e^{j\theta} + r_L e^{-j\theta})}$$

But

$$1+s_{11} = \frac{2z_0 z_1 \cos\theta + 2j z_1^2 \sin\theta}{2z_0 z_1 \cos\theta + j(z_0^2 + z_1^2) \sin\theta}$$


from which

$$S_{21} = \boxed{\frac{2z_0 z_1}{2z_0 z_1 \cos\theta + j(z_0^2 + z_1^2) \sin\theta}}$$

3'

Second - solution

ABCD for a Line:

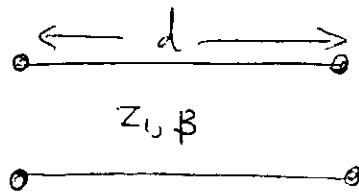

$$\begin{bmatrix} \cos \beta d & jz_1 \sin \beta d \\ j\frac{\sin \beta d}{z_1} & \cos \beta d \end{bmatrix} \quad \theta = \beta d$$

Convert to [S]:

$$S_{22} = S_{11} = \frac{A + \frac{B/z_0 - Cz_0}{D}}{A + \frac{B/z_0 + Cz_0 + D}{D}} = \frac{\cos \beta d + j\frac{z_1}{z_0} \sin \beta d - j\frac{z_0}{z_1} \sin \beta d - \cancel{Cz_0 \beta d}}{\cos \beta d + j\frac{z_1}{z_0} \sin \beta d + j\frac{z_0}{z_1} \sin \beta d + \cancel{Cz_0 \beta d}}$$

$$= \frac{j(z_1^2 - z_0^2) \sin \theta}{2z_0 z_1 \cos \theta + j(z_0^2 + z_1^2) \sin \theta}$$

$$S_{12} = S_{21} = \frac{2}{A + \frac{B/z_0 + Cz_0 + D}{D}} = \frac{2}{2\cos \beta d + j(\frac{z_1}{z_0} + \frac{z_0}{z_1}) \sin \beta d} = \frac{2z_0 z_1}{2z_0 \cos \theta + j(z_0^2 + z_1^2) \sin \theta}$$

## Problem 2 :

-4-

ECE424F HWK#5

Design a reciprocal, lossless Two-port with scattering matrix:

$$(1) \quad S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \text{ where } S_{11} = S_{22} = 0.2 / 108^\circ \text{ and} \\ S_{12} = S_{21} \text{ at } f = 1 \text{ GHz}$$

Since the two-port is lossless  $\tilde{S}\tilde{S}^T = \tilde{I}$  and once  $S_{11}$  is defined so is  $S_{12}$ . In our case  $\tilde{S}\tilde{S}^T = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} S_{11}^T & S_{21}^T \\ S_{12}^T & S_{22}^T \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \Rightarrow$

$$|S_{11}|^2 + |S_{12}|^2 = 1 \text{ and} \quad \dots \quad (1)$$

$$S_{11}S_{12}^T + S_{12}S_{11}^T = 0 \quad \dots \quad (2)$$

$$\text{From (1)} \quad S_{12} = \sqrt{1 - |S_{11}|^2} = \sqrt{1 - (0.2)^2} = 0.98$$



$$\text{From (2)} \quad |S_{11}| |S_{12}| e^{j(\phi_{11} - \phi_{12})} = - |S_{11}| |S_{12}| e^{j(\phi_{12} - \phi_{11})} \Rightarrow$$

$$\phi_{11} - \phi_{12} = \phi_{12} - \phi_{11} - \pi \Rightarrow \boxed{\phi_{12} = \frac{2\phi_{11} + \pi}{2}} \quad \dots \quad (3)$$

$$\text{I.C } \phi_{12} = \frac{2(108) + 180}{2} = 138^\circ (-162^\circ)$$


$$\text{Therefore } \boxed{S_{12} = 0.98 / -162^\circ} \quad \dots \quad (4)$$

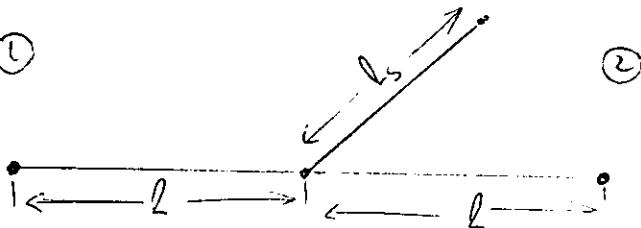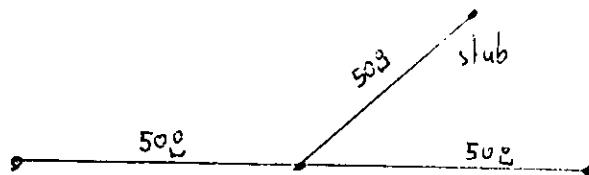- (a) The desired [S] is symmetrical ( $S_{11} = S_{22}$ ), reciprocal and lossless.  
A possible configuration would be:



The stub provides the magnitude of  $S_{11}$  and the line its phase.


(b) From the definition of the scattering matrix we get  $S_{11} = \frac{b_1}{a_1} |_{a_2=0}$ . if we are to connect the two-port to  $50\Omega$  lines then  $a_2=0$  when the output port is terminated to  $50\Omega$  load:

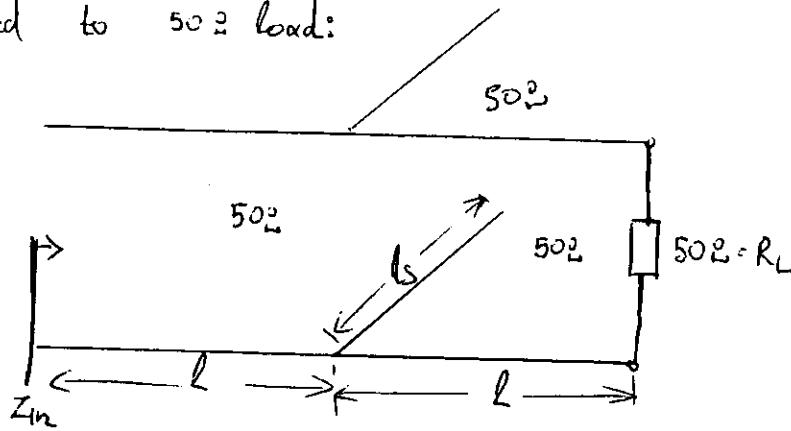

$$\text{Then } S_{11} = \Gamma_{in} = \frac{Z_{in} - 50}{Z_{in} + 50} \quad \dots \quad \dots \quad \dots \quad (5)$$

i.e  $S_{11}$  is the reflection coefficient of the above terminated two-port if considered as a one port.

To find  $Z_{in}$ :

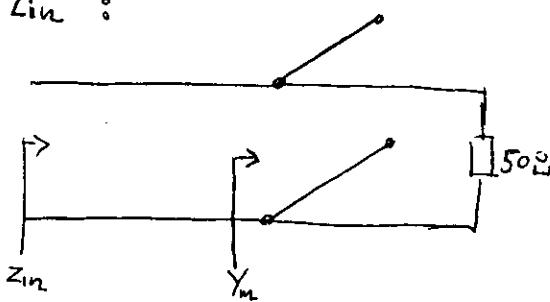

$$0.2e^{j10^\circ} = \frac{Z_{in} - 50}{Z_{in} + 50} \Rightarrow Z_{in} = 50 \frac{S_{11} + 1}{1 - S_{11}} = \frac{50(1 + 0.2e^{j10^\circ})}{(1 - 0.2e^{j10^\circ})} = 41.25 + 16.35j$$

Now we know that  $\bar{Y}_m = \bar{Y}_{\text{stub}} + 1; = j\bar{\beta} + 1$ . Therefore  $\text{Re}[\bar{Y}_m] = 1$ .

Therefore, starting from  $\bar{Z}_{in}$  on the Smith chart and moving towards the load on the constant SWR circle we should reach the point  $\bar{Y}_m$  with  $\text{Re}[\bar{Y}_m] = 1$ . The constant SWR circle intersects the  $\text{Re}[Y] = 1$  circle at two points. One of them is very close to  $\bar{Y}_{in}$  leading to a very short  $l$  to be practically designed.

ie the sensitivity of  $[S]$  with small <sup>-G-</sup> percentile variations of the length  $L$  will be very large. (For example :  $\frac{|AS_{11}|/|S_{11}|}{|\Delta L|/L}$ , Large)

The second point of intersection is at  $\bar{Y}_m = 1 + 0.41j$  which corresponds to a length  $L = (0.36 - 0.153) \lambda = 0.207 \lambda$


Now  $\bar{Y}_m = 1 + j\bar{B}$  therefore  $\bar{B} = 0.41$  ie we need a capacitive (open-circuited) stub with  $\bar{B} = 0.41$ . Starting from the point  $\bar{y} = 0$  on the outermost circle of the Smith chart and moving towards the generator until  $\bar{y} = 0.41j$  we find that  $Q_s = (0.061 - 0.000) \lambda = 0.061 \lambda$

Therefore the designed characteristics of our Two-port are the following:


1. All lines with  $Z_0 = 50 \Omega$
2.  $L = 0.207 \lambda$
3.  $Q_s = 0.061 \lambda$

Problem 4.8 :

Use the equivalent model for a 2-port:

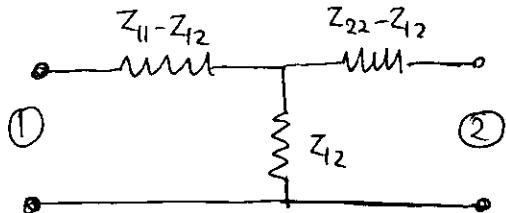

Then shorting port ②:

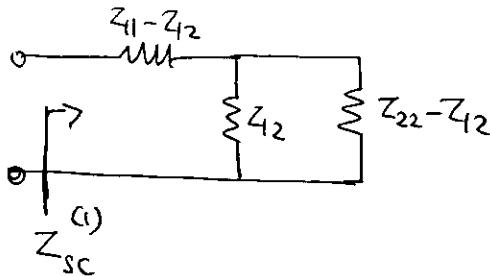


$$Z_{sc}^{(1)} = Z_{11} - Z_{12} + \frac{Z_{12}(Z_{22} - Z_{12})}{Z_{22}} = Z_{11} - \frac{Z_{12}^2}{Z_{22}} \quad \dots \quad (1)$$

Similarly

$$Z_{sc}^{(2)} = Z_{22} - \frac{Z_{12}^2}{Z_{11}}$$

For an open circuited port ②:

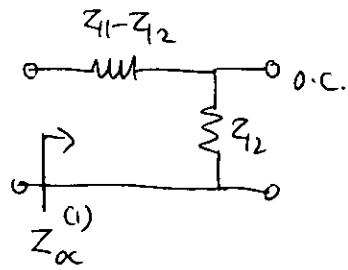

$$Z_{oc}^{(1)} = Z_{11}, \text{ similarly } Z_{oc}^{(2)} = Z_{22}$$

$$\text{Hence } Z_{12}^2 = -(Z_{sc}^{(1)} - Z_{11})Z_{22} = (Z_{oc}^{(1)} - Z_{sc}^{(1)})Z_{oc}^{(2)} \quad (\text{from (1)}).$$

I.E: By measuring  $Z_{oc}^{(1)}$ ,  $Z_{oc}^{(2)}$  and  $Z_{sc}^{(1)}$  we can identify the equivalent 2-port circuit and corresponding impedance-matrix.

(4.16)

a) To be lossless,  $[S]$  must be unitary :

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = (.1)^2 + (.6)^2 + (.6)^2 = 0.73 \neq 1$$

Thus the network is not lossless

b) To be reciprocal,  $[S]$  must be symmetric :

Since  $S_{13} \neq S_{31}$ , the network is not reciprocal.

c) When all other ports are matched,  $\Gamma = S_{11}$

Thus,  $RL = -20 \log |\Gamma| = -20 \log (.1) = \underline{20 \text{ dB}}$  at port 1. ✓

d) When all other ports are matched, the insertion loss from port 2 to port 4 is,

$$IL = -20 \log |S_{42}| = -20 \log (.6) = \underline{4.4 \text{ dB}}. \text{ Phase delay} = \underline{45^\circ} \checkmark$$

e) For a short circuit at port 3, and matched loads at other ports, we have,

$$V_2^+ = V_4^+ = 0, \quad V_3^+ = -V_3^-$$

$$V_1^- = S_{11}V_1^+ + S_{13}V_3^+ = S_{11}V_1^+ - S_{13}V_3^-$$

$$V_3^- = S_{31}V_1^+ + S_{33}V_3^+ = S_{31}V_1^+ - S_{33}V_3^-$$

Solving the second equation for  $V_3^-$ :

$$V_3^- = \frac{S_{31}V_1^+}{1 + S_{33}}$$

Then,

$$\Gamma^{(1)} = \frac{V_1^-}{V_1^+} = S_{11} - \frac{S_{13}S_{31}}{1 + S_{33}} \checkmark$$

$$= .1j - \frac{(.6 \angle 45^\circ)(.6 \angle -45^\circ)}{1 + 0} = .1j - .36 = 0.374 \angle 164^\circ \checkmark$$

(verified with supercompact)

4.24


9-

Using Table 4.1, the ABCD matrix of the cascade of four components is,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & 40+j30 \\ 0 & 1 \end{bmatrix}}_{R+jX} \underbrace{\begin{bmatrix} 3 & 0 \\ 0 & \frac{1}{3} \end{bmatrix}}_{\text{TRANSF.}} \underbrace{\begin{bmatrix} 0 & j75 \\ j75 & 0 \end{bmatrix}}_{T-\text{LINE}} = \begin{bmatrix} (-1333+j1778) & j225 \\ j/225 & 0 \end{bmatrix}$$

CHECK:  $AD - BC = 1 \checkmark$ 

Then we have,

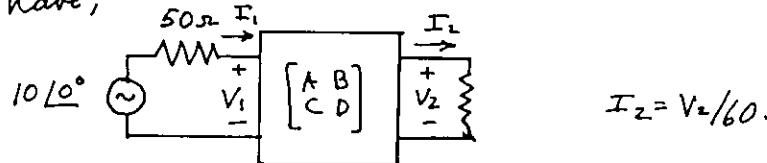

$$V_1 = AV_2 + BI_L = (A+B/60)V_2$$

$$I_1 = CV_2 + DI_L = (C+D/60)V_2$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{(A+B/60)}{(C+D/60)} = \frac{(-1333+j1778+j225/60)}{j/225} = 883.8 + j30.0 \text{ } \Omega \checkmark$$

$$V_L = V_2 = \frac{I_1}{(C+D/60)} = \frac{V_1}{(C+D/60)(Z_{in}+50)} = \frac{10(-j225)}{883.8+j30} = 2.41/-92^\circ$$

68