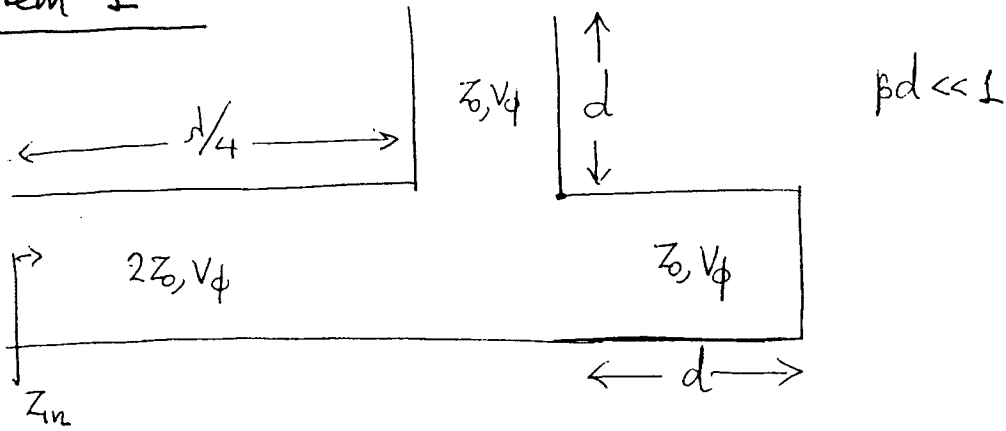


# Problem 1




For the shorted-stub:

$$Z_{in} = jZ_0 \tan \beta d \approx jZ_0 \beta d = jZ_0 \frac{\omega d}{V_\phi} \equiv j\omega L_{eq} \Rightarrow L_{eq} = \frac{Z_0 d}{V_\phi}$$

For the open-stub:

$$Z_{in} = -jZ_0 \cot \beta d \approx \frac{-jZ_0}{\beta d} = \frac{-jZ_0 V_\phi}{\omega d} \equiv \frac{-j}{\omega C_{eq}} \Rightarrow C_{eq} = \frac{d}{Z_0 V_\phi}$$

So,

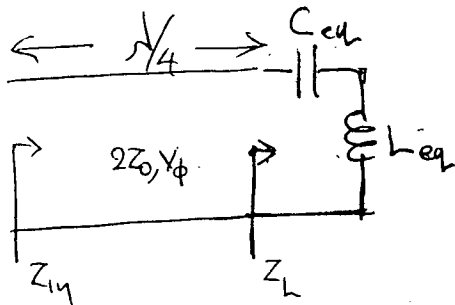


But for an  $d/4$ -transformer:  $Z_{in} = \frac{(2Z_0)^2}{Z_L}$ , i.e.,  $Y_{in} = \frac{Z_L}{4Z_0^2} = \frac{j\omega L_{eq} + \frac{1}{j\omega C_{eq}}}{4Z_0^2}$


This is a parallel combination of  $C'_{eq} = \frac{L_{eq}}{4Z_0^2} = \frac{Z_0 d}{V_\phi} \frac{1}{4Z_0^2} = \frac{d}{4Z_0 V_\phi} = \frac{1}{4} C_{eq}$

$$L'_{eq} = 4Z_0^2 C_{eq} = 4Z_0^2 \frac{d}{Z_0 V_\phi} = \frac{4Z_0 d}{V_\phi} = 4L_{eq}$$

Equivalent Circuit:

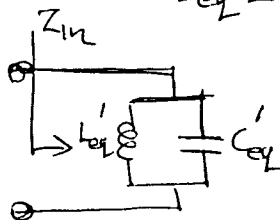

Problem ②:

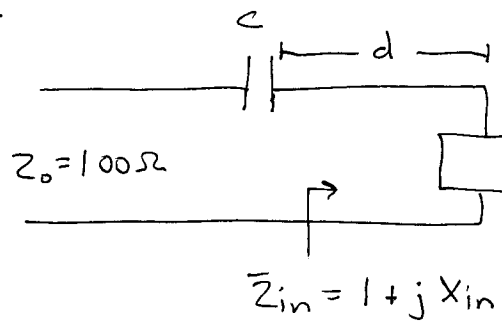


$$f = 3 \text{ GHz}$$

$$\lambda = \frac{c}{f} = 10 \text{ cm}$$

$$Z_L = \cancel{70 + j50} \Omega = 70 + j50 \Omega$$
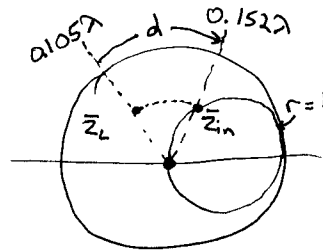
$$\bar{Z}_L = \frac{Z_L}{100} = 0.7 + j0.5$$



$$d = 0.047\lambda = (0.047)(10 \text{ cm}) = \underline{\underline{0.47 \text{ cm}}}$$

Moving towards the generator by a distance 'd' we cross the  $\text{Re}(Z) = 1$  circle.

Hence, the value of  $\bar{X}_{in} = 0.7$


$$\Rightarrow X_{in} = (\bar{X}_{in})(100) = 70 \Omega$$

$$\text{Then, } X_{in} = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_{in}} = \frac{1}{(2\pi)(3 \times 10^9)(70)} = 0.758 \text{ pF}$$

$\therefore$  For  $d = 0.47 \text{ cm}$  and  $C = 0.758 \text{ pF}$  a match is achieved.

### Problem 3 :

-3-

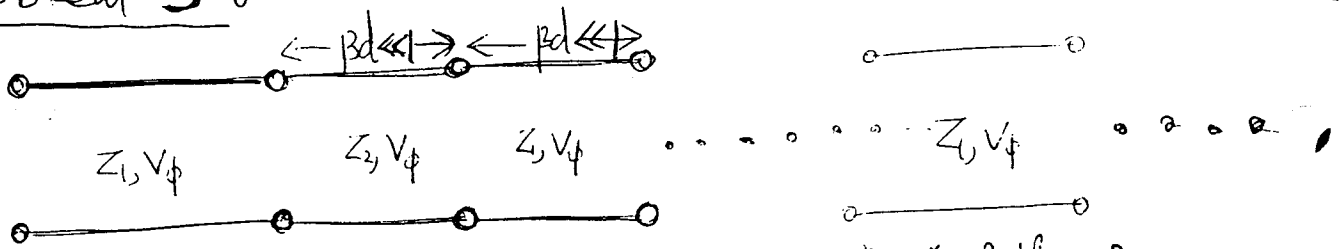

HW#3, Problem 2


For a short-section of a high-impedance T-line:

$$L_{eq} = \frac{Z_1 d}{V_\phi} \text{ in series.}$$


For a short-section of a low-impedance line:

$$C_{eq} = \frac{d}{Z_2 V_\phi} \text{ in shunt}$$

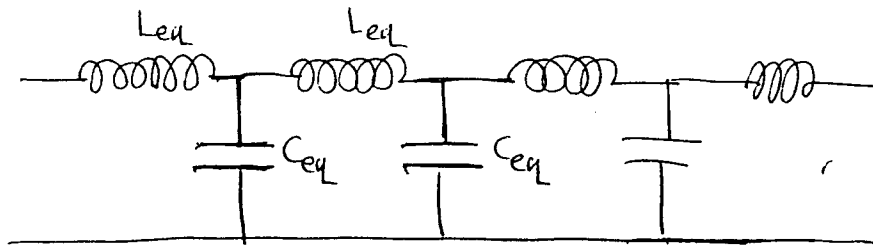Hence the equivalent lumped element circuit is:



Microstrip realization

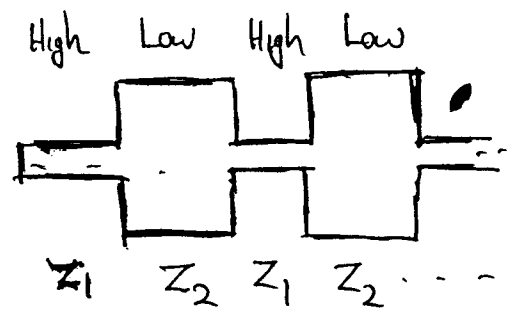

We note that this is the circuit of an equivalent transmission-line with per-unit quantities:

$$\left. \begin{aligned} L' &= L_{eq}/d = Z_1/V_\phi \\ C' &= C_{eq}/d = 1/Z_2 V_\phi \end{aligned} \right\} \begin{array}{l} \text{The limit } \beta d \ll 1 \\ \text{implies that } d \ll \lambda \end{array}$$

So I can define an equivalent characteristic-impedance  $Z_0' = \sqrt{L'/C'}$   
 $= \sqrt{Z_1 Z_2}$

Hence, if the circuit is terminated to  $Z_0'$ , the equivalent

line will be matched and no-reflections shall be incurred.