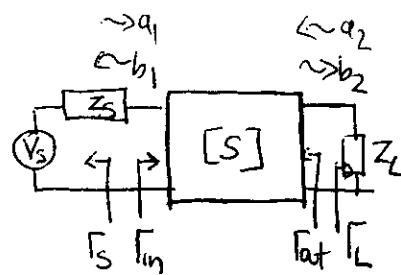


Homework #9

# Problem #4 :



(i) (a) 
$$\begin{cases} b_1 = S_{11}a_1 + S_{12}a_2 \\ b_2 = S_{21}a_1 + S_{22}a_2 \end{cases}$$
 Let  $\Gamma_L = \frac{a_2}{b_2}$  hence  $b_2 = \frac{a_2}{\Gamma_L} = S_{21}a_1 + S_{22}a_2$

$$\Rightarrow a_2 = S_{21}\Gamma_L a_1 + S_{22}\Gamma_L a_2 \Rightarrow a_2(1 - S_{22}\Gamma_L) = S_{21}\Gamma_L a_1$$


Hence  $b_1 = S_{11}a_1 + S_{12} \frac{S_{21}\Gamma_L a_1}{1 - S_{22}\Gamma_L}$  i.e.  $\beta$

$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

(b) By symmetry 
$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

(ii) Let  $Z_s = Z_0 \Rightarrow \Gamma_S = 0$ .

$$P_{avs} = \frac{|V_s|^2}{8Z_0}$$

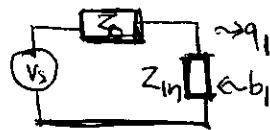

$$V_L = \frac{V_s Z_{in}}{Z_{in} + Z_0} = \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_0} (1 + \Gamma_{in}) a_1$$

$$\Rightarrow a_1 = \frac{V_s Z_{in}}{Z_{in} + Z_0} \frac{1}{\sqrt{Z_0} (1 + \Gamma_{in})}$$

But  $1 + \Gamma_{in} = \frac{2Z_{in}}{Z_{in} + Z_0}$

$$\Rightarrow a_1 = \frac{V_s Z_{in}}{Z_{in} + Z_0} \frac{1}{\sqrt{Z_0}} \frac{Z_{in} + Z_0}{2Z_{in}} = \frac{V_s}{2\sqrt{Z_0}}$$

Hence 
$$P_{avs} = \frac{|V_s|^2}{8Z_0} = \frac{|a_1 2\sqrt{Z_0}|^2}{8Z_0} = \frac{1}{2} |a_1|^2$$

$$(iii) P_{\text{Load}} = \frac{1}{2} (|b_1|^2 - |a_2|^2) = \frac{1}{2} |b_2|^2 (1 - |\Gamma_L|^2)$$

$$\text{But } b_2 = S_{21} a_1 + S_{22} a_2 = S_{21} a_1 + \frac{S_{22} b_2}{\Gamma_L} \Rightarrow$$

$$b_2 (1 - S_{22} \Gamma_L) = S_{21} a_1 \Rightarrow$$

$$b_2 = \frac{S_{21}}{1 - S_{22} \Gamma_L} a_1$$

$$\text{Hence } P_{\text{Load}} = \frac{1}{2} \frac{|S_{21}|^2}{|1 - S_{22} \Gamma_L|^2} (1 - |\Gamma_L|^2) |a_1|^2$$


$$\text{But } a_1 = \frac{V_s}{2Z_0}, \text{ Hence}$$

$$P_{\text{Load}} = P_{\text{avs}} \frac{|S_{21}|^2}{|1 - S_{22} \Gamma_L|^2} (1 - |\Gamma_L|^2), \quad P_{\text{avs}} = \frac{|V_s|^2}{8Z_0}$$

$$(iv) G_T = \frac{P_{\text{Load}}}{P_{\text{avs}}} = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

8.9  $f_0 = 1\text{GHz}$ , HIGH PASS, 3dB E.R.,  $N=5$ ,  $Z_0 = 50\Omega$   
at  $f = 0.6\text{GHz}$ ,  $|\frac{\omega}{\omega_c}| - 1 = \frac{1}{6} - 1 = 0.667$ , so from Figure 8.27b,  
the attenuation for  $N=5$  should be about 41 dB. From  
Table 8.4 the prototype values are,

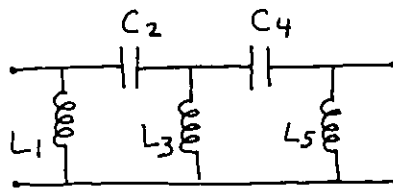- $g_1 = 3.4817$
- $g_2 = 0.7618$
- $g_3 = 4.5381$
- $g_4 = 0.7618$
- $g_5 = 3.4817$



Impedance and frequency scaling using (8.70):

$$L_1 = \frac{Z_0}{\omega_c g_1} = 2.28 \text{ mH} \quad \checkmark$$


$$C_2 = \frac{1}{Z_0 \omega_c g_2} = 4.18 \text{ pF} \quad \checkmark$$

$$L_3 = \frac{Z_0}{\omega_c g_3} = 1.75 \text{ mH} \quad \checkmark$$



$$C_4 = \frac{1}{Z_0 \omega_c g_4} = 4.18 \text{ pF} \quad \checkmark$$

$$L_5 = \frac{Z_0}{\omega_c g_5} = 2.28 \text{ mH} \quad \checkmark$$

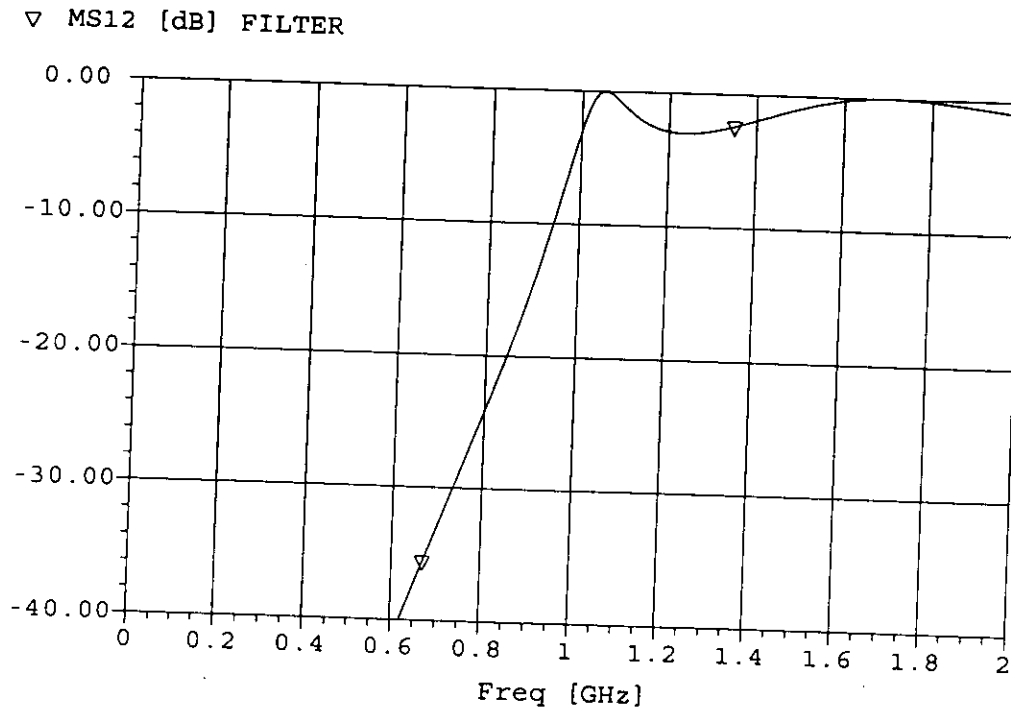The calculated filter response is shown below. Note that the insertion loss at  $f=0.6 \text{ GHz}$  is just a bit more than 40dB.





8.12

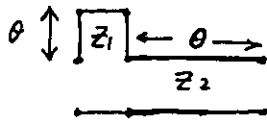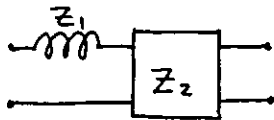

$$Z_s = jZ_1 \tan \theta$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & jZ_1 \tan \theta \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \cos \theta & jZ_2 \sin \theta \\ \frac{j}{Z_2} \sin \theta & \cos \theta \end{bmatrix}$$
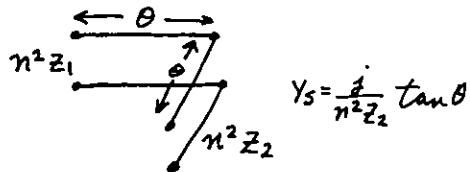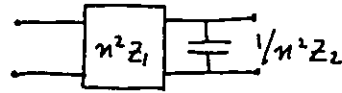
$$= \begin{bmatrix} \cos \theta - \frac{Z_1}{Z_2} \frac{\sin^2 \theta}{\cos \theta} & j(Z_1 + Z_2) \sin \theta \\ \frac{j}{Z_2} \sin \theta & \cos \theta \end{bmatrix}$$



$$Y_s = \frac{j}{n^2 Z_2} \tan \theta$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \theta & j n^2 Z_2 \sin \theta \\ \frac{j \sin \theta}{n^2 Z_1} & \cos \theta \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{j \tan \theta}{n^2 Z_2} & 1 \end{bmatrix}$$

$$= \begin{bmatrix} \cos \theta - \frac{Z_1}{Z_2} \frac{\sin^2 \theta}{\cos \theta} & j n^2 Z_1 \sin \theta \\ \frac{j}{n^2} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) \sin \theta & \cos \theta \end{bmatrix}$$


So these two matrices are equal if,

$$Z_1 + Z_2 = n^2 Z_1$$


$$\text{or, } n^2 = 1 + Z_2/Z_1 \quad \checkmark$$

8.14  $f_0 = 8 \text{ GHz}$ ,  $N = 4$ , L.P., M.F.,  $Z_0 = 50 \Omega$


From Table 8.3 the L.P. prototype is,

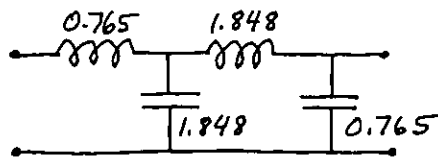


Applying Richards' transform:

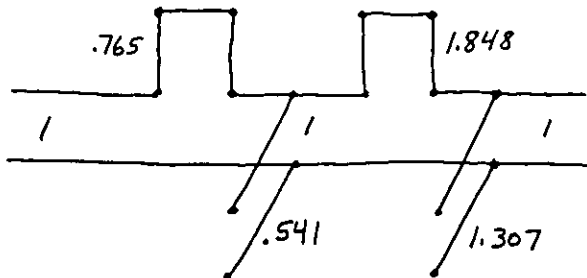


add unit elements:

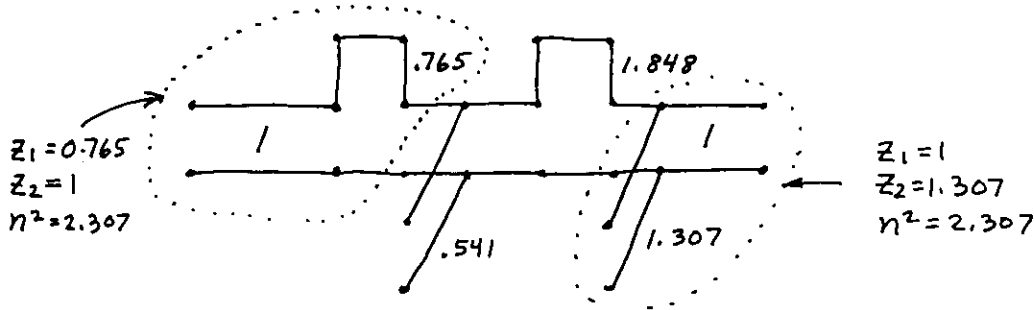

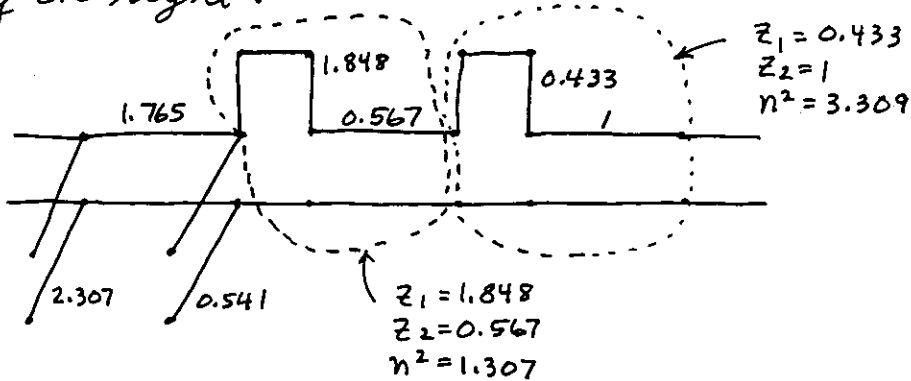
Use the second Kuroda identity on left; first Kuroda identity on right:



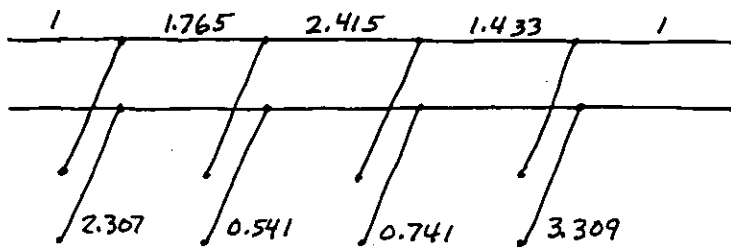Now use the second Kuroda identity twice:



Scale to 50Ω:

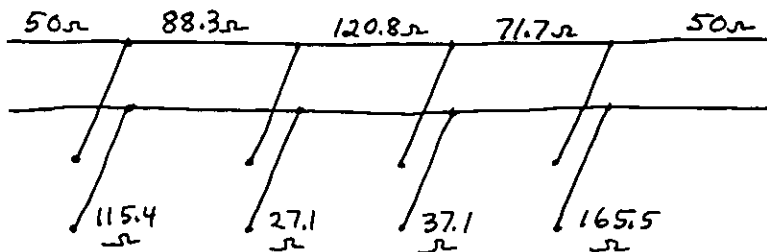

all lines are  $\lambda/8$  long at 8GHz. The calculated filter response is shown on the following page.



▽ MS12 [dB] FILTER

