

ECE424F MICROWAVE CIRCUITS

Homework #2

1. A voltage generator V_g has an internal impedance $Z_g = R_g + jX_g$ and provides power to a lossless transmission line of characteristic impedance Z_0 and propagation constant β . The line has a length l and is terminated to a load impedance Z_L .

a.) Prove that the real power delivered to the load impedance can be expressed as:

$$P = P_A \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_L \Gamma_G e^{-2j\beta l}|^2}$$

where $P_A = |V_g|^2 / (8R_g)$ is the available power from the source and Γ_G , Γ_L are the reflection coefficients at the source and load respectively.

- b.) Deduce an expression for the delivered power when the load is matched to the line.
- c.) Deduce an expression for the delivered power when the generator is matched to the line.
- d.) Starting from the expression found in (a) above, prove that in the case of a conjugate matched line $P = P_A$.

2. Problem 2.13 in textbook.

3. Problem 2.22 in textbook.

4. An air filled transmission line 250m long, operating at 2.86 MHz, is terminated to a load impedance of 200Ω . The line characteristics are $Z_0 = 300\Omega$ and $\alpha = 4 \times 10^{-4}$ Np/m. The line is fed at its input by a voltage generator $V_g = 30V$. Compute the power delivered to the loaded line at input, the power delivered to the load, the power lost in the line and the power reflected from the load.

