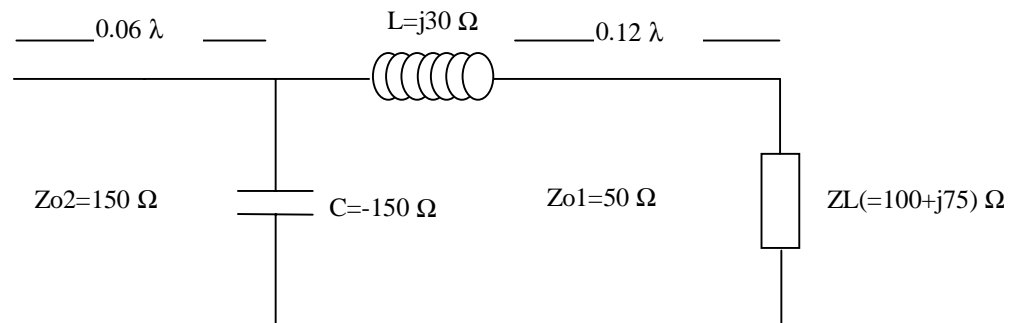


ECE424F MICROWAVES

Homework #3

- 1) Show that a quarter-wavelength $l = \lambda / 4$ open circuited line behaves like a series resonator. Determine the equivalent series inductance L and capacitance C . The line is assumed lossless with characteristic impedance Z_o and phase velocity V_ϕ .
- 2) Show that a short section of a high-impedance line ($Z_o = Z_H$) terminated to a resistive load $R_L \ll Z_H$ behaves like a series inductance L . Determine the equivalent inductance L in terms of the line length l , Z_H and the phase velocity on the line V_ϕ . Likewise, show that a short section of a low-impedance line ($Z_o = Z_L$) terminated to a resistive load $R_L \gg Z_L$ behaves like a shunt capacitance C . Determine the equivalent capacitance C in terms of l , Z_L and V_ϕ .
- 3) Using the Smith chart determine the input impedance of the following circuit:



- 4) Problem 5.9 in textbook.