## **ECE424F MICROWAVE CIRCUITS**

## Homework #6

1. Find expressions for the scattering matrix of a transmission-line with length d, characteristic impedance  $Z_1$  and propagation constant  $\beta$ . The S-parameters refer to an impedance level of  $Z_0$ .

2. Synthesize a two-port passive, reciprocal and lossless transmission-line network with the following scattering parameters:  $S_{11} = S_{22} = 0.2 \angle 108^{\circ}$ .

3. Problems 4.8, 4.16 and 4.24 in textbook.