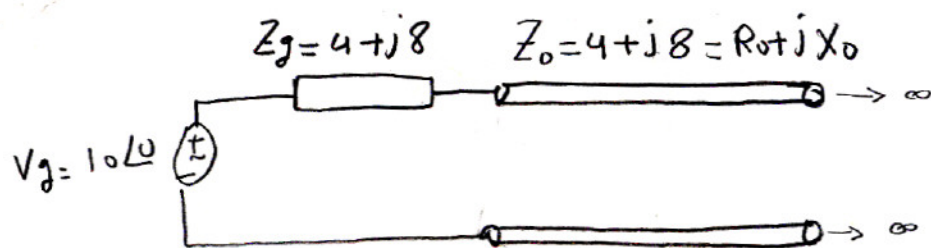


Question 1:

A sinusoidal voltage source $V_g = 10\angle 0^\circ$ with internal impedance of $Z_g = 4 + j8 \ \Omega$ is connected to an *infinitely long general transmission line* with characteristic impedance of $Z_0 = 4 + j8 \ \Omega$. The transmission line resistance and conductance were measured to be $R = 3.2 \ \Omega/\text{m}$ and $G = 5 \times 10^{-4} \ \text{S}/\text{m}$, respectively.

- Find a numerical value for the attenuation constant in Np/m and dB/m. (12 Pts)
- What is the numerical value for the *magnitude of the voltage* wave 2 meters away from the source? (As always, source is at $z = 0$) (12 pts)
- Let $P(z)$ be the time averaged power. What is the numerical value for the ratio $P(z_2)/P(z_1)$ where $z_2 = 2 \ \text{m}$ and $z_1 = 0 \ \text{m}$. (11pts)



note line is matched to source

$$R = 3.2 \text{ } [\Omega/\text{m}]$$

$$G = 5 \times 10^{-4} \text{ } [\text{S}/\text{m}]$$

a) For an infinitely long TL we have shown (in class & HW & lectures) that

$$\textcircled{1} \alpha = \frac{1}{2R_0} (R + G|Z_0|^2) \text{ [NP/m]} \Rightarrow$$

$$\textcircled{2} \alpha = \frac{1}{2 \times 4} (3.2 + 5 \times 10^{-4} |4 + j8|^2) = 0.405 \text{ [NP/m]}$$

$$\frac{1 \text{ NP/m}}{0.405} = \frac{8.69 \text{ dB/m}}{\alpha(\text{dB})} \Rightarrow \alpha(\text{dB}) = 3.519 \text{ [dB/m]}$$

$$b) V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} = V_0^+ e^{-\gamma z} = V_0^+ e^{-\alpha z} e^{-j\beta z}$$

since line is infinitely long

Recall $V_0^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{(1 - \Gamma_L \Gamma_g e^{-2\gamma l})}$ + then

$$V_0^+ = V_g \frac{Z_0}{Z_0 + Z_g} = 10 \angle 0 \frac{Z_0}{2Z_0} = 5 \angle 0$$

since $\Gamma_L = \Gamma_g = 0$

then


$$V(z) = 5 e^{-0.405z} e^{-j\beta z} \Rightarrow |V(z=2)| = 5 e^{-0.405 \times 2} = 2.224 \text{ [V]}$$

c) we have $P(z) = \frac{|V_0^+|^2}{2|Z_0|^2} R_0 e^{-2\alpha z} \Rightarrow \frac{P(z=z_2)}{P(z=z_1)} = \frac{e^{-2\alpha z_2}}{e^{-2\alpha z_1}} = \frac{e^{-2\alpha z_2}}{e^{-0}} \Rightarrow$

$$\frac{P(z=z_2)}{P(z=z_1)} = e^{-4 \times 0.405} = 0.198$$

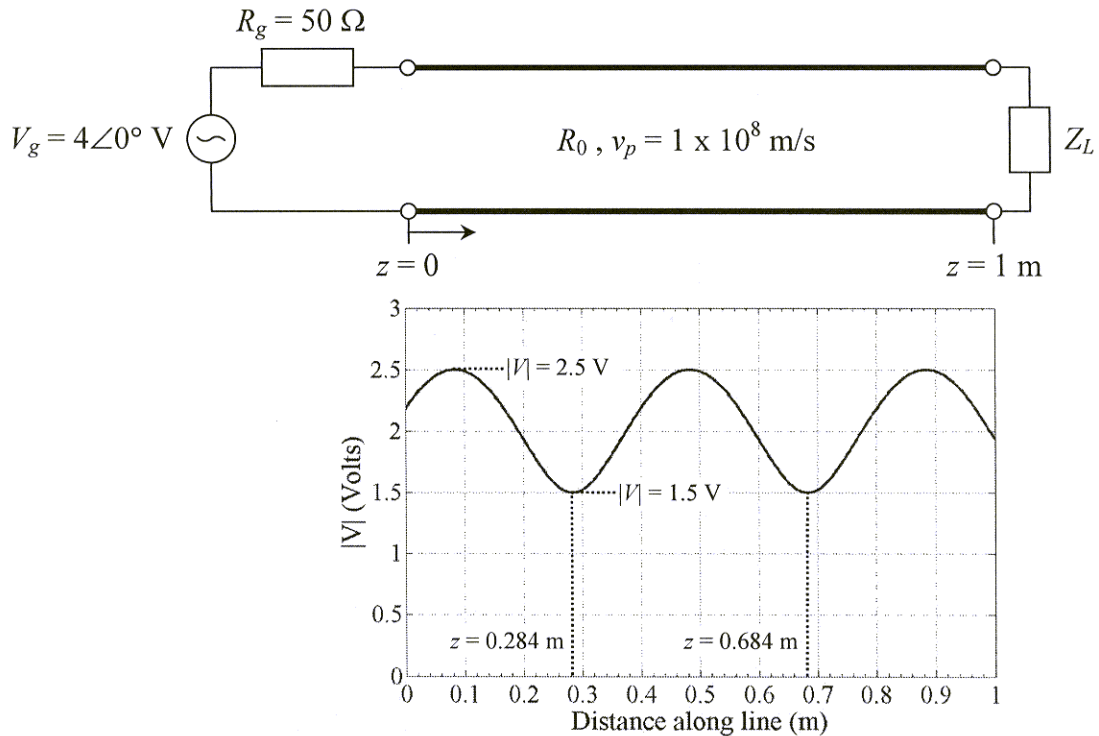Question 2

In the figure below, an unknown load, Z_L , is attached to an $R_0 = 50 \Omega$ lossless transmission line. Also shown is the measured voltage standing wave pattern for this transmission line circuit.



- (a) Determine the standing wave ratio, S , the wavelength, λ , and the frequency of the source, f .

$$S = \frac{|V_{\max}|}{|V_{\min}|} = \frac{2.5}{1.5} = 1.\bar{6} = \underline{\underline{1.67}}$$

$$\lambda = 2 \times (0.684 \text{ m} - 0.284 \text{ m}) = \underline{\underline{0.8 \text{ m}}}$$

$$f = \frac{v_p}{\lambda} = \frac{1 \times 10^8 \text{ m/s}}{0.8 \text{ m}} = 1.25 \times 10^8 \text{ Hz} = \underline{\underline{125 \text{ MHz}}}$$

(b) Find the magnitude *and* phase of the reflection coefficient at the load.

* The magnitude is found from the standing wave ratio value

$$|\Gamma_L| = \frac{S-1}{S+1} = \underline{\underline{\frac{1}{4}}}$$

* The phase is found from the position of the first minimum from the load.

$$\phi_{\Gamma_L} - 2\beta z'_{\min} = \pm \pi$$

$$\rightarrow \text{with } z'_{\min} = 1\text{m} - 0.684\text{m} = 0.316\text{m}$$

$$\begin{aligned} \rightarrow \text{For } +\pi, \quad \phi_{\Gamma_L} &= \pi + 2\left(\frac{2\pi}{\lambda}\right)z'_{\min} = \pi + 4\pi\left(\frac{0.316\text{m}}{0.8\text{m}}\right) \\ &= 2.58\pi = 464.4^\circ \text{ or } 104.4^\circ. \end{aligned}$$

$$\rightarrow \text{For } -\pi, \quad \phi_{\Gamma_L} = -\pi + 4\pi\left(\frac{0.316\text{m}}{0.8\text{m}}\right) = 0.58\pi = 104.4^\circ$$

$\rightarrow$ So it doesn't matter whether you choose $\pm\pi$.

$$\therefore \Gamma_L = \frac{1}{4} \angle 104.4^\circ = \underline{\underline{-0.062 + j0.242}}$$

(c) Find the unknown load impedance, Z_L .

$$\text{Since } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{we can solve for } Z_L.$$

$$\text{So } (Z_L + Z_0)\Gamma_L = Z_L - Z_0$$

$$Z_L(\Gamma_L - 1) = Z_0(-1 - \Gamma_L)$$

$$\begin{aligned} \therefore Z_L &= Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = (50) \frac{1 + 0.25 \angle 104.4^\circ}{1 - 0.25 \angle 104.4^\circ} \\ &= \underline{\underline{39.5 + 20.4j}} \end{aligned}$$

* So we can see this load is a resistance in series with an inductance.

(d) Determine the expression for the instantaneous voltage on the line.

* The general expression for the total phasor voltage on the line is

$$\bar{V}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

→ Since the source is matched to the line ($R_g = R_0 = 50 \Omega$),

$$V_0^+ = V_g \frac{R_0}{R_0 + R_g} = \frac{V_g}{2} = 2 \angle 0^\circ \text{ V.}$$

* To find out what V_0^- is we must evaluate $\bar{V}(z)$ at the load:

$$\bar{V}(z=l) = \underbrace{V_0^+ e^{-j\beta(l)}}_{\text{incident wave at the load}} + \underbrace{V_0^- e^{+j\beta(l)}}_{\text{reflected wave at the load}}$$

$$\rightarrow \text{We know that } \Gamma_L = \frac{V_{\text{ref at load}}}{V_{\text{inc at load}}} = \frac{V_0^- e^{j\beta l}}{V_0^+ e^{-j\beta l}} = \frac{V_0^-}{V_0^+} e^{2j\beta l}$$

$$\therefore V_0^- = V_0^+ \Gamma_L e^{-2j\beta l} = V_0^+ |\Gamma_L| e^{j\phi_{\Gamma_L}} e^{-2j\beta l} = V_0^+ |\Gamma_L| e^{j(\phi_{\Gamma_L} - 2\beta l)}$$

$$\begin{aligned} \therefore \bar{V}(z) &= V_0^+ e^{-j\beta z} + V_0^+ |\Gamma_L| e^{j(\phi_{\Gamma_L} - 2\beta l)} e^{+j\beta z} \\ &= V_0^+ e^{-j\beta z} + V_0^+ |\Gamma_L| e^{j(\phi_{\Gamma_L} - 2\beta l + \beta z)} \end{aligned}$$

* The instantaneous voltage is then

$$\begin{aligned} v(t, z) &= \text{Re}[\bar{V}(z) e^{j\omega t}] = \text{Re}[V_0^+ e^{j(\omega t - \beta z)} + V_0^+ |\Gamma_L| e^{j(\omega t + \phi_{\Gamma_L} - 2\beta l + \beta z)}] \\ &= V_0^+ \cos(\omega t - \beta z) + V_0^+ |\Gamma_L| \cos(\omega t + \beta z + \phi_{\Gamma_L} - 2\beta l) \end{aligned}$$

→ For this circuit, $\phi_{\Gamma_L} = 0.58\pi$, $2\beta = 2\left(\frac{\pi}{\lambda}\right) = 2\left(\frac{2\pi}{0.8}\right) = 5\pi = \pi$

$$\therefore \boxed{v(t, z) = 2 \cos(\omega t - \beta z) + 0.5 \cos(\omega t + \beta z - 0.42\pi)}$$

→ For $z' \Rightarrow z = l - z'$ this becomes

$$v(t, z') = 2 \sin(\omega t + \beta z') + 0.5 \sin(\omega t - \beta z' + 0.58\pi)$$

Question 3:

A researcher has measured the input impedance of a lossless transmission line of the length $l = 57$ cm, under the open condition, to be $-j121.24 \Omega$. The input impedance of the same line under the short condition is $j40.42 \Omega$. She also knows that the line length is between 3λ and 3.25λ . Answer the following questions:

- What are the numerical values for the Z_0 , α , and β . (20 pts)
- For the above line terminated with $Z_L = 3 + j5$, what is the numerical value of the input impedance? (10 pts)

$$Z_{in}^{op} = -j121.24 \Omega, \quad Z_{in}^{sh} = j40.42 \Omega \quad 3\lambda < l < \frac{13}{4}\lambda$$

a)

$$l = 0.57 \text{ m}$$

$$Z_0 = \sqrt{Z_{in}^{op} Z_{in}^{sh}} = \sqrt{(-j121.24)(j40.42)} \Rightarrow$$

$$Z_0 = 70 \Omega \Rightarrow R_0 = 70 \Omega \text{ \& } X_0 = 0$$

For General TL we have $\tanh \beta l = \sqrt{\frac{Z_{in}^{sh}}{Z_{in}^{op}}} \Rightarrow$ For lossless line

$$j \tan(\beta l) = \sqrt{\frac{j40.42}{-j121.24}} \Rightarrow \beta l = \tan^{-1} \left[\frac{1}{j} \sqrt{\frac{j40.42}{-j121.24}} \right] + n\pi$$

$$\beta l = 0.524 + n\pi$$

when $n = 0, \pm 1, \pm 2, \dots$

$$\text{since } 3\lambda < l < \frac{13}{4}\lambda \Rightarrow 3 \times \frac{2\pi}{\lambda} < \beta l < \frac{13}{4} \times \frac{2\pi}{\lambda} \Rightarrow$$

$$6\pi < \beta l < 6.5\pi \Rightarrow 6\pi < 0.524 + n\pi < 6.5\pi \Rightarrow$$

$$18.850 < 0.524 + n\pi < 20.420 \Rightarrow \boxed{n=6} \text{ then}$$

$$\beta = \frac{0.524 + n\pi}{l} = \frac{0.524 + 6\pi}{0.57} = 33.989 \text{ rad/m}$$

$$\beta l = 19.373$$

$$b) \quad Z_{in} = R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = 70 \frac{(3+j5) + j70 \tan(19.373)}{70 + j(3+j5) \tan(19.373)} \Rightarrow$$

$$Z_{in} = 41.35 + j47.24 = 47.44 e^{j84.74^\circ}$$

$$= 47.44 e^{j1.48(\text{rad})}$$