ame:
re

Faculty of Applied Science and Engineering

ECE357 Electromagnetic Fields

First Test, February 16, 2006

Examiners – M. Mojahedi

Only Calculators approved by Registrar allowed Answer the questions in the spaces provided or on the facing page A complete paper consists of answers to all questions For numerical answers specify units

DO NOT REMOVE STAPLE

Do not write in these spaces

1	2	3	TOTAL

 $\varepsilon_0 = 8.854 \times 10^{-12} [F/m], \quad \mu_0 = 4\pi \times 10^{-7} [H/m], \quad c = 3 \times 10^8 [m/s]$

4.5.4
$$\operatorname{csch} z = 1/\operatorname{sinh} z$$

4.5.5 $\operatorname{sech} z = 1/\operatorname{csch} z$
4.5.6 $\operatorname{coth} z = 1/\operatorname{tanh} z$
4.5.6 $\operatorname{coth} z = 1/\operatorname{tanh} z$
4.5.2 $\operatorname{cosh} z - \operatorname{sinh} z = e^{-z}$
Negative Angle Formulas
4.5.21 $\operatorname{sinh} (-z) = -\operatorname{sinh} z$
4.5.22 $\operatorname{cosh} (-z) = \operatorname{cosh} z$
4.5.23 $\operatorname{tanh} (-z) = -\operatorname{tanh} z$
4.5.23 $\operatorname{tanh} (-z) = -\operatorname{tanh} z$
4.5.24 $\operatorname{sinh} (z_1 + z_2) = \operatorname{sinh} z_1 \operatorname{cosh} z_2$
 $+\operatorname{cosh} z_1 \operatorname{sinh} z_2$
 $+\operatorname{cosh} z_1 \operatorname{sinh} z_2$
 $+\operatorname{sinh} z_1 \operatorname{sinh} z_2$
4.5.25 $\operatorname{cosh} (z_1 + z_2) = \operatorname{cosh} z_1 \operatorname{cosh} z_2$
 $+\operatorname{sinh} z_1 \operatorname{sinh} z_2$
 $+\operatorname{sinh} z_1 \operatorname{sinh} z_2$
4.5.26 $\operatorname{tanh} (z_1 + z_2) = (\operatorname{coth} z_1 + \operatorname{tanh} z_2)/(1 + \operatorname{tanh} z_1 \operatorname{tanh} z_2)$
4.5.27 $\operatorname{coth} (z_1 + z_2) = (\operatorname{coth} z_1 - \operatorname{tanh} z_2)/(1 + \operatorname{tanh} z_1 \operatorname{tanh} z_2)$

Relation to Circular Functions (see 4.3.49 to 4.3.54)

Hyperbolic formulas can be derived from trigonometric identities by replacing z by iz

4.5.7 $\sinh z = -i \sin iz$

4.5.28
$$\sinh \frac{z}{2} = \left(\frac{\cosh z - 1}{2}\right)^{\frac{1}{2}}$$

Half-Angle Formulas

$$\cosh x = \frac{e^x + e^{-x}}{2}, \quad \sinh x = \frac{e^x - e^{-x}}{2}, \quad \cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}, \quad \sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

Problem 1: On a lossless transmission line with characteristic impedance of 150Ω the following observations were noted: distance of first voltage minimum from the load = 3 cm; distance of first voltage maximum from the load = 9 cm, standing wave ratio = 3. Determine the value of the load impedance (Z_L). (Total points: 30)

* The distance between Consecutive maximum Eminimum in a TL is $\lambda/4 \Longrightarrow \qquad \lambda = 0.09 - 0.03 \Longrightarrow$ $\lambda = 0.24 \text{ [m]}$ * Location of Volfese maximums are givenly $\theta_{\Gamma-2B} = 2m \times 100 \text{ m}$ first maximum is at $n=0 \Rightarrow$ $\theta_{\Gamma-2B} = 2m \times 2m \times 100 \text{ m}$

$$\begin{aligned}
\Theta_{\Gamma} - 2RS Smex = 0 &= -7 \\
\Theta_{\Gamma} = \frac{4R}{J}Smex = \frac{4R}{0.24} \times 0.09 = 4.7/2 (Rdian) = 270^{\circ} \\
\Theta_{\Gamma} = \frac{4R}{J}Smex = \frac{4R}{0.24} \times 0.09 = 4.7/2 (Rdian) = 270^{\circ} \\
\text{For similary the location of first minimum is given by } \\
\Theta_{\Gamma} - 2RS Timin = -R => \Theta_{\Gamma} = \frac{4R}{J}Simin - R = \frac{4R}{0.24} \times 0.03 - R => \\
\Theta_{\Gamma} = -1.5708(Rd) = 4.712(Rd) = 270^{\circ} \\
\Theta_{\Gamma} = -1.5708(Rd) = 4.712(Rd) = 270^{\circ} \\
\text{Fom clowe } J = 1\Gamma R = 0.\Gamma R = 0.10.5 R \\
= 0.10.5 R$$

Problem 2: In class we showed that the input impedance $[Z_i(l)]$ for a lossless transmission line terminated on a short is identically zero at $l = \lambda/2$, λ , $3\lambda/2$, 2λ , Prove that for a short circuited lossy transmission line the input impedance is never identically zero at $l = \lambda/2$, λ , $3\lambda/2$, 2λ , ... (Total points: 35)

$$Problem 2)$$
For a Jussy Transmission Line
$$Z_{i}(l) = Z_{0} \quad \frac{Z_{i}+Z_{i} \tan h(ll)}{Z_{0}+Z_{i} \tanh h(ll)} \quad \text{for short } cht$$

$$Z_{i}(l) = Z_{0} \tanh (kl) = Z_{0} \tanh (ll) \quad \text{for short } cht$$

$$Z_{i}(l) = Z_{0} \tanh (kl) = Z_{0} \tanh (ll) \quad \text{for short } cht$$

$$Z_{i}(l) = Z_{0} \tanh (kl) = Z_{0} \tanh (ll) \quad \text{for } h(ll) \quad \text{for } h$$

Problem 3: A transmission line is modeled by an equivalent circuit shown below. For this transmission line, find the general transmission line equations (the so-called telegrapher's equations) for instantaneous voltage and current, i.e., as a function of time (t) and space (z). Show all your work. (Total points: 35)



KCL at node A: $i(z,t) = i' + v(z,t) \frac{G}{2} \delta z + \frac{G}{2} \Delta z \frac{1}{2t} v(z,t)$ (1) KCL at node B: $i' = i(z + \Delta z, t) + \frac{G}{2} \Delta z v(z + \Delta z, t) + \frac{G}{2} \Delta z \frac{1}{2t} v(z + \Delta z, t)$ (2) KVL of inner loop: $v(z,t) = R\Delta z i' + L\Delta z \frac{1}{2t} i' + v(z + \Delta z, t)$ (3) USE (2) in (1) to eliminate i': $i(z,t) - i(z + \Delta t, t) = \frac{G}{2} \Delta z v(z, t) + \frac{G}{2} \Delta z \frac{1}{2t} v(z + \Delta z, t) + \frac{G}{2} \Delta z v(z + \Delta z, t) + \frac{G}{2} \Delta z \frac{1}{2t} v(z + \Delta z, t) +$

 $\frac{I(z,t) - I(z+\Delta t,t)}{\delta z} = \frac{1}{2} \Delta z \quad v(z,t) + \frac{1}{2} \Delta z \quad \frac{1}{2} \quad v(z,t) + \frac{1}{2} \Delta z \quad v(z,t) + \frac{1}{2} \frac{1}{2} \quad v(z,t) + \frac{1}{2} \frac{1}{2} \quad v(z,t) = \frac{1}{2} \frac{1}{2} \quad \frac{1$

Note that lim v(z+AZ, t) = v(z,t); Physically this would mean that nodes A and B have the same voltage and R,L contribute zero voltage drop.

sub (3) into (9) to diminite
$$v(z + \Delta z_1 t)$$
:

$$-\frac{\partial i(z_1 t)}{\partial z} = \frac{G}{2} v(z_1 t) + \frac{G}{2} \frac{1}{2} v(z_1 t) + \lim_{d \to \infty} \left[\frac{G}{2} v(z_1 t) - \frac{G}{2} R_{\Delta z} \frac{1}{t} - \frac{G}{2} L_{\Delta z} \frac{2}{\delta t} \frac{1}{t} + \frac{G}{2} \frac{1}{2} v(z_1 t) - \frac{G}{2} R_{\Delta z} \frac{2}{\delta t} \frac{1}{t} - \frac{G}{2} L_{\Delta z} \frac{2}{\delta t} \frac{1}{t} + \frac{G}{2} \frac{1}{2} v(z_1 t) - \frac{G}{2} R_{\Delta z} \frac{2}{\delta t} \frac{1}{t} - \frac{G}{2} L_{\Delta z} \frac{2}{\delta t} \frac{1}{t} + \frac{G}{2} \frac{1}{t} v(z_1 t) - \frac{G}{2} R_{\Delta z} \frac{2}{\delta t} \frac{1}{t} - \frac{G}{2} L_{\Delta z} \frac{2}{\delta t} \frac{1}{t} + \frac{G}{2} \frac{1}{t} v(z_1 t) - \frac{G}{2} R_{\Delta z} \frac{2}{\delta t} \frac{1}{t} - \frac{G}{2} L_{\Delta z} \frac{2}{\delta t} \frac{1}{t} \frac{1}{t} + \frac{G}{2} \frac{1}{t} \frac{1}{$$