

### Problem Set #3

#### ECE357 /ECE320 University of Toronto

- Plot the voltage standing wave patterns for the case of a lossless line
  - Terminated with an open ( $R_L \rightarrow \infty$ ).
  - Terminated with a short ( $R_L \rightarrow 0$ ).
  - How are these patterns different from those obtained in class?
- The standing wave ratio  $S$  on a lossless  $50\Omega$  line ( $Z_0 = R_0 = 50\Omega$ ) terminated in an unknown load impedance is found to be 3. The distance between successive voltage minima is 20cm and the first minimum is located 5cm from the load. Determine
  - the reflection coefficient  $\Gamma$ ,
  - the load impedance  $Z_L$ ,
  - the length of a lossless line and a terminating resistive load that can replace the original load ( $Z_L$ ) without effecting the waveforms to the left of the original  $Z_L$ .
- A lossless transmission line has a capacitance of 200pF/m and an inductance of  $0.5 \mu\text{H/m}$ . It is excited with a 1kHz sinusoidal source. The magnitude of the voltage measured across a  $35\Omega$  load is 100V. Find
  - the line characteristic impedance  $R_0$ ,
  - the voltage reflection coefficient  $\Gamma$  at the load,
  - the phase velocity  $v_p$ ,
  - the wavelength  $\lambda_0$ ,
  - the forward and backward traveling wave amplitudes  $|V_0^+|$  and  $|V_0^-|$ ,
  - the line propagation constant  $\beta$ .
- A transmission line of characteristic impedance  $R_0 = 50\Omega$  is to be matched to a load impedance of  $Z_L = 40 + j10\Omega$  through a length  $l'$  of another transmission line of characteristic impedance  $R_0'$ . What are the required  $l'$  and  $R_0'$  for matching?
- A generator with an open circuit voltage  $V_g = 10 \cos(8000\pi t)$  [V] and internal impedance  $Z_g = 40 + j30[\Omega]$  is connected to a  $50[\Omega]$  distortionless line. The line has a resistance of  $0.5 [\Omega/m]$  and its lossy dielectric medium has a loss tangent of 0.18%. The line is 50 [m] long and is terminated in a matched load. Find
  - the instantaneous expressions for the voltage and current at an arbitrary location on the line,
  - the instantaneous expressions for the voltage and current of the load,
  - the average power transmitted to the load.

6. A 2m lossless air-spaced transmission line with a characteristic impedance of  $50\Omega$  is terminated with an impedance of  $40 + j30\Omega$ . At an operating frequency of 200MHz the phase velocity in the line is the same as the speed of light in vacuum. What is the line input impedance?
7. A sinusoidal voltage generator with  $V_g = 0.1\angle 0^\circ$  V and internal impedance  $Z_g = R_0$  is connected to a lossless transmission line having a characteristic impedance  $R_0 = 50\Omega$ . The line is  $l$  meters long and is terminated with a load resistance  $R_L = 25\Omega$ . Find
- $V_i, I_i, V_L, I_L$  in terms of the line length  $l$ ,
  - the standing wave ratio on the line,
  - the average power delivered to the load.