

Problem Set #4
ECE357/ECE320
University of Toronto

1) Let $Z_L = 60 + j 43 [\Omega]$ and $Z_o = 50 [\Omega]$. Find the input impedance with $l = 0.32$ [m] and line wavelength of $\lambda = 0.854$ [m].

2) The inductance and capacitance of a lossless $50 [\Omega]$ line are $0.251 [\mu\text{H}/\text{m}]$ and $99.5 [\text{pF}/\text{m}]$. The line is attached to a source of $10\cos(2\pi 10^6 t)$ with internal impedance of $1[\Omega]$. The length of the line is 5 [m] and is terminated on a load resistance of $50 [\Omega]$.

- a) What are the instantaneous voltage and current at any point?
- b) What is the power delivered to the load?

3) This problem answers the question why we want to minimize the standing wave ratio on the line. Let P_i be the incident time averaged power approaching a point on a lossless line, P_r the time averaged reflected power on the line, and P_t the time averaged transmitted power available to do work on the load. You can think of the P_t as a useful power since, for example, it can be radiated by an antenna connected to the line. Show that the following is true:

$$P_t = P_i - P_r = \frac{|V_o^+|^2}{2Z_o} (1 - |\Gamma_L|^2) = P_i (1 - |\Gamma_L|^2)$$

4) The capacitance of a 0.6 [m] long lossless line measured at 100 [KHz] was 54 [pF] and its inductance was equal to 0.3 [μH].

- a) Determine Z_o
- b) Calculate X_{io} and X_{is} (open and short circuit impedance) at 10 MHz
- c) What is the dielectric constant of the insulating medium used in the transmission line?

5) The characteristic impedance of an air-line lossless transmission line is $75 [\Omega]$. Use a Smith chart to find the input impedance and input admittance at 200 [MHz] of such a line that is a) 1 [m] long and open-circuited, and (b) 0.8 [m] long and short-circuited.

6) For a general transmission line (lossy or lossless)

- a) Express $V(z)$ and $I(z)$ in terms of the load voltage V_L and load current I_L in exponential form and in hyperbolic form
- b) Express $V(z)$ and $I(z)$ in terms of the voltage V_i and current I_i at the input end in exponential form and hyperbolic form.

7) A d-c voltage V_o is applied at $t = 0$ to the input terminals of an open-circuited air-dielectric line of length l through a series-resistance equal to $R_o/2$, where R_o is the characteristic resistance of the line.

a) Draw the voltage reflection diagram

b) Sketch $V(z = 0, t)$.

c) Sketch $V(l/2, t)$.