

voltage

Q: Plot the standing wave patterns for the case of lossless line terminated with open ($R_L \rightarrow \infty$) and lossless line terminated in short ($R_L \rightarrow 0$). How are these patterns different from those obtained in class with $R_L > R_0$ & $R_L < R_0$ (with $R_L \neq 0$ & $R_L \neq \infty$)

Sol: We use the expression for $V(z')$ from notes EQ (1-P52)

$$\textcircled{1} V(z') = \frac{I_L (R_L + R_0)}{2} e^{j\beta z'} \left\{ 1 + |\Gamma| e^{j(\theta_\Gamma - 2\beta z')} \right\}$$

Under open condition $R_L \rightarrow \infty$:


Note that for $R_L \rightarrow \infty$ $\Gamma = \frac{R_L - R_0}{R_L + R_0} \rightarrow \frac{\textcircled{2}}{\textcircled{3}} = 1 \angle 0 = 1 e^{j0}$

Also $\textcircled{4} I_L = 0$ but $V_L \neq 0$ $V_L = I_L R_L$ $\textcircled{6}$

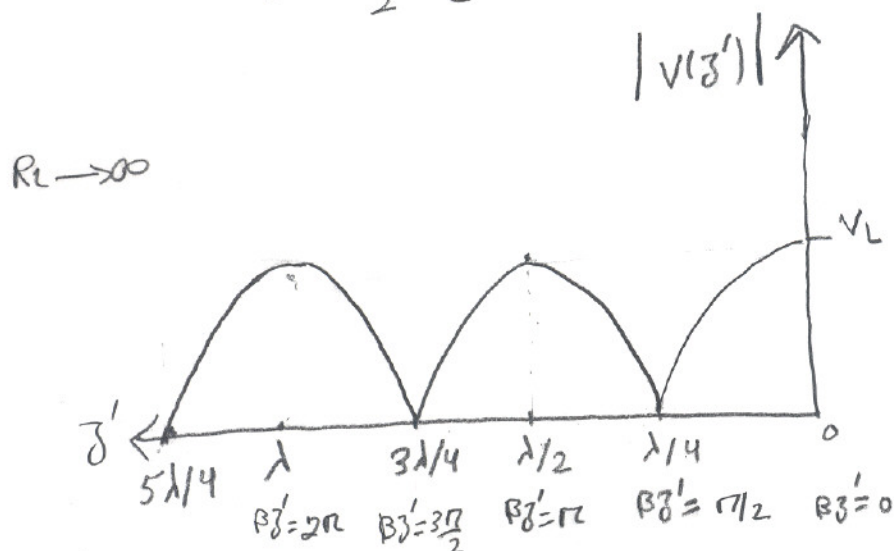(1) Can be written as-

$$V(z') = \frac{V_L + I_L R_0}{2} e^{j\beta z'} \left\{ 1 + e^{-j2\beta z'} \right\} \quad \textcircled{7}$$

$$= \frac{V_L}{2} \left\{ e^{j\beta z'} + e^{-j\beta z'} \right\} = V_L \cos(\beta z')$$



↑ This is EQ 9-143a of Cheng. You may want to look at the way that Cheng derives this equation.

$$\beta z' = \frac{2\pi}{\lambda} z'$$

Fig 1

* The main difference between this curve & what we found in class for $R_L > R_0$, is that curves in Fig 1 go to zero at $\lambda/4, 3\lambda/4, 5\lambda/4$, etc.

Under short condition:

$$\begin{aligned} R_L &\rightarrow 0 & \Gamma &= \frac{R_L - R_0}{R_L + R_0} = -1 = 1 e^{-j\pi} \Rightarrow |\Gamma| = 1 & \angle \Gamma &= -\pi \\ \textcircled{1} & & \textcircled{2} & & \textcircled{3} & \textcircled{4} \end{aligned}$$

For short $V_L = 0$, $I_L \neq 0$ $V_L = I_L R_L$


⑤ ⑥ ⑦

Eq (1-P1) $\Rightarrow$

$$\begin{aligned} \textcircled{8} \quad V(z') &= \frac{V_L + I_L R_0}{2} e^{j\beta z'} \left\{ 1 + |\Gamma| e^{j(-\pi - 2\beta z')} \right\} \\ &= \frac{I_L R_0}{2} e^{j\beta z'} \left\{ 1 - e^{j2\beta z'} \right\} \\ &= \frac{I_L R_0}{2} \left\{ e^{j\beta z'} - e^{-j\beta z'} \right\} \frac{j}{j} = j I_L R_0 \sin(\beta z') \end{aligned}$$

$$\Rightarrow |V(z')| = R_0 |I_L \sin(\beta z')|$$

← this is equation 9-144 of Cheng

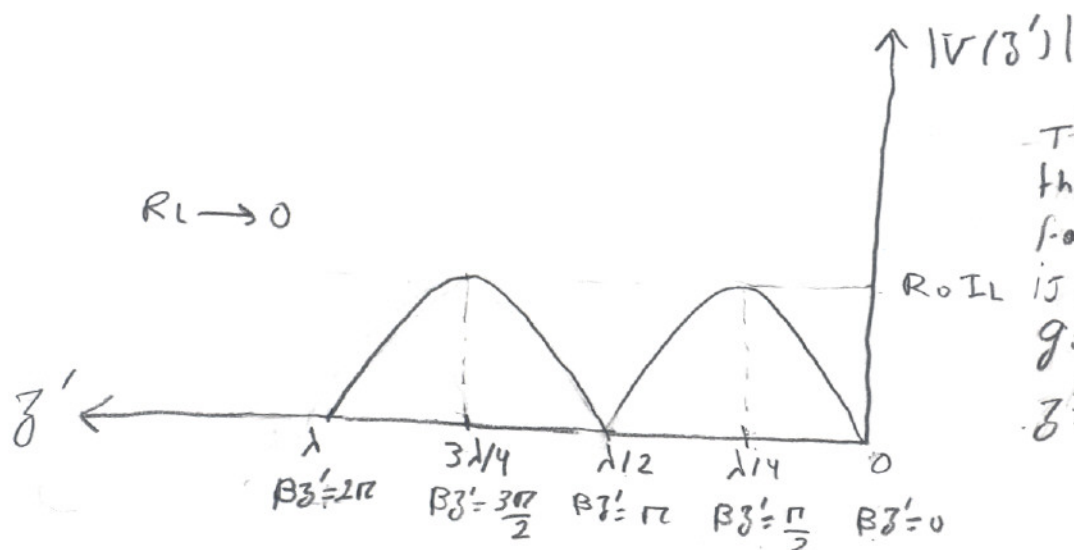

The difference between this curve & the one we found in class ($R_L < R_0$) is that here $|V(z')|$ goes to zero at $z' = \lambda/4, 3\lambda/4, \dots$

Q: The standing wave ratio (S') on a lossless $50\ \Omega$ line ($Z_0 = R_0 = 50$) terminated in an unknown load impedance is found to be 3. The distance between successive voltage minima is 20 cm, & first minimum is located at 5 cm from the load. Determine a) the reflection coefficient Γ , and b) the load impedance Z_L & c) Find the length of a lossless line and a terminating resistive load that can replace the original load (Z_L) without effecting the wave forms to the left of the Z_L .

Note: this is Example 9-9 of Cheng. repeated here so few important points are brought to your attention.

Sol: We find $|\Gamma|$ from
$$\textcircled{1} \quad |\Gamma| = \frac{S' - 1}{S' + 1} = \frac{3 - 1}{3 + 1} = \frac{1}{2}$$

We also need to find the phase angle for Γ . From your class notes you know that $|V_{\min}|$ occurs at
$$\textcircled{2} \quad \theta_\Gamma - 2\beta z'_m = -(2n+1)\pi$$

 $n=0, 1, 2, \dots$
 where θ_Γ is the Γ phase angle & z'_m is the location of voltage minimum measured from the load. since the problem states, the location of first minimum then $n=0$ in (2) & $z'_m = 5\text{ cm}$.

But what is β ? We are told the distance between successive voltage minima is 20 cm, this means
$$\textcircled{3} \quad \frac{\lambda}{2} = 20\text{ cm} \Rightarrow$$

$$\textcircled{4} \quad \lambda = 40\text{ cm} \quad \& \quad \textcircled{5} \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.4} = 5\pi \text{ (rad)}$$

then in (2-P3) we have

$$\theta_r = -\pi + 2\beta z'_m$$

4

then

$$\Gamma = |\Gamma| e^{j\theta_r} = \frac{1}{2} e^{-j0.5\pi}$$

$$= 0.5 \left[\cos\left(\frac{\pi}{2}\right) - j \sin\left(\frac{\pi}{2}\right) \right] = -j0.5$$

$$= -\pi + 2 \times 5\pi \times 0.05 = -0.5\pi \text{ (rad)}$$

b) The load impedance can be found from

$$\textcircled{1} \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \text{ with } Z_0 = 50 \text{ \& } \Gamma = -j0.5 \Rightarrow$$

$$\Gamma(Z_L + Z_0) = Z_L - Z_0 \Rightarrow \Gamma Z_L - Z_L = -\Gamma Z_0 - Z_0 \Rightarrow$$


$$Z_L(\Gamma - 1) = -Z_0(\Gamma + 1) \Rightarrow Z_L = Z_0 \frac{\Gamma + 1}{1 - \Gamma} \Rightarrow$$

$$Z_L = 50 \frac{-0.5j + 1}{1 + 0.5j} = 30 - j40$$

c) To answer the part a) it takes a little explanation. Consider

Fig. 1 which shows the original TL terminated on Z_L &

Fig. 2 which shows the same TL but extended by length l_m & terminated on R_m

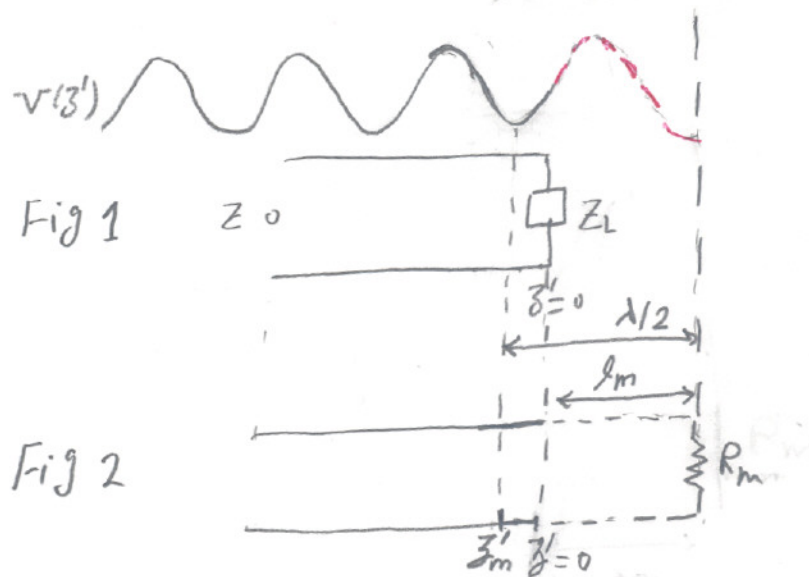

* Note the following about the figures 1 & 2.

1) Neither a voltage maximum nor minimum appears at $z'=0$, 5

Since Z_L is arbitrary (here we found out it was $Z_L = 30 - j40$)

2) By extending the TL with length l_m & terminating it on a purely resistive load, we have ensured that either a maximum or minimum will appear at R_m , [see class notes Pages 55-57].
In fact, since $R_L = 30 < R_0 = 50$ we will have a minimum at R_m as discussed in lecture notes.

3) The lossless line of length l_m & terminated with R_m must be chosen such that impedance at $z'=0$ & looking to right should be equal to our original Z_L .

4) The impedance at $z'=0$, looking to right can be calculated from

$$Z_i = R_0 \frac{R_m + jR_0 \tan(\beta l_m)}{R_0 + jR_m \tan(\beta l_m)} \quad (1)$$

E9(1) is the input impedance at $z'=0$ (looking to right) for a lossless line with characteristic impedance of R_0 terminated with R_m .

5) The problem [Part (c)] asks us to find l_m & R_m such that the impedance of E9(1) is the same as Z_L . We found out that $Z_L = 30 - j40$,

therefore we must solve the following E9.

$$30 - j40 = 50 \frac{R_m + j50 \tan(5\pi l_m)}{50 + jR_m \tan(5\pi l_m)} \quad (2)$$

E9 (2-P5) Can be solved for R_m & l_m since there are two equations & two unknowns. 6

6) There is an easier way to find l_m & R_m from Fig 5.12 Page 4, note that $z'_m + l_m = \lambda/2$. Here we know $z'_m = 0.05 - j$ & $\frac{\lambda}{2} = 0.2$ meter $\Rightarrow l_m = 0.2 - 0.05 = 0.15$. Also from example

9-8 of Cheng (Page 463), with $R_L < R_0$ we found that

$$R_L = \frac{R_0}{S} \Rightarrow R_m = \frac{R_0}{S} \Rightarrow R_m = \frac{50}{3} = 16.7 \Omega.$$

7) make sure you study Example 9-8 of Cheng, Page 463.

8) Note that for any load impedance $\sqrt{\frac{Z_L}{E_9(1-P5)}}$ can be used to find l_m & R_m such that load impedance Z_L can be replaced with a lossless line terminated on R_m , without disturbing the wave forms to the left of $z' = 0$.

Q: A lossless TL has capacitance of 200 [pF/m] & 7
 inductance of 0.5 [nH/m] . It is excited with sinusoidal source
 of frequency 1 [kHz] . The magnitude of the voltage measured
 across a $35 \text{ [}\Omega\text{]}$ load is 100 [V] . Find the following:-

- The line characteristic impedance R_0 .
- The voltage reflection coefficient at load Γ
- The phase velocity, V_p
- The wavelength, λ .
- The forward & backward traveling waves amplitude, V_0^+ , V_0^-
- The line propagation constant β .

Sol: $C = 200 \times 10^{-12} \text{ [F/m]}$

$L = 0.5 \times 10^{-6} \text{ [H/m]}$

$f = 1 \times 10^3 \text{ [Hz]}$

$R_L = 35 \text{ [}\Omega\text{]}$

$|V(z'=0)| = |V(z=l)| = V_L = 100 \text{ [V]}$

a) For lossless line $R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.5 \times 10^{-6}}{200 \times 10^{-12}}} = 50 \text{ [}\Omega\text{]}$

b) $\Gamma = \frac{R_L - R_0}{R_0 + R_L} = \frac{35 - 50}{35 + 50} = -0.1765$

c) $V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 10^{-6} \times 200 \times 10^{-12}}} = 1 \times 10^8 = 0.33 c \text{ [m/s]}$
 ↑ speed of light in vacuum

$$d) \lambda = \frac{V_p}{f} = \frac{1 \times 10^8}{1 \times 10^3} = 10^5 \text{ [m]} \quad \textcircled{1} \text{ Let this is } 1/\lambda \text{ of the operating wave length} \quad \underline{\underline{8}}$$

$$e) \text{ Recall } \textcircled{2} \quad V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \\ = V_0^+ e^{-j\beta z} \left[1 + \frac{V_0^- e^{j\beta z}}{V_0^+ e^{-j\beta z}} \right]$$

at load $z=l$ we have $\textcircled{3}$

$$\textcircled{4} \quad V(z=l) = V_L = V_0^+ e^{-j\beta l} \left[1 + \frac{V_0^- e^{j\beta l}}{V_0^+ e^{-j\beta l}} \right] = V_0^+ e^{-j\beta l} [1 + \Gamma]$$

$$\text{where } \Gamma = \Gamma_L = \frac{V_0^- e^{j\beta l}}{V_0^+ e^{-j\beta l}} \quad \textcircled{5}$$

$$(4) \Rightarrow \textcircled{6} \quad |V_L| = |V_0^+| |1 + \Gamma| \Rightarrow$$

$$\textcircled{7} \quad |V_0^+| = \frac{|V_L|}{|1 + \Gamma|} = \frac{100}{|1 - 0.176j|} \Rightarrow |V_0^+| = 121.4286 \text{ Volt}$$

$$\text{Similarly from (2) we have } V_L = V_0^- e^{j\beta l} \left[1 + \frac{V_0^+ e^{-j\beta l}}{V_0^- e^{j\beta l}} \right] \\ = V_0^- e^{j\beta l} \left[1 + \frac{1}{\Gamma} \right] \\ = V_0^- e^{j\beta l} \left[\frac{\Gamma + 1}{\Gamma} \right] \Rightarrow$$

$$|V_L| = |V_0^-| \left| \frac{\Gamma + 1}{\Gamma} \right| \Rightarrow |V_0^-| = \left| \frac{\Gamma}{\Gamma + 1} \right| |V_L| = \left| \frac{-0.176j}{1 - 0.176j} \right| \times 100 \Rightarrow$$


$$|V_0^-| = 21.4286 \text{ [VOLT]}$$

$$c) \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{10^5} = 6.2832 \times 10^{-5} \text{ [rad/m]}$$

Q: A Transmission line of characteristic impedance $R_0 = 50 [\Omega]$ is to be matched to a load impedance $Z_L = 40 + j10 [\Omega]$ through a length l' of another transmission line of characteristic impedance R_0' . What are the required l' & R_0' for matching.

9

Sol:

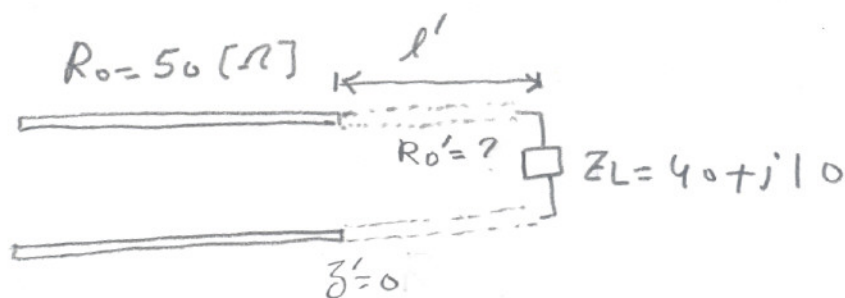

We calculate the input impedance seen at $z' = 0$ & looking to the right (toward the load Z_L). To have match condition this input impedance must be made equal to the original line impedance, i.e. $R_0 = 50 \Omega$.

$$\textcircled{1} \quad Z_i = R_0' \frac{Z_L + j R_0' \tan(\beta l')}{R_0' + j Z_L \tan(\beta l')} \quad \text{let } \tan \beta l' = T$$

↑
input at
 $z' = 0$ &
to the right

$$\textcircled{2} \quad Z_i = R_0' \frac{Z_L + j R_0' T}{R_0' + j Z_L T}$$

Now as stated earlier to have matched condition we must equate $Z_i = 50$, which is the original line impedance - substituting values for Z_i & Z_L we have

$$50 = R_o' \frac{(40 + 10j) + j R_o' T}{R_o' + j(40 + 10j)T} \Rightarrow$$

$$50 \{ R_o' + (40j - 10)T \} = 40 R_o' + j(10 R_o' + R_o'^2 T)$$

$$50 R_o' - 500T + j2000T = 40 R_o' + j R_o' (10 + R_o' T) \Rightarrow$$

$$50 R_o' - 500T = 40 R_o' \Rightarrow \boxed{50 R_o' = 40 R_o' + 500T} \quad (1)$$

$$2000T = 10 R_o' + (R_o')^2 T \Rightarrow \boxed{-(R_o')^2 T = 10 R_o' - 2000T} \quad (2)$$

Solve (1) & (2) for R_o' & T & we have

$$(3) \quad R_o' = 38.7 \text{ \& } T = \tan(\beta l') = 0.775 \Rightarrow$$

$$\tan\left(\frac{2\pi}{\lambda} l'\right) = 0.775 \Rightarrow \boxed{l' = 0.105 \lambda}$$

Q: A generator with an open ckt voltage $V_g = 10 \cos 8000\pi t$ [V] & internal impedance of $Z_g = 40 + j30$ is connected to a $50 [\Omega]$ distortionless line. The line has a resistance of $0.5 [\Omega/m]$ & its lossy dielectric medium has a loss tangent of 0.18% . The line is 50 (m) long & is terminated in a matched load. Find (a) the instantaneous expressions for the voltage & current at an arbitrary location on the line (b) the instantaneous expressions for the voltage & current at the load (c) the average power transmitted to the load

Sol: Let us write down the information given

$$V_g = 10 \angle 0, \omega = 8000\pi, Z_g = 40 + j30, R = 0.5 [\Omega/m]$$

$$\textcircled{1} \tan \delta_c = \frac{\epsilon''}{\epsilon'} = 0.0018, Z_0 = R_0 = 50, Z_L = R_0 = 50 \text{ (matched condition)}$$

$$l = 50 \text{ (m)}, \text{ \& since this is a distortionless line } \frac{R}{L} = \frac{G}{C}.$$

$$\text{For line that is matched } \textcircled{3} V(z) = V_i e^{-\gamma z} \text{ \& } \textcircled{4} I(z) = I_i e^{-\gamma z}$$

We need to calculate $\textcircled{5} \gamma = \alpha + j\beta$. For distortionless line

$$\textcircled{6} \alpha = R \sqrt{\frac{C}{L}} \quad \textcircled{7} \beta = \omega \sqrt{LC} \quad \text{To Find } \alpha \text{ \& } \beta$$

We need to know G \& L

From Eq. for loss tan $\textcircled{1} \tan \delta_c = \frac{\epsilon''}{\epsilon'} \approx \frac{\sigma}{\omega \epsilon}$ (See cheng Eq 7-111) 12

Also recall that in previous HW ^{Set 123 Prob 5} we showed that $\textcircled{2} \frac{\sigma}{\epsilon} = \frac{G}{C}$ & since for distortionless line $\textcircled{3} \frac{G}{C} = \frac{R}{L}$ we can

write $\textcircled{4} \tan \delta_c = 0.0018 = \frac{\epsilon''}{\epsilon'} \approx \frac{\sigma}{\omega \epsilon} = \frac{G}{\omega C} = \frac{1}{\omega} \frac{R}{L} \Rightarrow$

$$L = \frac{R}{\omega \tan \delta_c} = \frac{0.5}{8000\pi \times 0.0018} = 0.0111 \text{ [H/m]}$$

x for distortionless line $R_0 = \sqrt{\frac{L}{C}} \Rightarrow C = \frac{L}{R_0^2} = \frac{0.0111}{(50)^2} \Rightarrow$
 $C = 4.4210 \times 10^{-6} = 4.4210 \text{ [nF/m]}$

then from (6-P11) $\alpha = R \sqrt{\frac{C}{L}} = 0.5 \sqrt{\frac{4.421 \times 10^{-6}}{0.0111}} \Rightarrow$


$$\alpha = 0.01 \text{ [NP/m]}$$

From (7-P11)

$$\beta = \omega \sqrt{LC} = 8000\pi \sqrt{0.0111 \times 4.421 \times 10^{-6}} = 5.5556 \text{ [rad/m]}$$

x From Eq 5 (3-LP11) $V(z) = V_i e^{-\gamma z}$ we also need to know

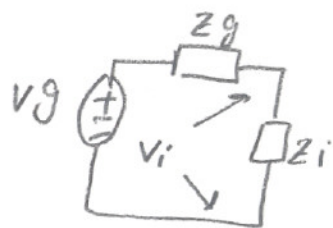V_i . Recall that V_i can be calculated from voltage divider



$$V_i = V_g \frac{Z_i}{Z_i + Z_g}$$

& for matched line $Z_i = Z_0$ & here $Z_0 = R_0 \Rightarrow$

$$Z_i = Z_0 = R_0 = 50 \Rightarrow$$

$$Z_i = Z_0 = R_0 = 50 \text{ &}$$

$$Z_g = 40 + j30$$

$$V_i = \frac{10 \angle 0^\circ \times 50}{50 + 40 + j30} \Rightarrow$$

$$V_i = \frac{10 \frac{500 \angle 0}{90 + j30}}{9 + j3} = \frac{50 \angle 0}{9.4868 \angle 0.3218} \Rightarrow \underline{5.2705 \angle -0.3218} = \underline{13}$$

① $V_i = 5.2705 \angle -0.3218$ then from (3-P11) we have

$$V(z) = V_i \cdot e^{-\gamma z} = V_i \cdot e^{-\alpha z} e^{-j\beta z} = 5.2705 e^{-0.01z} e^{-j5.5556z}$$

$$V(z) = 5.2705 \angle -0.3218 e^{-0.01z} e^{-j5.5556z}$$

$$= 5.2705 e^{-0.01z} e^{-j(5.5556z + 0.3218)} \Rightarrow$$

$$v(z,t) = \text{Re}[V(z)e^{j\omega t}] = \text{Re}\left[5.2705 e^{-0.01z} e^{j[8000\pi t - 5.5556z - 0.3218]}\right]$$

$$v(z,t) = 5.2705 e^{-0.01z} \cos(8000\pi t - 5.5556z - 0.3218) \quad \text{①}$$

For $I(z) = I_i e^{-\gamma z}$ we note that $I_i = \frac{V_i}{Z_g + Z_i} = \frac{Z_i}{Z_i + Z_g} \frac{V_g}{Z_i}$

$$= \frac{V_i}{Z_i} = \frac{V_i}{Z_0} \text{ since for matched lines } Z_i = Z_0$$

then

$$I(z) = \frac{V_i \cdot e^{-\gamma z}}{Z_0} \Rightarrow$$

$$I(z) = 0.1054 e^{-0.01z} \cos(8000\pi t - 5.5556z - 0.3218)$$

b) at load $z = 50 \Rightarrow$

$$v_L = v(z=50, t) = 5.2705 e^{-0.01 \times 50} \cos(8000\pi t - 5.5556 \times 50 - 0.3218)$$

$$= 3.2 \cos(8000\pi t - 278.102)$$

$$i_L = i(z=50, t) = 0.064 \cos(8000\pi t - 278.102)$$

$$c) P_{ave} = \frac{1}{2} \operatorname{Re}[V I^*]$$

$$= \frac{1}{2} \operatorname{Re} \left[5.2705 e^{-0.01 \times 50} e^{-j(5.5556 \times 50 + 0.3218)} \times 0.1054 e^{-0.01 \times 50} e^{+j(5.5556 \times 50 + 0.3218)} \right]$$

$$= \frac{1}{2} 5.2705 \times 0.1054 \times e^{-2 \times 0.01 \times 50}$$

$$= 0.102 \text{ Watt}$$

Q: A 2 [m] lossless air-spaced transmission line having a characteristic impedance $50 [\Omega]$ is terminated with an impedance $40 + j30 [\Omega]$. At an operating frequency of $200 [\text{MHz}]$, the phase velocity in the line is the same as speed of light in vacuum (c). What is the line input impedance

$$\text{Sol: } l = 2 [\text{m}], \quad Z_0 = R_0 = 50 [\Omega] \text{ lossless}, \quad Z_L = 40 + j30$$

$$f = 200 \times 10^6 [\text{Hz}], \quad V_p = c = 3 \times 10^8$$

$$Z_i = R_i + jX_i = R_0 \frac{Z_L + jR_0 \tan(\beta l)}{R_0 + jZ_L \tan(\beta l)}$$

$$V_p = \frac{\omega}{\beta} \Rightarrow \beta = \frac{\omega}{V_p} = \frac{\omega}{c} = \frac{2\pi \times 200 \times 10^6}{3 \times 10^8} = 4.189 [\text{rad/m}]$$

$$\beta l = 4.189 \times 2 = 8.378 = 480^\circ$$

$$Z_i = 50 \frac{(40 + j30) + j50 \tan(8.378)}{50 + j(40 + j30) \tan(8.378)} \Rightarrow$$

15

$$Z_i = 26.32 - j9.87$$

Q. A sinusoidal voltage generator with $V_g = 0.1 \angle 0^\circ$ [V] & internal impedance $Z_g = R_g$ is connected to a lossless transmission line having a characteristic impedance $R_0 = 50 [\Omega]$. The line is 1 meter long & is terminated in a load resistance $R_L = 25 [\Omega]$. Find a) V_i , I_i , V_L & I_L in terms of the line length (l).
b) The standing-wave ratio on the line & c) the average power delivered to the load.

Sol: $V_g = 0.1 \angle 0^\circ$; $Z_g = R_g = R_0 = 50$, line is lossless & is matched to the generator. ($Z_L = R_L = 25$ (the line is not matched to the load))

a) For a lossless line $Z_i = R_0 \frac{R_L + jR_0 \tan(\beta l)}{R_0 + jR_L \tan(\beta l)}$
with $R_0 = 50$, $R_L = 25 \Rightarrow$

$$Z_i = 50 \frac{1 + 2j \tan(\beta l)}{2 + j \tan(\beta l)}$$

* Furthermore at load $\beta' = 0 \Rightarrow \beta = 1$, then (2-P16) $\Rightarrow$

17

$$V_L = V(\beta' = 0) = \frac{R_o V_g}{R_o + R_g} e^{-j\beta l} (1 + \Gamma_L) \Rightarrow$$

$$V_L = \frac{50 \times 0.1}{50 + 50} e^{-j\beta l} \left(1 - \frac{1}{3}\right) = \frac{1}{30} e^{-j\beta l}$$

$$I_L = \frac{V_g}{R_o + R_o} e^{-j\beta l} (1 - \Gamma_L) = \frac{0.1}{100} e^{-j\beta l} \left(1 + \frac{1}{3}\right) = \frac{4}{3000} e^{-j\beta l} [A]$$

$$\text{or } I_L = 1000 \frac{4}{3000} e^{-j\beta l} = \frac{4}{3} e^{-j\beta l} [mA]$$

$$b) S' = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1/3}{1 - 1/3} = 2$$

$$c) (P_{\text{load}})_{\text{time averaged}} = \frac{1}{2} \text{Re}[V_L I_L^*] = \frac{1}{2} \text{Re}\left[\frac{1}{30} \times \frac{4}{3000}\right]$$

$$= \frac{2}{90000} = 2.22 \times 10^{-5} [\text{Watt}]$$