

# HW 4

Q: Let  $Z_L = 60 + j43 [\Omega]$  &  $Z_0 = 50 [\Omega]$ . Find the input impedance with  $l = 0.32 [m]$  & line wavelength of  $\lambda = 0.854 [m]$ .

Sol: we first calculate the normalized load impedance

$$Z_L = \frac{Z_L}{Z_0} = \frac{60 + j43}{50} = 1.2 + j0.86 = r + jx$$

locate  $Z_L = 1.2 + j0.86$  on the chart, this is point ① on the figure.

\* To find the input impedance a distance  $l = 0.32$ , we first evaluate


$$\frac{\Delta Z'}{\lambda} = \frac{l}{\lambda} = \frac{0.32}{0.854} = 0.375$$

\* Join ① to Perimeter via line ①-②. Read the value for  $\frac{l}{\lambda}$  at ② which is  $\approx 0.172$ . Now move from ② toward the generator a distance equal to  $0.375$ . In other words you need to locate a point for which we have  $0.172 + 0.375 = 0.547$ . This means we go around the Perimeter, come to  $\frac{Z'}{\lambda} = 0.5$  (this is  $P_{sc}$ ) & go further by an amount  $= 0.547 - 0.5 = 0.047$ . This point is marked

③.

\* Draw a line from ③ to center. This line intersects the original circle at ④. The  $r$  &  $x$  for point ④ are given by
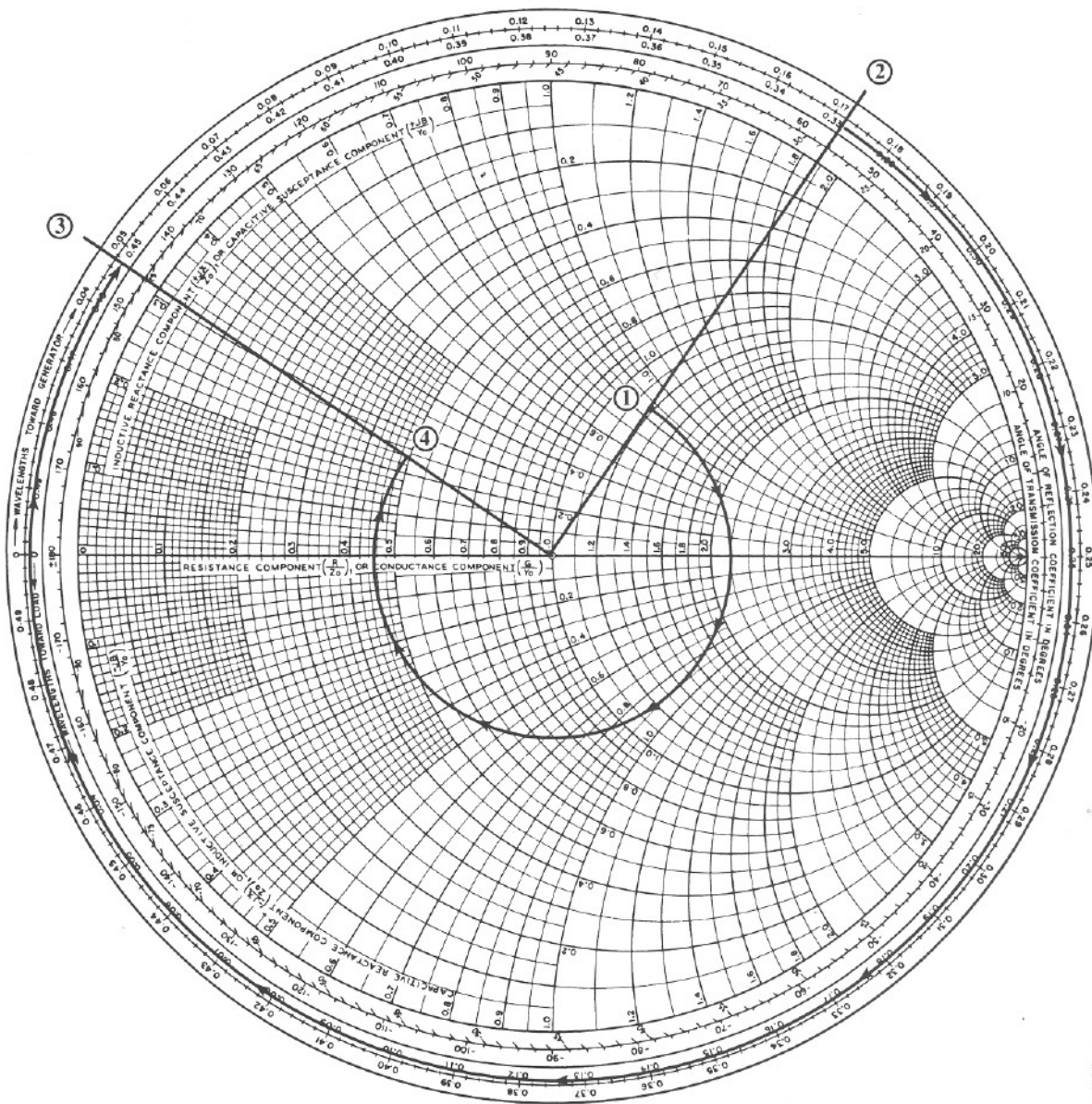
$$Z_i = 0.5 + j0.25 \Rightarrow Z_i = 50 Z_i = 25 + j12.5 [\Omega]$$




Q: The inductance & capacitance of a lossless  $50[\Omega]$  line are  $0.251 [\mu\text{H}/\text{m}]$  &  $99.5 [\text{pF}/\text{m}]$ . The line is attached to a source of  $10 \cos(2\pi \times 10^6 t)$  with internal impedance of  $1 [\Omega]$ . The length of the line is 5 meter & the is terminated on a load resistance of  $50[\Omega]$ . a) What are the instantaneous voltage & current at any point b) what is the power delivered to the load


Sol:  $Z_0 = R_0 = 50$ ,  $L = 0.251 \times 10^{-6} [\text{H}/\text{m}]$ ,  $C = 99.5 \times 10^{-12} [\text{F}/\text{m}]$ ,  
 $\omega = 2\pi \times 10^6$ ,  $Z_g = R_g = 1$ ,  $l = 5$ ,  $Z_L = R_L = 50$ ,  $V_g = 10 \angle 0$

\* since the line is match there is no reflected wave & the voltage & current (in phasor form) are given by

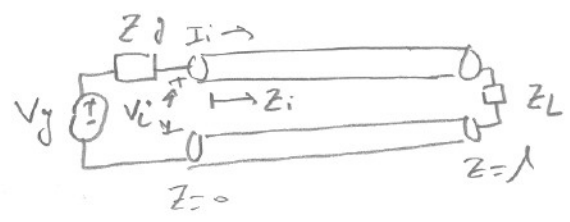①  $V(z) = V_i e^{-j\beta z}$   
 ②  $I(z) = I_i e^{-j\beta z}$



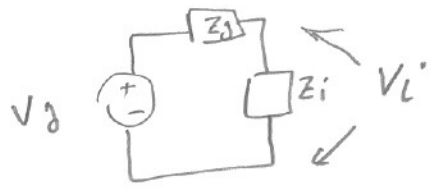\* To find  $V(z)$  &  $I(z)$  we need to find  $I_i$  &  $V_i$ . These are given by Eq (3.14),



but what is  $Z_i$ . For matched line  $Z_i = Z_0$  since

③  $V_i = V_g \frac{Z_i}{Z_i + Z_g} = 10$

④  $I_i = \frac{V_g}{Z_g + Z_i}$

⑤  $Z_i = R_0 \frac{Z_L + jR_0 \tan(\beta l)}{R_0 + jZ_L \tan(\beta l)} = R_0 \frac{R_0 + jR_0 \tan(\beta l)}{R_0 + jR_0 \tan(\beta l)} = R_0 = Z_0$

\* Then ①  $V_i = V_g \frac{Z_0}{Z_0 + Z_g} = 10 \frac{50}{50 + 1} = 9.8039 \angle 0$

4

②  $I_i = \frac{V_g}{Z_g + Z_0} = \frac{10}{1 + 50} = 0.1961 \angle 0$

\*  $\beta$  can be found from ③  $\beta = \frac{\omega}{V_p}$  & ④  $V_p = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.251 \times 10^{-6} \times 99.5 \times 10^{-12}}}$

⑤  $V_p = 2 \times 10^8 \text{ [m/s]}$  &  $\beta = \frac{2\pi \times 10^6}{2 \times 10^8} = 0.01 \pi$

\* We now have enough information to write  $V(z)$  &  $I(z)$

⑥  $V(z) = 9.8039 e^{-j0.01\pi z}$

⑦  $I(z) = 0.1961 e^{-j0.01\pi z} \Rightarrow$

$v(z,t) = \text{Re}[V(z)e^{j\omega t}] = 9.8039 \cos(\omega t - 0.01\pi z)$

$i(z,t) = \text{Re}[I(z)e^{j\omega t}] = 0.1961 \cos(\omega t - 0.01\pi z)$

b) For a lossless line terminated on a match Power delivered to the load is the same as power input to the line

$(P_{\text{ave}})_L = (P_{\text{ave}})_i = \frac{1}{2} \text{Re}[V_i \cdot I_i^*] = \frac{1}{2} 9.8039 \times 0.1961$   
 $= 0.9613 \text{ [watt]}$

time averaged

Q: let  $P_i$  be the incident <sup>time averaged</sup> power approaching a point on a lossless 5 line,  $P_r$  the time averaged reflected power on the line, and  $P_t$  the time averaged transmitted power available to do work on the load. You can think of the  $P_t$  as a useful power since, for example, it can be radiated by an antenna connected to the line. Show the following is true  $P_t = P_i - P_r = \frac{|V_o^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = P_L (1 - |\Gamma_L|^2)$

Sol: The voltage & current on line are given by (lossless case)

$$\textcircled{1} V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z}$$

$$\textcircled{2} I(z) = I_o^+ e^{-j\beta z} + I_o^- e^{j\beta z} = \frac{V_o^+}{Z_0} e^{-j\beta z} - \frac{V_o^-}{Z_0} e^{j\beta z}$$

or equivalently

$$\textcircled{3} V(z) = V_o^+ e^{-j\beta z} \left[ 1 + \frac{V_o^- e^{j\beta z}}{V_o^+ e^{-j\beta z}} \right]$$

$$\textcircled{4} I(z) = \frac{V_o^+}{Z_0} e^{-j\beta z} \left[ 1 - \frac{V_o^- e^{j\beta z}}{V_o^+ e^{-j\beta z}} \right]$$

since  $z + z' = l \Rightarrow z = l - z'$  we can write (3) & (4) as-

$$\textcircled{5} V(z) = V_o^+ e^{-j\beta z} \left[ 1 + \frac{V_o^- e^{j\beta l} e^{-j\beta z'}}{V_o^+ e^{-j\beta l} e^{j\beta z'}} \right]$$

$$\textcircled{6} \text{ Recall } F(z) = \frac{V_o^- e^{j\beta z}}{V_o^+ e^{-j\beta z}} \quad \textcircled{7} \Gamma(z=l) = \Gamma_L = \frac{V_o^- e^{j\beta l}}{V_o^+ e^{-j\beta l}}$$

then (5)  $\Rightarrow$

$$\textcircled{7} V(z) = V_o^+ e^{-j\beta z} \left[ 1 + \Gamma_L e^{-2j\beta z'} \right] \quad \&$$

similarly

$$\textcircled{8} I(z) = \frac{V_o^+}{Z_0} e^{-j\beta z} \left[ 1 - \Gamma_L e^{-2j\beta z'} \right]$$

Now the time averaged power transmitted at any point is

6

$$\begin{aligned} \textcircled{1} P_t &= \frac{1}{2} \operatorname{Re} [V(z) I^*(z)] \\ &= \frac{1}{2} \operatorname{Re} \left[ V_0^+ e^{-j\beta z} (1 + \Gamma e^{-2j\beta z'}) \cdot \frac{(V_0^+)^*}{Z_0^*} e^{j\beta z} [1 - \Gamma^* e^{2j\beta z'}] \right] \\ &= \frac{1}{2} \operatorname{Re} \left[ \frac{|V_0^+|^2}{Z_0^*} (1 - \Gamma^* e^{2j\beta z'} + \Gamma e^{-2j\beta z'} - |\Gamma|^2) \right] \end{aligned}$$

\* Recall  $\textcircled{2} V_0^+ \cdot (V_0^+)^* = |V_0^+|^2$  &  $\textcircled{3} \Gamma \Gamma^* = |\Gamma|^2$

$$\textcircled{4} P_t = \frac{1}{2} \operatorname{Re} \left[ \frac{|V_0^+|^2}{Z_0} (1 + \Gamma e^{-2j\beta z'} - (\Gamma e^{-2j\beta z'})^* - |\Gamma|^2) \right]$$

since  $\textcircled{5} Z_0 = Z_0^*$  because the line is lossless.

but  $\textcircled{6} \Gamma e^{-2j\beta z'} - (\Gamma e^{-2j\beta z'})^* = j 2 \operatorname{Im} [\Gamma e^{-2j\beta z'}]$

then

$$\textcircled{7} P_t = \frac{1}{2} \operatorname{Re} \left[ \frac{|V_0^+|^2}{Z_0} (1 + j 2 \operatorname{Im} [\Gamma e^{-2j\beta z'}] - |\Gamma|^2) \right]$$

$$\textcircled{8} P_t = \frac{1}{2} \left[ \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2) \right] = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2)$$

\* We can think of  $\frac{|V_0^+|^2}{2Z_0}$  as the power incident &  $\frac{|V_0^+|^2}{2Z_0} |\Gamma|^2$  as the power reflected then

$$P_t = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2) = P_i - P_r = P_i (1 - |\Gamma|^2)$$

So to have maximum power available for work we should minimize  $|\Gamma|^2 \Rightarrow \Gamma = 0 \Rightarrow S = 1$  (matched condition)

Q: The capacitance of a 0.6 [m] long lossless line measured at 100 [kHz] was 54 [pF] & its inductance was equal to 0.3 [μH]. 7

- Determine  $Z_0$
- Calculate  $X_{io}$  &  $X_{is}$  (open & short ckt impedance) at 10 MHz.
- Can you find out the value of the dielectric constant of the cable insulating medium

Sol: a)  $C' = \frac{54 \times 10^{-12}}{0.6} = 9 \times 10^{-11} \text{ [F/m]}$

$L = \frac{0.3 \times 10^{-6}}{0.6} = 5 \times 10^{-7} \text{ [H/m]}$

$Z_0 = R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{5 \times 10^{-7}}{9 \times 10^{-11}}} = 74.54 \text{ [Ω]}$

b)  $Z_{io} = jX_{io} = -j R_0 \cot \beta l$  ;  $\beta = \omega \sqrt{LC} = 2\pi \times 10^7 \sqrt{\frac{0.3 \times 10^{-6}}{0.6} \times \frac{54 \times 10^{-12}}{0.6}}$

$Z_{io} = jX_{io} = -j 74.54 \cot \beta (0.4215 \times 0.6)$   $\beta = 0.4215$

$= -j 288.42$

$Z_{is} = j R_0 \tan(\beta l) = j 74.54 \tan(0.4215 \times 0.6) = j 19.26$

c) To do this part we need a piece of information that although we did not cover in class, yet it is very useful.

$\mu \epsilon = LC' \Rightarrow \mu_r \mu_0 \epsilon_r \epsilon_0 = LC' \Rightarrow$  since  $\mu_r = 1$  &

$\epsilon_r = \frac{LC'}{\mu_0 c^2} = \frac{9 \times 10^{-11} \times 5 \times 10^{-7}}{(3 \times 10^8)^2} = 4.05$

↑  
speed of light in vacuum

$c = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$   
↑  
speed of light in vacuum

Q: The characteristic impedance of a given lossless transmission line 8 is  $75 \Omega$ . Use a Smith chart to find the impedance & admittance at  $200 \text{ MHz}$  of such line that is (a)  $1 \text{ m}$  long & open circuited, and (b)  $0.8 \text{ m}$  long & short circuited.

Sol:  $R_0 = 75$

$$a) \quad l = 1 \quad \lambda = \frac{c}{v} = \frac{3 \times 10^8}{200 \times 10^6} = 1.5 \text{ m}$$

$$\frac{Z'}{Z} = \frac{1}{1.5} = 0.667.$$

Since open ckt, enter the chart at  $P_{oc}$  (the point on the extreme right). The value of  $\frac{Z'}{Z}$  here is  $0.25$ . To find input impedance move toward the generator an amount equal to  $0.667$  i.e. the total distance of  $0.25 + 0.667 = 0.917$ . To find this  $0.917$  on the Smith Chart Perimeter, marked as wavelength toward generator, note that you must start from  $\frac{Z'}{Z} = 0$  which is on the extreme left. Going around one time is equal to  $0.5$ , then  $0.917 - 0.5 = 0.417$ . Locate  $0.417$  on the wavelength toward generator. This is marked as  $P_1$ . Draw a line from  $P_1$  to  $O$  & continue to  $O P_1$  intersects the  $x$ -circles at  $x = 0.57$ . then  $Z_i = -j 0.57 \times 75 = -j 42.75$

The line  $O P_2$  intersects the  $x$ -circles at  $x = 1.75$  then

$$Z_i = j \frac{1.75}{75} \approx j 0.023$$



$$b) \rho = 0.8 \Rightarrow \frac{\Delta \Gamma'}{\Gamma} = \frac{0.8}{1.5} = 0.533$$

9

Enter the chart at  $P_{sc}$  (extreme left). Move toward generator a distance 0.533. This means going around one time & then another 0.033. ( $0.533 = 0.5 + 0.033$ ). This point is marked  $P_3$ .

Draw a line joining  $P_3$  to 0 & extend it to the other side (to  $P_4$ ).

Read the value of  $g$ -circle intersecting  $OP_3$  &  $r=0$  circle.

This the input impedance of the shorted line.



$$x = 0.21 \Rightarrow Z_i = jx R_0 = j 0.21 \times 75 = \boxed{j 15.75}$$

\*The value of admittance can be read from the intersection of  $OP_4$  with  $r=0$  circle &  $g$ -circles (diametrically across of

$$OP_3). \text{ This is } x = 4.7 \Rightarrow Y_i = -\frac{j 4.7}{75} = -j 0.063 \quad \boxed{\phantom{0.063}}$$

# IMPEDANCE OR ADMITTANCE COORDINATES

10

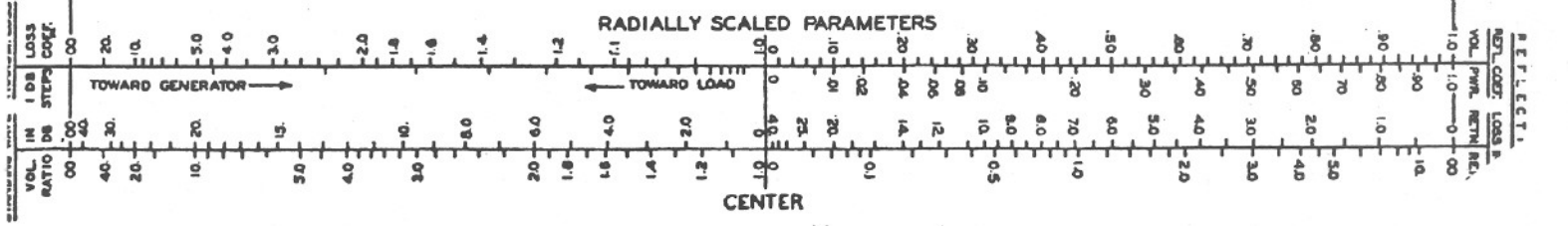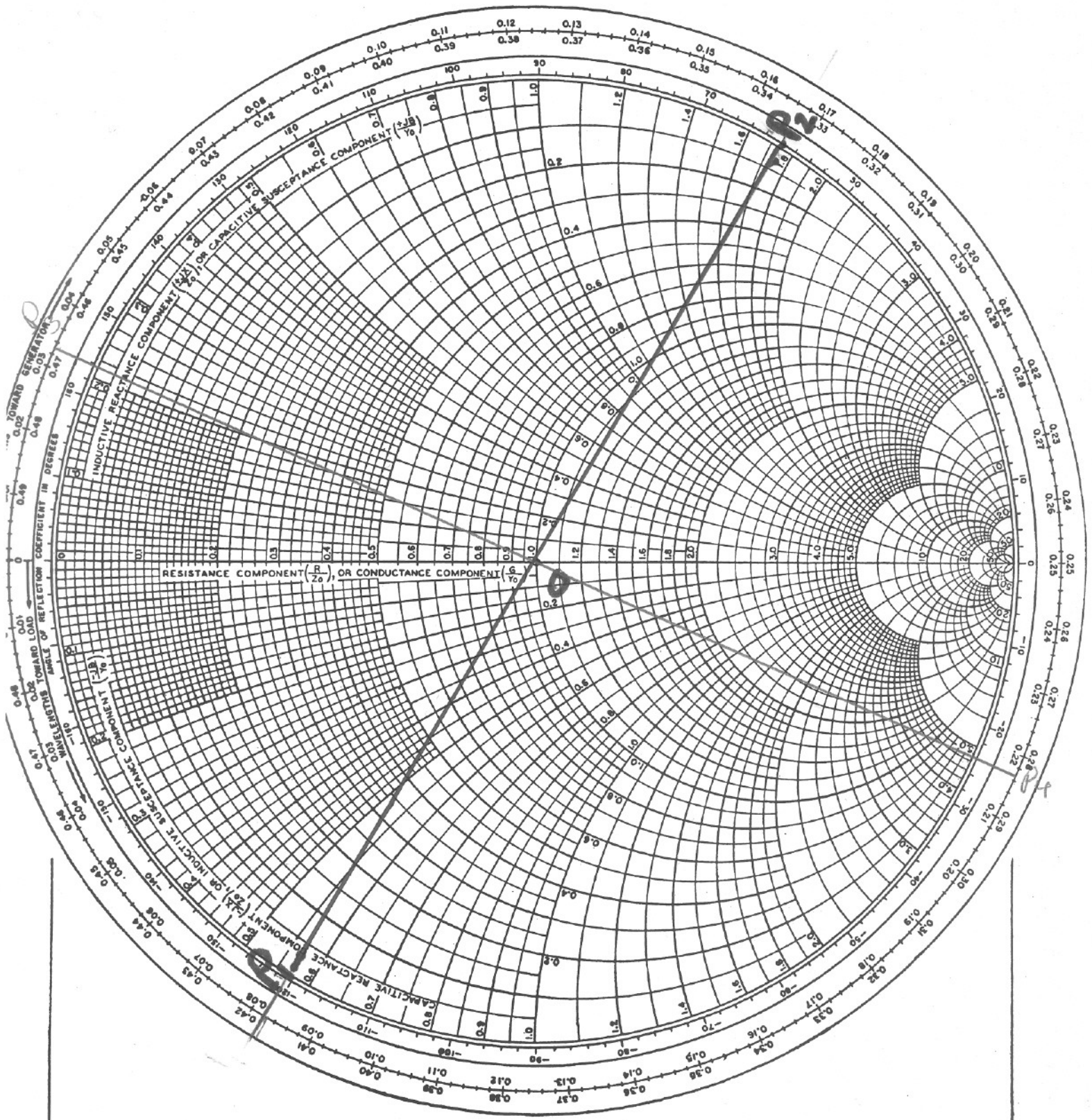

Q: a) Express  $V(z)$  &  $I(z)$  in terms of the load voltage ( $V_L$ ) & load current ( $I_L$ ) in exponential form & in hyperbolic form

b) Express  $V(z)$  &  $I(z)$  in terms of the Input voltage ( $V_i$ ) & Input current ( $I_i$ ) at the input end in exponential form & hyperbolic form.

Sol:


a) The point of this exercise is to show that starting with

$$\textcircled{1} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad \text{and} \quad \textcircled{2} I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

We express (1) & (2) in terms of  $V_L$  &  $I_L$  or  $V_i$  &  $I_i$ .

Note that since  $\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0$
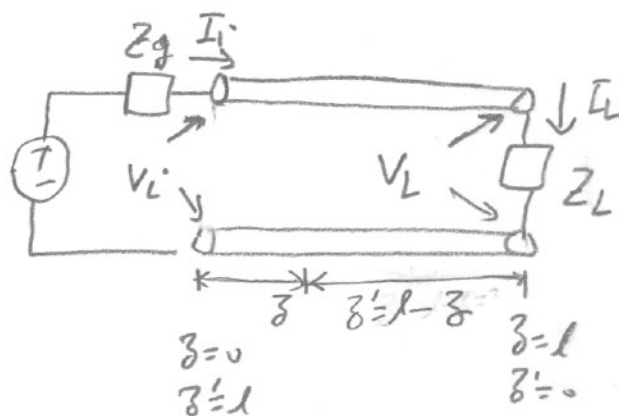
$$(2) \Rightarrow I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z}$$



+ The part (a) was done in class and we saw that

$$V(z') = \frac{I_L}{2} [(Z_L + Z_0) e^{\gamma z'} + (Z_L - Z_0) e^{-\gamma z'}]$$

$$I(z') = \frac{I_L}{2Z_0} [(Z_L + Z_0) e^{\gamma z'} - (Z_L - Z_0) e^{-\gamma z'}]$$

OR

$$V(z') = I_L (Z_L \cosh \gamma z' + Z_0 \sinh \gamma z')$$

$$I(z') = \frac{I_L}{Z_0} (Z_L \sinh \gamma z' + Z_0 \cosh \gamma z')$$

Plse check  
your notes pages  
37 - 38

b)

To express the  $V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$  & 1.2

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}$$

in terms of input voltage  $V_i$  & input current  $I_i$ , we note the

fact the  $V_i = V(z=0)$  &  $I_i = I(z=0)$  then

$$(5) \quad V_i = V_0^+ + V_0^-$$

$$(6) \quad I_i = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

Now (5) & (6) are two equations & 2 unknowns ( $V_0^+$  &  $V_0^-$ ) that can be solved for  $V_0^+$  &  $V_0^-$

$$(7) \quad V_i = V_0^+ + V_0^-$$

$$(8) \quad Z_0 I_i = V_0^+ - V_0^-$$

$$\Rightarrow (9) \quad \frac{Z_0 I_i + V_i}{2} = V_0^+ \text{ \& } \frac{V_i - Z_0 I_i}{2} = V_0^-$$

$$(10) \quad \frac{V_i - Z_0 I_i}{2} = V_0^-$$

Sub (9) & (10) in (1) & (2)

$$(11) \quad V(z) = \frac{1}{2} [Z_0 I_i + V_i] e^{-\gamma z} + \frac{1}{2} [V_i - Z_0 I_i] e^{\gamma z}$$

$$(12) \quad V(z) = -\frac{1}{2} Z_0 I_i (e^{\gamma z} - e^{-\gamma z}) + \frac{1}{2} V_i (e^{\gamma z} + e^{-\gamma z})$$

$$(13) \quad I(z) = \frac{1}{Z_0} e^{-\gamma z} \left[ \frac{Z_0 I_i + V_i}{2} \right] - \frac{e^{\gamma z}}{Z_0} \left[ \frac{V_i - Z_0 I_i}{2} \right]$$

$$(14) \quad I(z) = \frac{I_i}{2} [e^{\gamma z} + e^{-\gamma z}] - \frac{V_i}{2Z_0} [e^{\gamma z} - e^{-\gamma z}]$$

from (12-P9) & (14-P9) it is clear that we

can write

①

$$V(z) = V_i \cosh(\gamma z) - Z_0 I_i \sinh(\gamma z) \quad \&$$

②

$$I(z) = I_i \cosh(\gamma z) - \frac{V_i}{Z_0} \sinh(\gamma z)$$

Q: A d-c voltage  $V_0$  is applied at  $t=0$  to the input terminals of an open-circuited air-dielectric line of length  $l$  through a series resistance equal to  $R_0/2$ , where  $R_0$  is the characteristic resistance of the line. a) Draw the voltage reflection diagram b) sketch


$V(z=0, t)$  c) sketch  $V(l/2, t)$

Sol:

a)  $\Gamma_L = 1$ ,  $\Gamma_g = \frac{\frac{R_0}{2} - R_0}{\frac{R_0}{2} + R_0} = -\frac{1}{3}$ ,  $V_1^+ = V_0 \frac{R_0}{R_0 + \frac{R_0}{2}} = \frac{2}{3} V_0 = 0.67 V_0$

$V_L = V_1^+ \frac{1 + \Gamma_L}{1 - \Gamma_L \Gamma_g} = V_1^+ \frac{1 + 1}{1 + \frac{1}{3}} = \frac{3}{2} V_1^+ = \frac{3}{2} \cdot \frac{2}{3} V_0 = V_0$

Expected for an open ckt

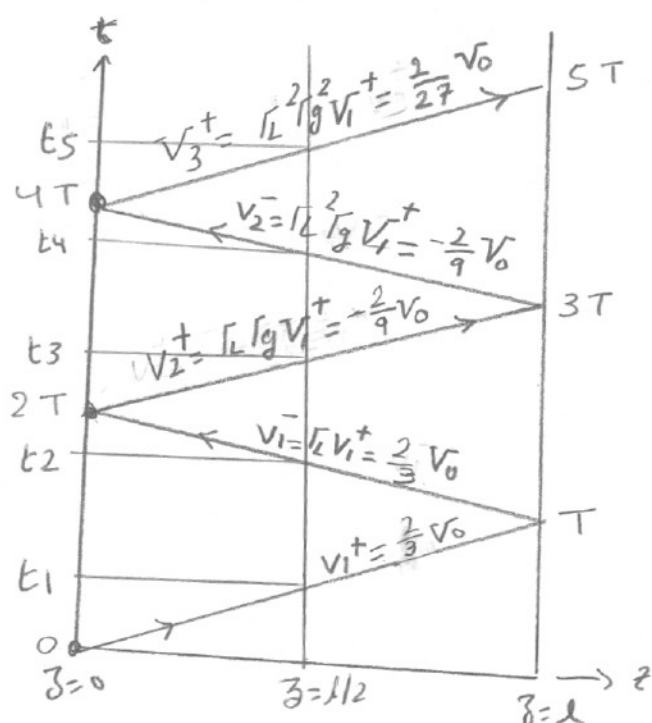


\* To find  $V(z=0, t)$  draw a vertical line at  $z=0$ . This intersects the directed lines at  $t=0$ ,  $t=2T$ ,  $t=4T$ , ..

\* The points  $0$ ,  $2T$ ,  $4T$ ,  $6T$  are important since new voltages appear on the line

b)

| Time interval    | voltage on the line                                                                                                                                  | Discontinuity                                                                     |
|------------------|------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------|
| $0 \leq t < 2T$  | $V_1^+ = \frac{2}{3} V_0$                                                                                                                            | $V_1^+ = \frac{2}{3} V_0$ at $t=0$                                                |
| $2T \leq t < 4T$ | $V_1^+ + V_1^- + V_2^+ = V_1^+ (1 + \Gamma_L + \Gamma_L \Gamma_g) = \frac{10}{9} V_0$                                                                | $V_1^+ (\Gamma_L + \Gamma_L \Gamma_g) = \frac{4}{9} V_0$ at $2T$                  |
| $4T \leq t < 6T$ | $V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ = V_1^+ (1 + \Gamma_L + \Gamma_L \Gamma_g + \Gamma_L^2 \Gamma_g + \Gamma_L^2 \Gamma_g^2) = \frac{26}{27} V_0$ | $V_1^+ (\Gamma_L^2 \Gamma_g + \Gamma_L^2 \Gamma_g^2) = -\frac{4}{27} V_0$ at $4T$ |

$$V(z=0, t)$$

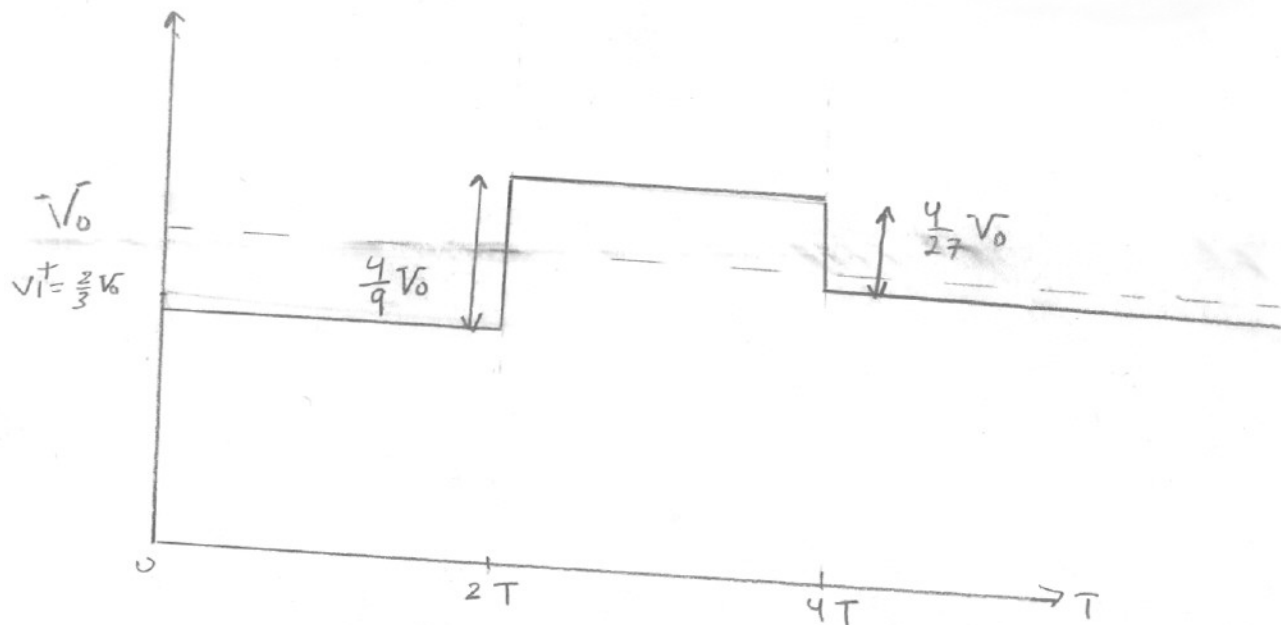

\* Note that Voltage goes above  $V_0$  for some time & drops below  $V_0$  at other time intervals, while it is approaching the value of  $V_L = V_0$

c) for  $V(z=1/2, t)$  we draw the line at  $z=1/2$  (shown in red)

The important time points are  $t_1, t_2, t_3, t_4, \dots$

| Time interval      | voltage on the line                                                                                              | Discontinuity                                          |
|--------------------|------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------|
| $0 < t < t_1$      | 0                                                                                                                | 0                                                      |
| $t_1 \leq t < t_2$ | $V_1^+ = \frac{2}{3}V_0$                                                                                         | $V_1^+ = \frac{2}{3}V_0$ at $t_1$                      |
| $t_2 \leq t < t_3$ | $V_1^+ + V_1^- = V_1^+(1 + \Gamma_L) = \frac{4}{3}V_0$                                                           | $V_1^+ \Gamma_L = \frac{2}{3}V_0$ at $t_2$             |
| $t_3 \leq t < t_4$ | $V_1^+ + V_1^- + V_2^+ = V_1^+(1 + \Gamma_L + \Gamma_L \Gamma_g) = \frac{10}{9}V_0$                              | $V_1^+ \Gamma_L \Gamma_g = -\frac{2}{9}V_0$ at $t_3$   |
| $t_4 \leq t < t_5$ | $V_1^+ + V_1^- + V_2^+ + V_2^- = V_1^+(1 + \Gamma_L + \Gamma_L \Gamma_g + \Gamma_L^2 \Gamma_g) = \frac{8}{9}V_0$ | $V_1^+ \Gamma_L^2 \Gamma_g = -\frac{2}{9}V_0$ at $t_4$ |

Note  $t_1 = \frac{1/2}{v}$ ,  $t_2 = 2T - t_1$ ,  $t_3 = 2T + t_1$ ,  $t_4 = 4T - t_1$ ,  $t_5 = 4T + t_1$

