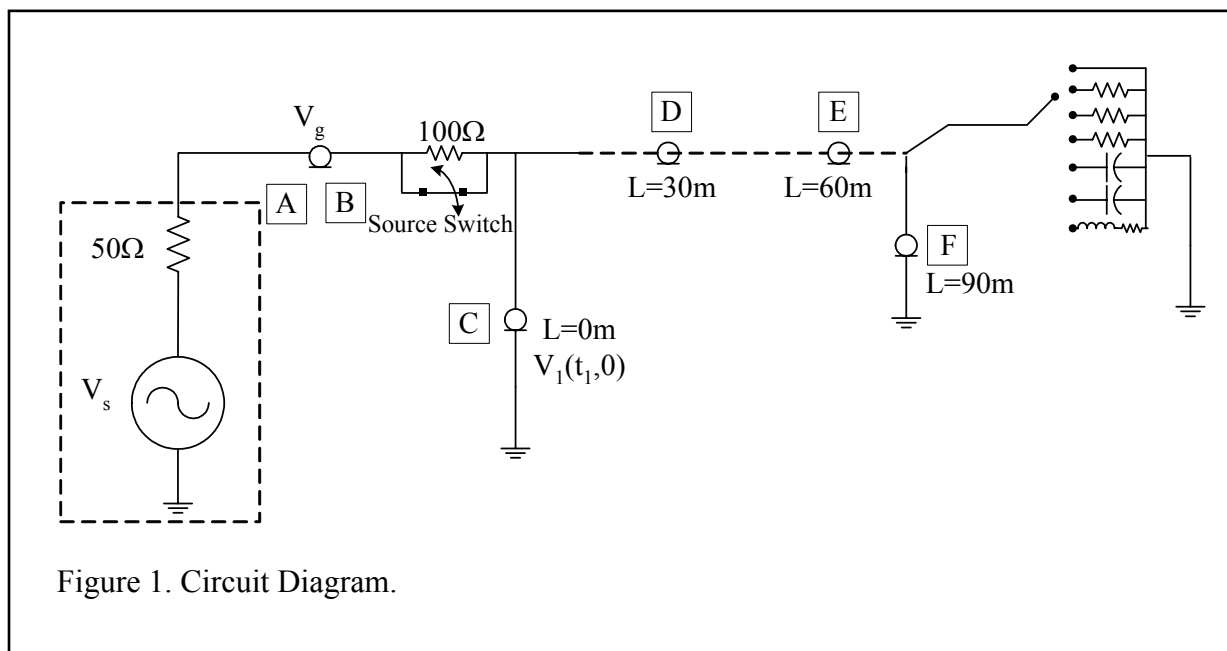


## ECE320F/ECE357S Waves on Transmission Lines - Laboratory Worksheet

**Section A:** Value of  $Z_o =$

**Section B:** Generator Voltage  $V_g =$   
 $V_I(t, 0) =$   
 $R_{series} =$   
 $Z_o =$

**Section C:** Refer to the figure below;



1. Plot  $V$  vs.  $t$  at  $C, D, E, F$  for  $R_L = 50\Omega$ .
2. Plot  $V$  vs.  $z$  for pertinent values of  $t$  (complete at home).

**Section D:** Complete the following table;

$z \text{ (m)}$	$t \text{ (s)}$	$v \text{ (m/s)}$
$C$		
$D$		
$E$		
$F$		

Average  $v =$

Dielectric Constant of the insulating medium ( $\epsilon$ ) =

$R_L (\Omega)$	$\Gamma_L(meas) = V_{reflect}/V_{incident}$	$\Gamma_L(calculated)$
0 $\Omega$		Complete at home
20 $\Omega$		Complete at home
100 $\Omega$		Complete at home
$\infty$		Complete at home

**Section E:** Complete the following table;

1. Plot  $V$  vs.  $t$  at  $C$  for  $R_L = 0 \Omega, 20 \Omega, 100 \Omega$  and  $\infty$
2. Plot  $V$  vs.  $t$  at  $F$  for  $R_L = 20 \Omega, 100 \Omega$  and  $\infty$
3. Plot  $V$  vs.  $t$  at  $C, D, E$ , and  $F$  for  $R_L = 20 \Omega$ .
4. Plot  $V$  vs.  $z$  for pertinent values of  $t$  for  $R_L = 20 \Omega$  (complete at home).

**Section F:** Plot  $V$  vs.  $t$  at  $C, D, E$ , and  $F$  (complete at home).

**Section G:**

Complete the following table with the line terminated in a short circuit:

Frequency (MHz)	Length ( $\lambda$ )	$V_I$	$V_g$

Complete the following table with the line terminated in a 0.01  $\mu\text{f}$  capacitor:

Frequency (MHz)	Length ( $\lambda$ )	$V_I$	$V_g$

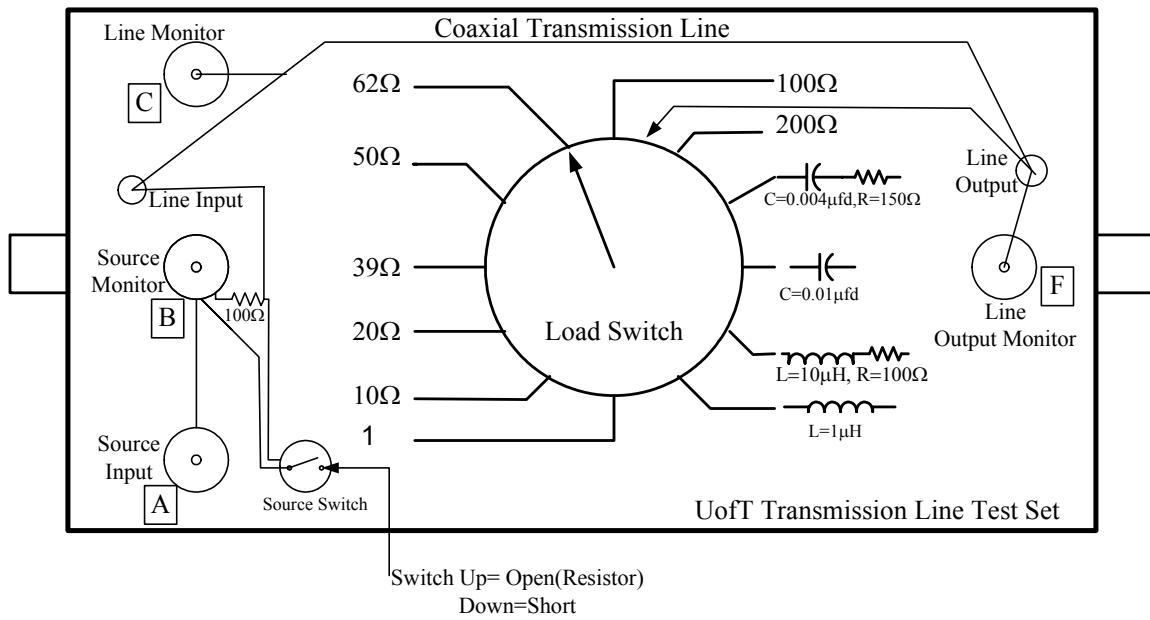


Figure 2. Transmission Line Test Set