

Answer the following questions:

a) What is the defining equation for a lossy transmission line (TL) characteristic impedance. (1 pt)

$$Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-}$$


b) Give an expression for a lossy transmission line characteristic impedance in terms of the line capacitance, inductance, etc. (1 Pt) $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

c) Write the voltage wave equation for a lossy transmission line. (Make sure you define your variables) (1 pt) $\frac{\partial^2 V(z)}{\partial z^2} = \gamma^2 V(z)$ where $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$

d) Write the solution to the equation you found in part (c). (Make sure you define your variables) (1 pt) $V = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$ V_0^+ & V_0^- are constants

e) Define the voltage reflection coefficient at the load, and explain what do we mean by a matched line. (1 pt) $\Gamma(z=l) = \frac{V_0^- e^{+\gamma l}}{V_0^+ e^{-\gamma l}} = \frac{Z_L - Z_0}{Z_L + Z_0}$; for matched line $Z_L = Z_0 \Rightarrow \Gamma(z=l) = \Gamma_L = 0$

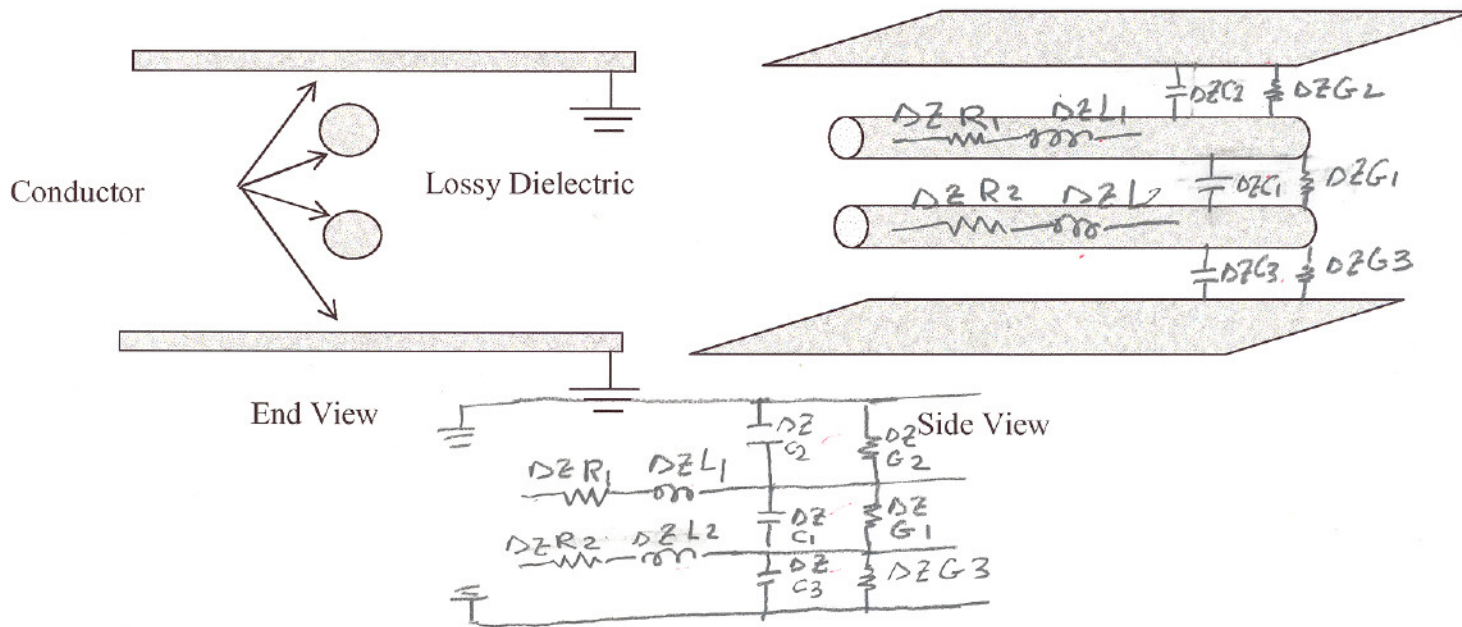f) Figures below show a shielded two-wire transmission line. On the figure to the right draw a distributed parameter model for this two wire transmission line. (Make sure you indicated what each element of your model represents) (5 pts)



Q2:

$$V_g = 10 \angle 0$$

$$R_o = 50 [\Omega]$$

$$l = 50 [m]$$

$$\omega = 2\pi \times 10^8 [Hz]$$

$$Z_g = R_g = 25 [\Omega]$$

$$R_L = 50 [\Omega]$$

$$V_p = 1 \times 10^8 [m/s]$$

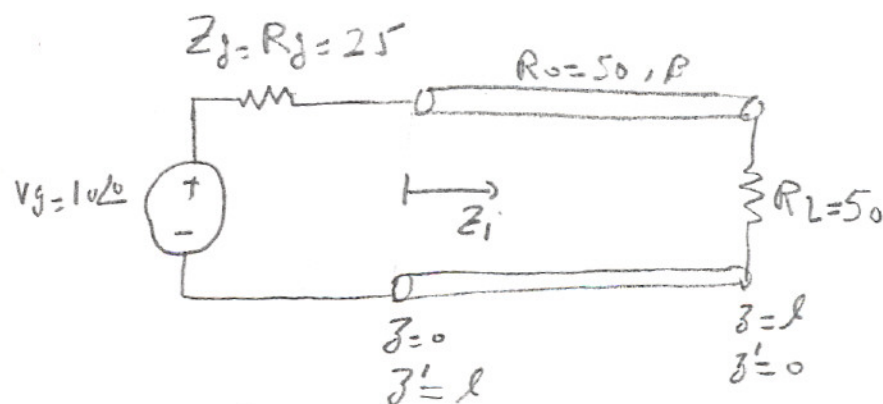


Fig 1.

$$\Gamma + \Gamma' = l$$

a) We find $V(z)$ & $I(z)$ in phasor form & from them obtain the instantaneous $v(z,t)$ & $i(z,t)$.

As far as the input to the line is concerned the Fig. 1

can be replaced with



where Z_i is the impedance at the input to the line

$$\textcircled{1} Z_i = R_o \frac{R_L + jR_o \tan \beta l}{R_o + jR_L \tan \beta l} \quad \text{for } R_L = R_o \Rightarrow$$

$$\textcircled{2} Z_i = R_o$$

$$\text{Then } \textcircled{3} V_i = V_g \frac{Z_i}{Z_i + R_g} = V_g \frac{R_o}{R_o + R_g} = 10 \frac{50}{50 + 25} = \frac{500}{75} = \frac{20}{3} = 6.667 [V]$$

$$\textcircled{4} I_i = \frac{V_i}{Z_i} = \frac{V_i}{R_o} = \frac{V_g}{R_o + R_g} = \frac{10}{50 + 25} = \frac{10}{75} = \frac{2}{15} = 0.1333 [A]$$

x since line is matched we can write

$$⑤ V = V_i e^{-j\beta z}$$

$$⑥ I = I_i e^{-j\beta z}$$

but what is β

$$\beta = \frac{\omega}{v_p} = \frac{2\pi \times 10^8}{1 \times 10^8} = 2\pi$$

If we want we can calculate $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{2\pi} = 1$

$$\text{Then } V(z) = V_i e^{-j\beta z} = 6.667 e^{-j2\pi z}$$

$$I(z) = I_i e^{-j\beta z} = 0.1333 e^{-j2\pi z}$$

The instantaneous fields are given by

$$v(z, t) = \text{Re}[V(z) e^{j\omega t}] = \text{Re}[6.667 e^{-j2\pi z} e^{j\omega t}] \Rightarrow$$

$$v(z, t) = 6.667 \cos(\omega t - 2\pi z) = 6.667 \cos(2\pi \times 10^8 t - 2\pi z) \quad [V]$$

$$i(z, t) = \text{Re}[I(z) e^{j\omega t}] = \text{Re}[0.1333 e^{-j2\pi z} e^{j\omega t}] \Rightarrow$$

$$i(z, t) = 0.1333 \cos(\omega t - 2\pi z) = 0.1333 \cos(2\pi \times 10^8 t - 2\pi z) \quad [Amp]$$

b) At load $z = l = 5$

$$V_L = 6.667 \cos(2\pi \times 10^8 t - 10\pi) = 6.667 \cos(2\pi \times 10^8 t) \quad [V]$$

$$I_L = 0.1333 \cos(2\pi \times 10^8 t - 10\pi) = 0.1333 \cos(2\pi \times 10^8 t) \quad [Amp]$$

c) $(P_{ave})_{Load} = (P_{ave})_{in}$ since matched line & lossless $\Rightarrow$

$$(P_{ave})_{Load} = \frac{1}{2} \text{Re}[V_i I_i^*] = \frac{1}{2} \text{Re}[6.667 \times 0.1333] = 0.444 [Watt]$$

Q3:

Sol: ① $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$

② $I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$ ③

We first recognize the fact that since $\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0$ (1) & (2)

Can be written as-

④ $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$

⑤ $I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$

Also note that the line is lossless.

* At $z=0$ (B.c) we have $V_i = V_0^+ + V_0^-$ ⑥

$I_i = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$ ⑦ $\Rightarrow I_i Z_0 = V_0^+ - V_0^-$ ⑧

$\therefore$ (6) & (8) are the unknown $(V_0^+ \& V_0^-)$ & two equations that can be solved $\Rightarrow$

⑨ $V_0^+ = \frac{V_i + I_i Z_0}{2}$ & $V_0^- = \frac{V_i - I_i Z_0}{2}$ ⑩

Sub (9) & (10) in (4) & (5) & we have

⑪ $V(z) = \left(\frac{V_i + I_i Z_0}{2} \right) e^{-j\beta z} + \left(\frac{V_i - I_i Z_0}{2} \right) e^{+j\beta z}$

⑫ $I(z) = \left(\frac{V_i + I_i Z_0}{2 Z_0} \right) e^{-j\beta z} - \left(\frac{V_i - I_i Z_0}{2 Z_0} \right) e^{+j\beta z}$

or equivalently

$$(13) \quad V(z) = V_i \frac{e^{j\beta z} + e^{-j\beta z}}{2} - I_i Z_0 \frac{e^{j\beta z} - e^{-j\beta z}}{2}$$

$$(14) \quad I(z) = I_i \frac{e^{j\beta z} - e^{-j\beta z}}{2} - \frac{V_i}{Z_0} \frac{e^{j\beta z} - e^{-j\beta z}}{2}$$

b) Above can also be written as-

$$(15) \quad V(z) = V_i \cos(\beta z) - j I_i Z_0 \sin(\beta z)$$

$$(16) \quad I(z) = I_i \cos(\beta z) - j \frac{V_i}{Z_0} \sin(\beta z)$$

Q 4%

$$l = 0.5 \text{ [m]}$$

$$f_1 = 100 \times 10^6 \text{ [Hz]}$$

$$R_0 = 50 \text{ [\Omega]}$$

$$f_2 = 200 \times 10^6 \text{ [Hz]}$$

$$V_p = 3 \times 10^8$$

we know that $Z_i = R_0 \frac{R_L + j R_0 \tan(\beta l)}{R_0 + j R_L \tan(\beta l)}$ $\beta = \omega$

If $R_L = 0 \Rightarrow Z_i = j R_0 \tan(\beta l)$

a) $\beta_1 = \frac{\omega_1}{V_p} = \frac{2\pi \times 100 \times 10^6}{3 \times 10^8} = 2\pi/3$

$$Z_1 = j 50 \tan\left(\frac{2\pi}{3} \times 0.5\right) = j 86.6025$$

This looks like the impedance of an inductor for which

$$Z = j\omega L \Rightarrow L = \frac{86.6025}{2\pi \times 100 \times 10^6} = 1.378 \times 10^{-7} \text{ [H]}$$

b) $\beta_2 = \frac{\omega_2}{V_p} = \frac{2\pi \times 200 \times 10^6}{3 \times 10^8} = 4\pi/3$


$$Z_i = j 50 \tan\left(\frac{4\pi}{3} \times 0.5\right) = -j 86.6025 \text{ [\Omega]}$$

It looks like the impedance of a capacitor for which

$$Z = \frac{-j}{\omega C} \Rightarrow \frac{1}{\omega C} = 86.6025 \Rightarrow C = \frac{1}{2\pi \times 200 \times 10^6 \times 86.6025} =$$

$$C = 9.1888 \times 10^{-12} \text{ [F]}$$


Q 5:

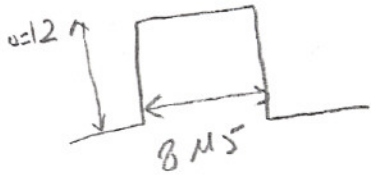



* Time to go from $z=0$ to $z=L$

$$T = \frac{L}{V_p} = \frac{600}{2 \times 10^8} = 3 \times 10^{-6} = 3 \text{ } \mu\text{s}$$

Reflection diagram for leading edge

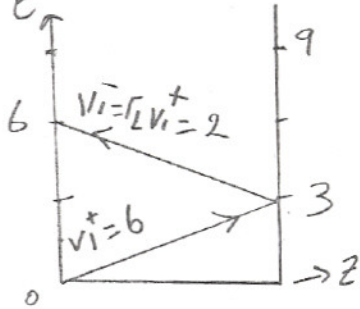

Reflection diagram for the tail

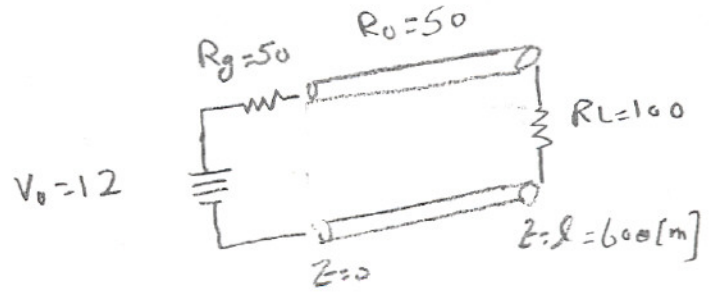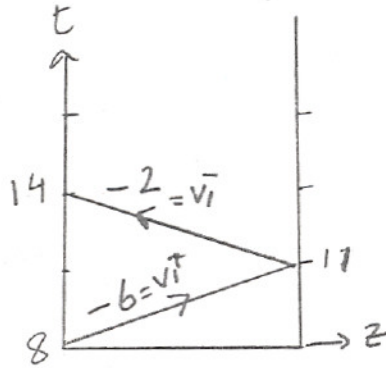


$$V_p = 2 \times 10^8 \text{ m/s}$$



$$V_1^+ = 12 \times \frac{50}{50+50} = 6 \text{ [V]}$$

$$\Gamma_L = \frac{100-50}{100+50} = \frac{50}{150} = 1/3$$
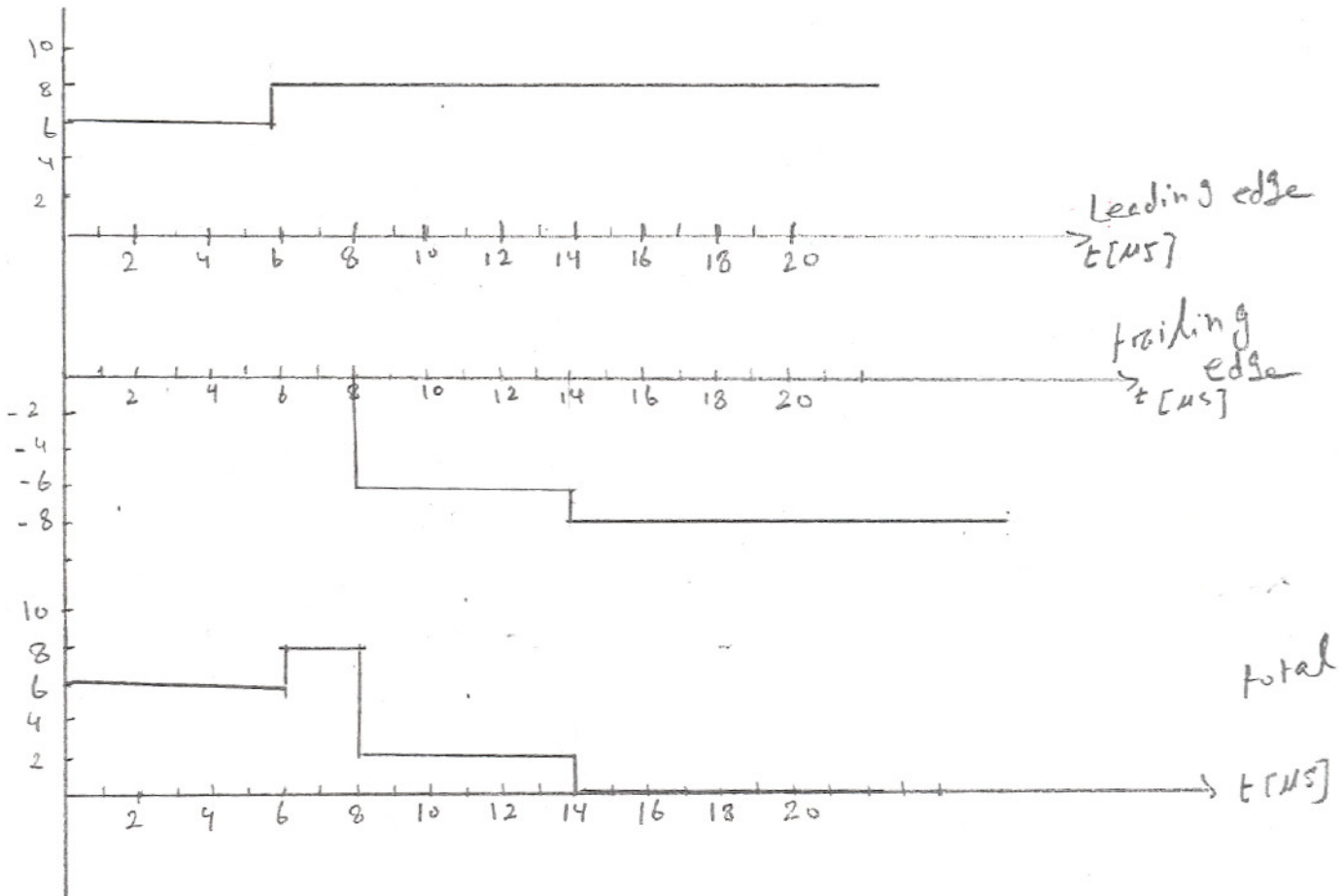
$$\Gamma_g = \frac{R_g - R_0}{R_g + R_0} = 0$$



$$Q.6: \quad Z_0 + Z_g \quad (1 - \Gamma_g e^{-j2\beta l})$$

$$a) V_i = \frac{Z_0}{Z_0 + Z_g} V_g = \frac{300}{300 + 300} 60 \angle 0^\circ = \boxed{30 \angle 0^\circ \text{ V}}$$

$$-\frac{8\pi}{5} = -5.03$$

$$b) V_L = V_i e^{-j\beta l} = 30 \angle 0^\circ e^{-j \frac{4\pi}{5} \cdot 2} = \boxed{30 \angle \frac{-8\pi}{5} \text{ or } 30 \angle -288^\circ}$$

$$l = 2 \text{ m}, \quad \beta = \frac{\omega}{v_p} = \frac{2\pi \cdot 100 \times 10^6}{2.5 \times 10^8} = \frac{2\pi}{2.5} = \frac{4\pi}{5} \text{ m}^{-1}$$

$$c) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{300 - 300}{300 + 300} = 0, \quad S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0}{1 - 0} = \boxed{1}$$

$$d) P_{ave} = \frac{1}{2} \frac{|V_L|^2}{R_L} = \frac{1}{2} \frac{|30 \angle \frac{-8\pi}{5}|^2}{300} = \frac{30^2}{2 \cdot 300} = \boxed{1.5 \text{ W}}$$

$$e) Z_L = \frac{1}{\frac{1}{300} + \frac{1}{300}} = 150 \Omega, \quad \Gamma = \frac{150 - 300}{150 + 300} = -\frac{1}{3}, \quad S = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = \boxed{2}$$

$$f) z = l, \quad z' = l - z = 0, \quad \Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = 0, \quad V(z') = \frac{Z_0 V_g}{Z_0 + Z_g} e^{-j\beta z'} \left(\frac{1 + \Gamma e^{-2j\beta z'}}{1 - \Gamma_g \Gamma e^{-2j\beta l}} \right) \Rightarrow$$

$$V(0) = \frac{300}{300 + 300} 60 e^{-j\beta l} \left[\frac{1 - \frac{1}{3} e^{-j2\beta \cdot 0}}{1 - 0} \right] = 30 e^{-j \frac{8\pi}{5}} \left(1 - \frac{1}{3} \right) = 20 \angle \frac{-8\pi}{5}$$

$$P_{ave} = \frac{1}{2} \frac{|V(0)|^2}{R_L} = \frac{1}{2} \frac{|20 \angle \frac{-8\pi}{5}|^2}{150} = \frac{20^2}{2 \cdot 150} = \boxed{1.33 \text{ W}}$$